 


Binary Logic and Gates


- ✓ Binary variables take on one of two values.
- ✓ Logical operators operate on binary values and binary variables.
- ✓ Basic logical operators are the logic functions AND, OR and NOT.
- ✓ Logic gates implement logic functions.
- ✓ Boolean Algebra: a useful mathematical system for specifying and transforming logic functions.
- ✓ We study Boolean algebra as a foundation for designing and analyzing digital systems!

George Boole (1815-1864)




An Investigation of the Laws
of Thought, on Which are
founded the Mathematical
Theories of Logic and
Probabilities (1854)

Claude Shannon (1916-2001)

 

A Symbolic Analysis of Relay and Switching Circuits (1938)

 ENIAC (1946)
Electronic
Numerical
Integrator
And
Calculator




Binary Variables

- ✓ Recall that the two binary values have different names:
 - True/False
 - On/Off
 - Yes/No
 - 1/0
- ✓ We use 1 and 0 to denote the two values.
- ✓ Variable identifier examples:
 - A, B, y, z, or X_1 for now
 - RESET, START_IT, or ADD1 later

Boolean functions

 - ✓ Basic logical operators are the boolean functions



The Boolean n-cube B^n





- ✓ $B = \{0,1\}$
- ✓ $B^2 = \{0,1\} \times \{0,1\} = \{00, 01, 10, 11\}$
- ✓ Arrangement of function table on a hypercube
 - The function value f_j is **adjacent** in each dimension of the hypercube to f_k where k is obtained from j by complementing one and only one input variable: $X_0 X_1 \dots X_n$

is adjacent to

$$\bar{X}_0 X_1 \dots X_n$$

$$X_0 \bar{X}_1 \dots X_n$$

$$X_0 X_1 \dots \bar{X}_n$$

    

Boolean Functions

Boolean Function: $f(x) : B^n \rightarrow B$

$B = \{0,1\}$


$x = (x_1, x_2, \dots, x_n) \in B^n; x_i \in B$

- x_1, x_2, \dots are **variables**
- $x_1, \bar{x}_1, x_2, \bar{x}_2, \dots$ are **literals**
- essentially: f maps each vertex of B^n to 0 or 1

Example:



$f = \{((x_1 = 0, x_2 = 0), 0), ((x_1 = 0, x_2 = 1), 1),$
 $((x_1 = 1, x_2 = 0), 1), ((x_1 = 1, x_2 = 1), 0)\}$

		x_2
		\rightarrow
x_1	\downarrow	
	0	1
	1	0

 

Boolean Functions

- The **Onset** of f is $\{x \mid f(x) = 1\} = f^{-1}(1) = f^1$
- The **Offset** of f is $\{x \mid f(x) = 0\} = f^{-1}(0) = f^0$
- if $f^1 = B^n$, f is the **tautology**. i.e. $f \equiv 1$
- if $f^0 = B^n$ ($f^1 = \emptyset$), f is **not satisfiable**, i.e. $f \equiv 0$
- if $f(x) = g(x)$ for all $x \in B^n$, then f and g **are equivalent**
- we say f instead of f^1
- literals: A **literal** is a variable or its negation x, \bar{x} and represents a logic function

  

Logical Operations

- ✓ The three basic logical operations are:
 - AND
 - OR
 - NOT
- ✓ AND is denoted by a dot (\bullet).
- ✓ OR is denoted by a plus ($+$).
- ✓ NOT is denoted by an overbar ($\bar{\quad}$), a single quote mark ($'$) after, or (\sim) before the variable.
- ✓ The order of evaluation in a Boolean expression is:
 1. Parentheses
 2. NOT
 3. AND
 4. OR
- ✓ Consequence: Parentheses appear around OR expressions
- ✓ Example: $F = A(B + C)(C + D)$

Fundamentals of Boolean Algebra

✓ Basic Postulates

- **Postulate 1 (Definition):** A Boolean algebra is a closed algebraic system containing a set K of two or more elements and the operators \bullet , $+$ and $\bar{}$.
- **Postulate 2 (Existence of 1 and 0 element):**
 - a) $a + 0 = a$ (identity for $+$),
 - b) $a \bullet 1 = a$ (identity for \bullet)
- **Postulate 3 (Commutativity):**
 - a) $a + b = b + a$
 - b) $a \bullet b = b \bullet a$
- **Postulate 4 (Associativity):**
 - a) $a + (b + c) = (a + b) + c$
 - b) $a \bullet (b \bullet c) = (a \bullet b) \bullet c$
- **Postulate 5 (Distributivity):**
 - a) $a + (b \bullet c) = (a + b) \bullet (a + c)$
 - b) $a \bullet (b + c) = a \bullet b + a \bullet c$
- **Postulate 6 (Existence of complement):**
 - a) $a + \bar{a} = 1$
 - b) $a \bullet \bar{a} = 0$

Normally \bullet is omitted.

A switching algebra is a BA with $K=\{0,1\}$

Notation Examples

✓ Examples:

- $Y = A \cdot B$ is read "Y is equal to A AND B"
- $z = x + y$ is read "z is equal to x OR y"
- $X = \overline{A}$ is read "X is equal to NOT A"

■ Note: The statement:

$1 + 1 = 2$ (+ is an algebraic operator, read "one plus one equals two")

is not the same as

$1 + 1 = 1$ (+ is a logic operator, read "1 or 1 equals 1").

Operator Definitions

- ✓ Operations are defined on the values "0" and "1" for each operator:

AND

$$0 \cdot 0 = 0$$

$$0 \cdot 1 = 0$$

$$1 \cdot 0 = 0$$

$$1 \cdot 1 = 1$$

OR

$$0 + 0 = 0$$

$$0 + 1 = 1$$

$$1 + 0 = 1$$

$$1 + 1 = 1$$

NOT

$$\bar{0} = 1$$

$$\bar{1} = 0$$

Boolean Algebra

- An algebraic structure defined on a set of at least two elements, B , together with three binary operators (denoted $+$, \cdot and $\bar{}$) that satisfies the following basic identities:

1. $X + 0 = X$

2. $X \cdot 1 = X$

Existence of 0 and 1

3. $X + 1 = 1$

4. $X \cdot 0 = 0$

5. $X + X = X$

6. $X \cdot X = X$

Idempotence

7. $X + \bar{X} = 1$

8. $X \cdot \bar{X} = 0$

Existence of complement

9. $\overline{\overline{X}} = X$

Involution

10. $X + Y = Y + X$

11. $XY = YX$

Commutative

12. $(X + Y) + Z = X + (Y + Z)$

13. $(XY)Z = X(YZ)$

Associative

14. $X(Y + Z) = XY + XZ$

15. $X + YZ = (X + Y)(X + Z)$

Distributive

16. $\overline{X + Y} = \bar{X} \cdot \bar{Y}$

17. $\overline{X \cdot Y} = \bar{X} + \bar{Y}$

De Morgan's

Generalized De Morgan's theorems

$$\overline{X_1 X_2 \dots X_n} = \overline{X_1} + \overline{X_2} + \dots + \overline{X_n}$$

$$\overline{\overline{X_1} + \overline{X_2} + \dots + \overline{X_n}} = \overline{X_1} \overline{X_2} \dots \overline{X_n}$$

- ✓ Proof Generalized De Morgan's theorems by general induction:

Two steps:

- Show that the statement is true for two variables
- Show that if is true for n variable , than is also true for n+1 variables:

$$\begin{aligned} \text{Let } Z &= X_1 + X_2 + \dots + X_n \\ \overline{(X_1 + X_2 + \dots + X_n + X_{n+1})} &= \overline{(Z + X_{n+1})} = \overline{(Z \cdot \overline{X_{n+1}})} = \\ &(\overline{X_1} \cdot \overline{X_2} \cdot \dots \cdot \overline{X_n}) \cdot \overline{X_{n+1}} \text{ by induction hypothesis} \end{aligned}$$

Example 1: Boolean Algebraic Proof

✓ $A + A \cdot B = A$

Absorption Theorem

Proof Steps

Justification

$$A + A \cdot B$$

$$= A \cdot 1 + A \cdot B$$

$$X = X \cdot 1$$

$$= A \cdot (1 + B)$$

$$X \cdot Y + X \cdot Z = X \cdot (Y + Z) \quad \text{Distributive Law}$$

$$= A \cdot 1$$

$$1 + X = 1$$

$$= A$$

$$X \cdot 1 = X$$

Some Properties of Identities & the Algebra

- ✓ The dual of an algebraic expression is obtained by interchanging + and \cdot and interchanging 0's and 1's.
- ✓ Unless it happens to be self-dual, the dual of an expression does not equal the expression itself.
- ✓ Example: $F = (A + \bar{C}) \cdot B + 0$
dual $F = ((A \cdot \bar{C}) + B) \cdot 1 = A \cdot \bar{C} + B$
- ✓ Example: $G = X \cdot Y + \overline{(W + Z)}$
dual $G = (X + Y) \cdot \overline{(W \cdot Z)} = (X + Y) \cdot (\bar{W} + \bar{Z})$
- ✓ Example: $H = A \cdot B + A \cdot C + B \cdot C$
dual $H = (A + B)(A + C)(B + C) = (A + AC + BA + BC)(B + C)$
 $= (A + BC)(B + C) = AB + AC + BC$. So H is self-dual.
- ✓ Are any of these functions self-dual?

Some Properties of Identities & the Algebra

- ✓ There can be more than 2 elements in B , i. e., elements other than 1 and 0. What are some common useful Boolean algebras with more than two elements?
 1. Algebra of Sets
 2. Algebra of n -bit binary vectors
 3. Quantified Boolean Algebra (QBA)
- ✓ If B contains only 1 and 0, then B is called the switching algebra which is the algebra we use most often.

Quantified Boolean formulas (QBFs)

- ✓ *Generalize (quantifier-free) Boolean formulas* with the additional universal and existential quantifiers: \forall and \exists , respectively.
- ✓ In writing a QBF, we assume that the precedences of the quantifiers are lower than those of the Boolean connectives.
- ✓ In a QBF, variables being quantified are called *bound variables*, whereas those not quantified are called *free variables*.
- ✓ Any QBF can be rewritten as a quantifier-free Boolean formula through quantifier elimination by formula expansion (among other methods), e.g.,

$$\forall x: f(x; y) = f(0; y) \cdot f(1; y)$$

and

$$\exists x: f(x; y) = f(0; y) + f(1; y)$$

- ✓ Consequently, for any QBF φ , there exists an equivalent quantifier-free Boolean formula that refers only to the free variables of φ .
- ✓ QBFs are thus of the same expressive power as quantifier-free Boolean formulas, but can be more succinct.

Example 2: Boolean Algebraic Proofs

$$\checkmark AB + \overline{AC} + BC = AB + \overline{AC}$$

Consensus Theorem

Proof Steps

$$\begin{aligned} & AB + \overline{AC} + BC \\ = & AB + \overline{AC} + 1 \cdot BC \\ = & AB + \overline{AC} + (A + \overline{A}) \cdot BC \\ = & AB + \overline{AC} + ABC + \overline{A}BC \\ = & AB \cdot (1 + C) + \overline{AC} \cdot (1 + B) \\ = & AB + \overline{AC} \end{aligned}$$

$$\checkmark (A+B) \cdot (\overline{A}+C) \cdot (B+C) = (A+B) \cdot (\overline{A}+C) \quad \text{dual identity}$$

Example 3: Boolean Algebraic Proofs

✓ $(\overline{X + Y})Z + X\overline{Y} = \overline{Y}(X + Z)$

Proof Steps

Justification

$$(\overline{X + Y})Z + X\overline{Y}$$

$$= X' Y' Z + X Y'$$

$$= Y' X' Z + Y' X$$

$$= Y' (X' Z + X)$$

$$= Y' (X' + X)(Z + X)$$

$$= Y' \cdot 1 \cdot (Z + X)$$

$$= Y' (X + Z)$$

$$(A + B)' = A' \cdot B'$$

$$A \cdot B = B \cdot A$$

$$A(B + C) = AB + AC$$

$$A + BC = (A + B)(A + C)$$

$$A + A' = 1$$

$$1 \cdot A = A, A + B = B + A$$

De Morgan's Law

Commutative Law

Distributive Law

Distributive Law

Commutative Law

Useful Theorems

✓ $X \cdot Y + \bar{X} \cdot Y = Y$ $(X + Y) \cdot (\bar{X} + Y) = Y$ Minimization

✓ $X + X \cdot Y = X$ $X \cdot (X + Y) = X$ Absorption

✓ $X + \bar{X} \cdot Y = X + Y$ $X \cdot (\bar{X} + Y) = X \cdot Y$ Simplification

✓ $X \cdot Y + \bar{X} \cdot Z + Y \cdot Z = X \cdot Y + \bar{X} \cdot Z$ Consensus
 $(X + Y) \cdot (\bar{X} + Z) \cdot (Y + Z) = (X + Y) \cdot (\bar{X} + Z)$

✓ $\overline{X + Y} = \bar{X} \cdot \bar{Y}$ $\overline{X \cdot Y} = \bar{X} + \bar{Y}$ De Morgan's Law

Boolean Function Evaluation

$$F1 = xy\bar{z}$$

$$F2 = x + \bar{y}z$$

$$F3 = \bar{x}\bar{y}\bar{z} + \bar{x}yz + x\bar{y}$$

$$F4 = x\bar{y} + \bar{x}z$$

x	y	z	F1	F2	F3	F4
0	0	0	0	0		
0	0	1	0	1		
0	1	0	0	0		
0	1	1	0	0		
1	0	0	0	1		
1	0	1	0	1		
1	1	0	1	1		
1	1	1	0	1		

Expression Simplification

- ✓ An application of Boolean algebra
- ✓ Simplify to contain the smallest number of literals (complemented and un-complemented variables):

$$AB + \bar{A}CD + \bar{A}BD + \bar{A}C\bar{D} + ABCD$$

$$\begin{aligned} &= AB + ABCD + \bar{A}CD + \bar{A}C\bar{D} + \bar{A}BD \\ &= AB + AB(CD) + \bar{A}C(D + \bar{D}) + \bar{A}BD \\ &= AB + \bar{A}C + \bar{A}BD = B(A + \bar{A}D) + \bar{A}C \\ &= B(A + D) + \bar{A}C \end{aligned}$$

Complementing Functions

✓ Use DeMorgan's Theorem to complement a function:

1. Interchange AND and OR operators

2. Complement each constant value and literal

✓ Example: Complement $F = \bar{x}y\bar{z} + x\bar{y}z$

$$\bar{F} = (x + \bar{y} + z)(\bar{x} + y + \bar{z})$$

✓ Example: Complement $G = (\bar{a} + bc)\bar{d} + e$

$$\bar{G} =$$

$$((a(\bar{b} + \bar{c})) + d)\bar{e} = (a(\bar{b} + \bar{c}) + d)\bar{e}$$

Shannon Expansion

- ✓ Let $f : B^n \rightarrow B$ be a Boolean function, and $x = (x_1, x_2, \dots, x_n)$ the variables in the support of f . The cofactor (residual) f_a of f by a literal $a=x_i$ or $a=\bar{x}_i$ is:

$$f_{x_i}(x_1, x_2, \dots, x_n) = f(x_1, \dots, x_{i-1}, 1, x_{i+1}, \dots, x_n)$$

$$f_{\bar{x}_i}(x_1, x_2, \dots, x_n) = f(x_1, \dots, x_{i-1}, 0, x_{i+1}, \dots, x_n)$$

- ✓ Shannon theorem:

$$f = x_i f_{x_i} + \bar{x}_i f_{\bar{x}_i}$$



- ✓ We say that f is **expanded** about x_i . x_i is called the **splitting variable**.

Example

$$F = ab + ac + bc$$

$$F = a F_a + \bar{a} F_{\bar{a}}$$

$$F = ab + ac + abc + \bar{a}bc$$

  

Cube **bc** got split into two cubes

Representation of Boolean Functions

- ✓ We need representations for Boolean Functions for two reasons:
 - to represent and manipulate the **actual circuit we are "synthesizing"**
 - as mechanism to do efficient **Boolean reasoning**
- ✓ **Forms to represent Boolean Functions**
 - Truth table
 - List of cubes (Sum of Products, Disjunctive Normal Form (DNF))
 - List of conjuncts (Product of Sums, Conjunctive Normal Form (CNF))
 - Boolean formula
 - Binary Decision Tree, Binary Decision Diagram
 - Circuit (network of Boolean primitives)

Truth Table

- ✓ Truth table (Function Table):

The truth table of a function $f : B^n \rightarrow B$ is a tabulation of its value at each of the 2^n vertices of B^n .

- ✓ In other words the truth table lists all **minterms**

Example: $f = \overline{a}\overline{b}\overline{c}\overline{d} + \overline{a}\overline{b}c\overline{d} + \overline{a}b\overline{c}\overline{d} + \overline{a}b\overline{c}d + \overline{a}bc\overline{d} + \overline{a}bcd + a\overline{b}\overline{c}\overline{d} + a\overline{b}\overline{c}d + a\overline{b}c\overline{d} + a\overline{b}cd + ab\overline{c}\overline{d} + ab\overline{c}d + abc\overline{d} + abcd$

The truth table representation is

- intractable for large n
- canonical

	<u>abcd</u>	<u>f</u>		<u>abcd</u>	<u>f</u>
0	0000	0	8	1000	0
1	0001	1	9	1001	1
2	0010	0	10	1010	0
3	0011	1	11	1011	1
4	0100	0	12	1100	0
5	0101	1	13	1101	1
6	0110	0	14	1110	1
7	0111	0	15	1111	1

Truth Tables

- ✓ *Truth table* – a tabular listing of the values of a function for all possible combinations of values on its arguments
- ✓ Example: Truth tables for the basic logic operations:

AND

X	Y	$Z=X \cdot Y$
0	0	0
0	1	0
1	0	0
1	1	1

OR


X	Y	$Z=X+Y$
0	0	0
0	1	1
1	0	1
1	1	1

NOT

X	$Z=\overline{X}$
0	1
1	0

Set of Boolean Functions

✓ Truth Table or Function table:

 

x_1	x_2	x_3	
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	$\Rightarrow 1$
1	0	1	0
1	1	0	1
1	1	1	0

- ✓ There are 2^n vertices in input space B^n
- ✓ There are 2^{2^n} distinct logic functions.
 - Each subset of vertices is a distinct logic function:
 $f \subseteq B^n$

Cubes




- ✓ A cube is defined as the AND of a set of literals ("conjunction" of literals).

Example:

$$C = \bar{x}_1 x_2 \bar{x}_3$$

represents the following function

$$f = (x_1=0)(x_2=1)(x_3=0)$$

   

Cubes

- ✓ If $C \subseteq f$, C a cube, then C is an implicant of f .
- ✓ If $C \subseteq B^n$, and C has k literals, then $|C|$ covers 2^{n-k} vertices.

Example:

$$C = x\bar{y} \subseteq B^3$$

$$k = 2, n = 3 \Rightarrow |C| = 2 = 2^{3-2}.$$

$$C = \{100, 101\}$$

- ✓ An implicant with n literals is a **minterm**.

List of Cubes

✓ Sum of Products (SOP):

- A function can be represented by a sum of cubes (products):

$$f = ab + ac + bc$$

Since each cube is a product of literals, this is a "sum of products" (SOP) representation



- A SOP can be thought of as a set of cubes F

$$F = \{ab, ac, bc\}$$


- A set of cubes that represents f is called a cover of f .

$$F_1 = \{ab, ac, bc\} \text{ and } F_2 = \{abc, abc\bar{b}, a\bar{b}c, \bar{a}bc\}$$

are covers of
 $f = ab + ac + bc$.

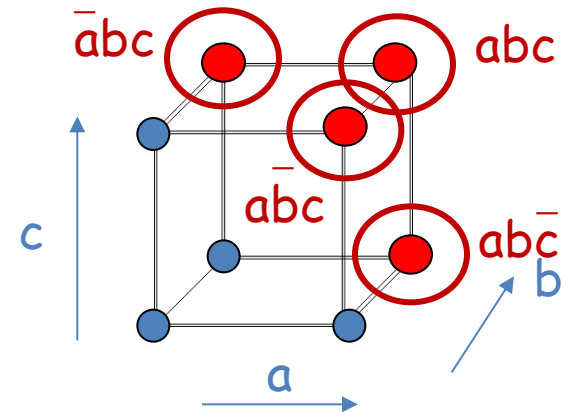 

Sum Of Products - SOP

 

● = onset minterm

Note that each onset minterm is "covered" by at least one of the cubes, and these do not covers offset minterm.

- ✓ Two-level minimization seeks the minimum size cover (least number of cubes)



Irredundant

✓ Let $F = \{c_1, c_2, \dots, c_k\}$ be a cover for f :

$$f = \sum_{i=1}^k c_i$$

A cube $c_i \in F$ is **irredundant** if $F \setminus \{c_i\} \neq f$

Example 2: $f = ab + ac + bc$

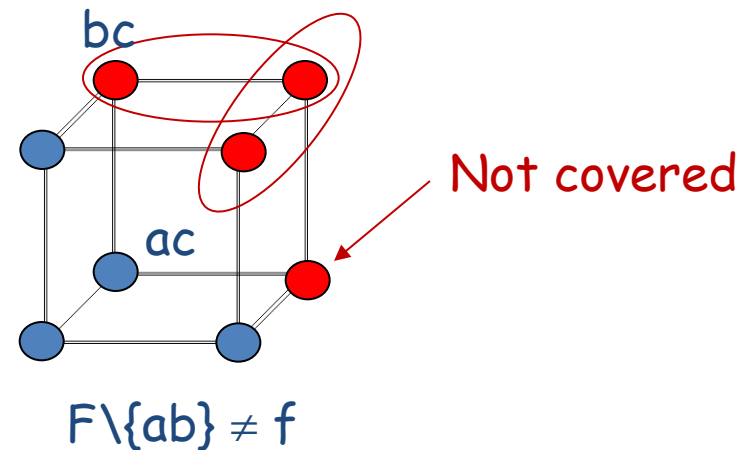 

Prime

✓ A **literal** j of cube $c_i \in F (=f)$ is **prime** if

$$(F \setminus \{c_i\}) \cup \{c'_i\} \neq f$$

where c'_i is c_i with literal j of c_i deleted.

✓ A **cube** of F is prime if all its literals are **prime**.

Example 3

$$f = ab + ac + bc$$


$$c_i = ab; c'_i = a \text{ (literal } b \text{ deleted)}$$

$$F \setminus \{c_i\} \cup \{c'_i\} = a + ac + bc$$

Not equal to f since
offset vertex is covered

$$F = ac + bc + a =$$

$$F \setminus \{c_i\} \cup \{c'_i\}$$

 

Prime and Irredundant Covers


- ✓ Definition 1 A cover is prime (irredundant) if all its cubes are prime (irredundant).
- ✓ Definition 2 A prime of f is **essential** (essential prime) if there is a minterm (essential vertex) in that prime but in no other prime.

Prime and Irredundant Covers

 Example 4



$f = abc + \bar{b}d + \bar{c}d$ is prime and irredundant.

abc is *essential* since $abcd \in abc$, but not in $\bar{b}d$ or $\bar{c}d$



Binary Decision Diagram (BDD)

  - ✓ Graph representation of a Boolean function f
 - vertices represent decision nodes for variables
 - two children represent the two subfunctions
 - $f(x = 0)$ and $f(x = 1)$ (cofactors)
 - restrictions on ordering and reduction rules can make a BDD representation canonical



Logic Functions

- ✓ However, there are infinite number of logic **formulas** and each one can have various forms:

$$f = x + y$$

$$= \bar{x}y + xy + x\bar{y}$$

$$= \bar{x}x + x\bar{y} + y$$

$$= (x + y)(\bar{x} + \bar{y}) + xy$$

x	y	f
0	0	0
0	1	1
1	0	1
1	1	1

- ✓ Synthesis = Find the best formula (or "representation")

Logic Function Implementation

✓ Using Switches


- For inputs:
 - logic 1 is switch closed
 - logic 0 is switch open

- For outputs:
 - logic 1 is light on
 - logic 0 is light off.



- NOT uses a switch such that:
- Normally-closed switch \Rightarrow NOT

- logic 1 is switch open
- logic 0 is switch closed

Switches in parallel \Rightarrow OR

 


Switches in series \Rightarrow AND

  

Logic Function Implementation (Continued)

✓ Example: Logic Using Switches

 

✓ Light is on ($L = 1$) for
 $L(A, B, C, D) = AD + ABC\bar{C}$
and off ($L = 0$), otherwise.


✓ Useful model for relay circuits and for CMOS gate circuits, the foundation of current digital logic technology

Logic Gates


- ✓ In the earliest computers, switches were opened and closed by magnetic fields produced by energizing coils in *relays*. The switches in turn opened and closed the current paths.
- ✓ Later, *vacuum tubes* that open and close current paths electronically replaced relays.
- ✓ Today, *transistors* are used as electronic switches that open and close current paths.

Logic Gate Symbols and Behavior

✓ Logic gates have special symbols:

 

 
✓ And waveform behavior in time as follows:



 (b) Timing diagram

Gate Delay

- ✓ In actual physical gates, if one or more input changes causes the output to change, the output change does not occur instantaneously.
- ✓ The delay between an input change(s) and the resulting output change is the *gate delay* denoted by t_G :



Logic Diagrams and Expressions


Truth Table

X Y Z	$F = X + \bar{Y} Z$
0 0 0	0
0 0 1	1
0 1 0	0
0 1 1	0
1 0 0	1
1 0 1	1
1 1 0	1
1 1 1	1

Equation

$$F = X + \bar{Y} Z$$

Logic Diagram

 

- ✓ Boolean equations, truth tables and logic diagrams describe the same function!
- ✓ Truth tables are unique; expressions and logic diagrams are not. This gives flexibility in implementing functions.

Boolean Circuits


Definition:

- ✓ A **Boolean circuit** is a directed graph $C(G, N)$ where G are the gates and $N \subseteq G \times G$ is the set of directed edges (nets) connecting the gates.
- ✓ Some of the vertices are designated:
 - Inputs:** $I \subseteq G$
 - Outputs:** $O \subseteq G, I \cap O = \emptyset$
- ✓ Each gate g is assigned a Boolean function f_g which computes the output of the gate in terms of its inputs.

Definitions

- ✓ The **fanin** $FI(g)$ of a gate g are all predecessor vertices of g :
 $FI(g) = \{g' \mid (g',g) \in N\}$
- ✓ The **fanout** $FO(g)$ of a gate g are all successor vertices of g :
 $FO(g) = \{g' \mid (g,g') \in N\}$
- ✓ The **cone** $CONE(g)$ of a gate g is the transitive fanin of g and g itself.
- ✓ The **support** $SUPPORT(g)$ of a gate g are all inputs in its cone:
 $SUPPORT(g) = CONE(g) \cap I$

Example

 

$$FI(6) = \{2,4\}$$

$$FO(6) = \{7,9\}$$

$$CONE(6) = \{1,2,4,6\}$$

$$SUPPORT(6) = \{1,2\}$$

Canonical Forms

- ✓ It is useful to specify Boolean functions in a form that:
 - Allows comparison for equality.
 - Has a correspondence to the truth tables
- ✓ Canonical Forms in common usage:
 - Sum of Minterms (SOM)
 - Product of Maxterms (POM)

Minterms

- ✓ **Minterms** are AND terms with every variable present in either true or complemented form.
- ✓ Given that each binary variable may appear normal (e.g., x) or complemented (e.g., \bar{x}), there are 2^n minterms for n variables.
- ✓ Example: Two variables (X and Y) produce $2 \times 2 = 4$ combinations:
 - $X Y$ (both normal)
 - $X \bar{Y}$ (X normal, Y complemented)
 - $\bar{X} Y$ (X complemented, Y normal)
 - $\bar{X} \bar{Y}$ (both complemented)
- ✓ Thus there are four minterms of two variables.

Maxterms

- ✓ **Maxterms** are OR terms with every variable in true or complemented form.
- ✓ Given that each binary variable may appear normal (e.g., x) or complemented (e.g., \bar{x}), there are 2^n maxterms for n variables.
- ✓ Example: Two variables (X and Y) produce $2 \times 2 = 4$ combinations:
 - $X Y$ (both normal)
 - $X \bar{Y}$ (x normal, y complemented)
 - $\bar{X} Y$ (x complemented, y normal)
 - $\bar{X} \bar{Y}$ (both complemented)

Maxterms and Minterms

- ✓ Examples: Two variable minterms and maxterms.

Index		Minterm	Maxterm
0	00	$\bar{x} \bar{y}$	$x + y$
1	01	$\bar{x} y$	$x + \bar{y}$
2	10	$x \bar{y}$	$\bar{x} + y$
3	11	$x y$	$\bar{x} + \bar{y}$

- ✓ The index above is important for describing which variables in the terms are true and which are complemented.

Standard Order

- ✓ Minterms and maxterms are designated with a subscript
- ✓ The subscript is a number, corresponding to a binary pattern
- ✓ The bits in the pattern represent the complemented or normal state of each variable listed in a standard order.
- ✓ All variables will be present in a minterm or maxterm and will be listed in the same order (usually alphabetically)
- ✓ Example: For variables a, b, c :
 - Maxterms: $(a + b + \bar{c})$, $(a + b + c)$
 - Terms: $(b + a + c)$, $a \bar{c} b$, and $(c + b + a)$ are NOT in standard order.
 - Minterms: $a \bar{b} c$, $a b c$, $a \bar{b} \bar{c}$
 - Terms: $(a + c)$, $\bar{b} c$, and $(\bar{a} + b)$ do not contain all variables

Purpose of the Index

- ✓ The index for the minterm or maxterm, expressed as a binary number, is used to determine whether the variable is shown in the true form or complemented form.
- ✓ For Minterms:
 - "1" means the variable is "Not Complemented" and
 - "0" means the variable is "Complemented".
- ✓ For Maxterms:
 - "0" means the variable is "Not Complemented" and
 - "1" means the variable is "Complemented".

Index Example in Three Variables

- ✓ Example (for three variables):
- ✓ Assume the variables are called X, Y, and Z.
- ✓ The standard order is X, then Y, then Z.
- ✓ The Index 0 (base 10) = 000 (base 2) (for three variables). All three variables are complemented for minterm 0 ($\overline{x}, \overline{y}, \overline{z}$) and no variables are complemented for Maxterm 0 (x,y,z).

- Minterm 0, called m_0 is $\overline{x} \overline{y} \overline{z}$.
- Maxterm 0, called M_0 is $(X + Y + Z)$.
- Minterm 6 ?

$$x y \overline{z}$$

- Maxterm 6 ?

$$(\overline{x} + \overline{y} + z)$$

Index Examples - Four Variables

Index	Binary	Minterm	Maxterm
i	Pattern	m_i	M_i
0	0000	$\bar{a}\bar{b}\bar{c}\bar{d}$	$a + b + c + d$
1	0001	$\bar{a}\bar{b}\bar{c}d$	$a + b + c + \bar{d}$
3	0011	?	?
5	0101	$\bar{a}b\bar{c}d$	$a + \bar{b} + c + \bar{d}$
7	0111	?	$a + \bar{b} + \bar{c} + \bar{d}$
10	1010	$\bar{a}b\bar{c}\bar{d}$	$\bar{a} + b + \bar{c} + d$
13	1101	$\bar{a}b\bar{c}d$?
15	1111	$abcd$	$\bar{a} + \bar{b} + \bar{c} + \bar{d}$

Minterm and Maxterm Relationship

- ✓ Review: De Morgan's Theorem

$$\overline{x \cdot y} = \bar{x} + \bar{y} \text{ and } \overline{\bar{x} + \bar{y}} = x \cdot y$$

- ✓ Two-variable example:

$$M_2 = \bar{x} + y \text{ and } m_2 = x \cdot \bar{y}$$

Thus M_2 is the complement of m_2 and vice-versa.

- ✓ Since De Morgan's Theorem holds for n variables, the above holds for terms of n variables giving:

$$M_i = \bar{m}_i \text{ and } m_i = \bar{M}_i$$

Thus M_i is the complement of m_i .

Function Tables for Both

- ✓ Minterms of 2 variables

$x y$	m_0	m_1	m_2	m_3
00	1	0	0	0
01	0	1	0	0
10	0	0	1	0
11	0	0	0	1

- Maxterms of 2 variables

$x y$	M_0	M_1	M_2	M_3
00	0	1	1	1
01	1	0	1	1
10	1	1	0	1
11	1	1	1	0

- ✓ Each column in the maxterm function table is the complement of the column in the minterm function table since M_i is the complement of m_i .

Observations

- ✓ In the function tables:
 - Each minterm has one and only one 1 present in the 2^n terms (a minimum of 1s). All other entries are 0.
 - Each maxterm has one and only one 0 present in the 2^n terms. All other entries are 1 (a maximum of 1s).
- ✓ We can implement any function by "ORing" the minterms corresponding to "1" entries in the function table. These are called the minterms of the function.
- ✓ We can implement any function by "ANDing" the maxterms corresponding to "0" entries in the function table. These are called the maxterms of the function.
- ✓ This gives us two **canonical forms**:
 - **Sum of Minterms (SOM)**
 - **Product of Maxterms (POM)**for stating any Boolean function.

Minterm Function Example

✓ Example: Find $F_1 = m_1 + m_4 + m_7$

✓ $F_1 = \overline{x} \overline{y} z + x \overline{y} \overline{z} + x y z$

x y z	index	m_1	+	m_4	+	m_7	= F_1
0 0 0	0	0	+	0	+	0	= 0
0 0 1	1	1	+	0	+	0	= 1
0 1 0	2	0	+	0	+	0	= 0
0 1 1	3	0	+	0	+	0	= 0
1 0 0	4	0	+	1	+	0	= 1
1 0 1	5	0	+	0	+	0	= 0
1 1 0	6	0	+	0	+	0	= 0
1 1 1	7	0	+	0	+	1	= 1

Minterm Function Example

✓ $F(A, B, C, D, E) = m_2 + m_9 + m_{17} + m_{23}$

✓ $F(A, B, C, D, E) =$

$$A'B'C'DE' + A'BC'D'E + AB'C'D'E + AB'CDE$$

Maxterm Function Example

✓ Example: Implement F1 in maxterms:

$$F_1 = M_0 \cdot M_2 \cdot M_3 \cdot M_5 \cdot M_6$$

$$F_1 = (x + y + z) \cdot (x + \bar{y} + z) \cdot (x + \bar{y} + \bar{z}) \\ \cdot (\bar{x} + y + \bar{z}) \cdot (\bar{x} + \bar{y} + z)$$

x y z	i	$M_0 \cdot M_2 \cdot M_3 \cdot M_5 \cdot M_6 = F_1$
0 0 0	0	$0 \cdot 1 \cdot 1 \cdot 1 \cdot 1 = 0$
0 0 1	1	$1 \cdot 1 \cdot 1 \cdot 1 \cdot 1 = 1$
0 1 0	2	$1 \cdot 0 \cdot 1 \cdot 1 \cdot 1 = 0$
0 1 1	3	$1 \cdot 1 \cdot 0 \cdot 1 \cdot 1 = 0$
1 0 0	4	$1 \cdot 1 \cdot 1 \cdot 1 \cdot 1 = 1$
1 0 1	5	$1 \cdot 1 \cdot 1 \cdot 0 \cdot 1 = 0$
1 1 0	6	$1 \cdot 1 \cdot 1 \cdot 1 \cdot 0 = 0$
1 1 1	7	$1 \cdot 1 \cdot 1 \cdot 1 \cdot 1 = 1$

Maxterm Function Example

✓ $F(A, B, C, D) = M_3 \cdot M_8 \cdot M_{11} \cdot M_{14}$

✓ $F(A, B, C, D) =$

$$F = (A + B + C' + D') (A' + B + C + D)$$

$$(A' + B + C' + D') (A' + B' + C' + D)$$

Canonical Sum of Minterms

- ✓ Any Boolean function can be expressed as a **Sum of Minterms**.
 - For the function table, the minterms used are the terms corresponding to the 1's
 - For expressions, expand all terms first to explicitly list all minterms. Do this by "ANDing" any term missing a variable v with a term $(v + \bar{v})$.
- ✓ Example: Implement $f = x + \bar{x} \bar{y}$ as a sum of minterms.

First expand terms: $f = x(y + \bar{y}) + \bar{x} \bar{y}$

Then distribute terms: $f = xy + x\bar{y} + \bar{x}\bar{y}$

Express as sum of minterms: $f = m_3 + m_2 + m_0$

Another SOM Example

- ✓ Example: $F = A + \bar{B}C$
- ✓ There are three variables, A , B , and C which we take to be the standard order.
- ✓ Expanding the terms with missing variables:
- ✓ Collect terms (removing all but one of duplicate terms):
- ✓ Express as SOM:

$$\begin{aligned}F &= A(B + B')(C + C') + (A + A')B'C \\ &= ABC + ABC' + AB'C + AB'C' + AB'C + A'B'C \\ &= ABC + ABC' + AB'C + AB'C' + A'B'C \\ &= m_7 + m_6 + m_5 + m_4 + m_1 = m_1 + m_4 + m_5 + m_6 + m_7\end{aligned}$$

Shorthand SOM Form

- ✓ From the previous example, we started with:

$$F = A + \bar{B}C$$

- ✓ We ended up with:

$$F = m_1 + m_4 + m_5 + m_6 + m_7$$

- ✓ This can be denoted in the formal shorthand:

$$F(A, B, C) = \sum_m (1, 4, 5, 6, 7)$$

- ✓ Note that we explicitly show the standard variables in order and drop the "m" designators.

Canonical Product of Maxterms

✓ Any Boolean Function can be expressed as a **Product of Maxterms (POM)**.

- For the function table, the maxterms used are the terms corresponding to the 0's.
- For an expression, expand all terms first to explicitly list all maxterms. Do this by first applying the second distributive law, "ORing" terms missing variable v with a term equal to $v \cdot \bar{v}$ and then applying the distributive law again.

✓ Example: Convert to product of maxterms:

$$f(x, y, z) = x + \bar{x} \bar{y}$$

Apply the distributive law:

$$x + \bar{x} \bar{y} = (x + \bar{x})(x + \bar{y}) = 1 \cdot (x + \bar{y}) = x + \bar{y}$$

Add missing variable z :

$$x + \bar{y} + z \cdot \bar{z} = (x + \bar{y} + z)(x + \bar{y} + \bar{z})$$

Express as POM: $f = M_2 \cdot M_3$

Function Complements

- ✓ The complement of a function expressed as a sum of minterms is constructed by selecting the minterms missing in the sum-of-minterms canonical forms.
- ✓ Alternatively, the complement of a function expressed by a Sum of Minterms form is simply the Product of Maxterms with the same indices.
- ✓ Example: Given $F(x, y, z) = \sum_m (1, 3, 5, 7)$
 $\bar{F}(x, y, z) = \sum_m (0, 2, 4, 6)$
 $\bar{F}(x, y, z) = \prod_M (1, 3, 5, 7)$
- ✓ So, to convert between sum-of-minterms and product-of-maxterms form (or vice-versa) we follow one of these steps:
 - Find the function complement by swapping terms in the list with terms not in the list.
 - Change from SOM to POM

Standard Forms

- ✓ **Standard Sum-of-Products (SOP) form:** equations are written as an OR of AND terms
- ✓ **Standard Product-of-Sums (POS) form:** equations are written as an AND of OR terms
- ✓ **Examples:**
 - SOP: $A B C + \overline{A} \overline{B} C + B$
 - POS: $(A + B) \cdot (A + \overline{B} + \overline{C}) \cdot C$
- ✓ These "mixed" forms are **neither SOP nor POS**
 - $(A B + C) (A + C)$
 - $A B \overline{C} + A C (A + B)$

Standard Sum-of-Products (SOP)

- ✓ A sum of minterms form for n variables can be written down directly from a truth table.
 - Implementation of this form is a two-level network of gates such that:
 - The first level consists of n -input AND gates, and
 - The second level is a single OR gate (with fewer than 2^n inputs).
- ✓ This form often can be simplified so that the corresponding circuit is simpler.

Standard Sum-of-Products (SOP)

- ✓ A Simplification Example:

$$F(A, B, C) = \sum_m (1, 4, 5, 6, 7)$$

- ✓ Writing the minterm expression:

$$F = \overline{A} \overline{B} C + A \overline{B} \overline{C} + A \overline{B} C + A B \overline{C} + A B C$$

- ✓ Simplifying:

$$F = A' B' C + A (B' C' + B C' + B' C + B C)$$

$$= A' B' C + A (B' + B) (C' + C)$$

$$= A' B' C + A \cdot 1 \cdot 1$$



$$= A' B' C + A$$

$$= B' C + A$$

- ✓ Simplified F contains 3 literals compared to 15 in minterm F

AND/OR Two-level Implementation of SOP Expression

  - ✓ The two implementations for F are shown below - it is quite apparent which is simpler!



SOP and POS observations

- ✓ The previous examples show that:
 - Canonical Forms (Sum-of-minterms, Product-of-Maxterms), or other standard forms (SOP, POS) differ in complexity
 - Boolean algebra can be used to manipulate equations into simpler forms.
 - Simpler equations lead to simpler two-level implementations
- ✓ Questions:
 - How can we attain a "simplest" expression?
 - Is there only one minimum cost circuit?
 - The next part will deal with these issues.