

Circuit Optimization

- ✓ Goal: To obtain the simplest implementation for a given function
- ✓ Optimization is a more formal approach to simplification that is performed using a specific procedure or algorithm
- ✓ Optimization requires a cost criterion to measure the simplicity of a circuit
- ✓ Distinct cost criteria we will use:
 - Literal cost (L)
 - Gate input cost (G)
 - Gate input cost with NOTs (GN)

Literal Cost


- ✓ Literal - a variable or its complement
- ✓ Literal cost - the number of literal appearances in a Boolean expression corresponding to the logic circuit diagram
- ✓ Example, which solution is best?
 - $F = BD + \overline{A}\overline{B}C + A\overline{C}\overline{D}$ $L = 8$
 - $F = BD + \overline{A}\overline{B}C + \overline{A}B\overline{D} + ABC\overline{D}$ $L = 11$
 - $F = (A + B)(A + D)(B + C + \overline{D})(\overline{B} + \overline{C} + D)$ $L = 10$

Gate Input Cost

- ✓ Gate input costs - the number of inputs to the gates in the implementation corresponding exactly to the given equation or equations. (G - inverters not counted, GN - inverters counted)
- ✓ For SOP and POS equations, it can be found from the equation(s) by finding the sum of:
 - all literal appearances
 - the number of terms excluding single literal terms, (G) and
 - optionally, the number of distinct complemented single literals (GN).
- ✓ Example, which solution is best?
 - $F = BD + A\bar{B}C + A\bar{C}\bar{D}$ $G = 11, GN = 14$
 - $F = BD + A\bar{B}C + A\bar{B}\bar{D} + ABC\bar{C}$ $G = 15, GN = 18$
 - $F = (A + \bar{B})(A + D)(B + C + \bar{D})(\bar{B} + \bar{C} + D)$ $G = 14, GN = 17$

Cost Criteria (continued)

 
✓ Example 1: $\nabla \nabla GN = G + 2 = 9$
 ✓ $F = \overset{\bullet}{A} + \overset{\bullet}{B} \overset{\bullet}{C} + \overset{\bullet}{\bar{B}} \overset{\bullet}{\bar{C}}$ $L = 5$
 $G = L + 2 = 7$



- L (literal count) counts the AND inputs and the single literal OR input.
- G (gate input count) adds the remaining OR gate inputs
- ▼ GN (gate input count with NOTs) adds the inverter inputs

Cost Criteria (continued)

 - ✓ Example 2:
- ✓ $F = A B C + \bar{A} \bar{B} \bar{C}$
- ✓ $L = 6 \quad G = 8 \quad GN = 11$
- ✓ $F = (A + \bar{C})(\bar{B} + C)(\bar{A} + B)$
- ✓ $L = 6 \quad G = 9 \quad GN = 12$
- ✓ Same function and same literal cost
- ✓ But first circuit has better gate input count and better gate input count with NOTs



Boolean Function Optimization

- ✓ Minimizing the gate input (or literal) cost of a (a set of) Boolean equation(s) reduces circuit cost.
- ✓ **We choose gate input cost.**
- ✓ Boolean Algebra and graphical techniques are tools to minimize cost criteria values.
- ✓ Some important questions:
 - When do we stop trying to reduce the cost?
 - Do we know when we have a minimum cost?
- ✓ Treat optimum or near-optimum cost functions for two-level (SOP and POS) circuits first.
- ✓ Introduce a graphical technique using Karnaugh maps (K-maps, for short)

Karnaugh Maps (K-map)

- ✓ A K-map is a collection of squares
 - Each square represents a minterm
 - The collection of squares is a graphical representation of a Boolean function
 - Adjacent squares differ in the value of one variable
 - Alternative algebraic expressions for the same function are derived by recognizing patterns of squares (corresponding to cubes)
- ✓ The K-map can be viewed as
 - A reorganized version of the truth table or a particular cube representation


Some Uses of K-Maps

- ✓ Provide a means for:
 - Finding **optimum**
 - SOP and POS standard forms, and
 - two-level AND/OR and OR/AND circuit implementations
- for **functions with small numbers of variables**
- Visualizing concepts related to manipulating Boolean expressions
- Demonstrating concepts used by computer-aided design programs to simplify large circuits


The Boolean Space B^n

- ✓ $B = \{0, 1\}$
- ✓ $B^2 = \{0, 1\} \times \{0, 1\} = \{00, 01, 10, 11\}$

Karnaugh Maps:

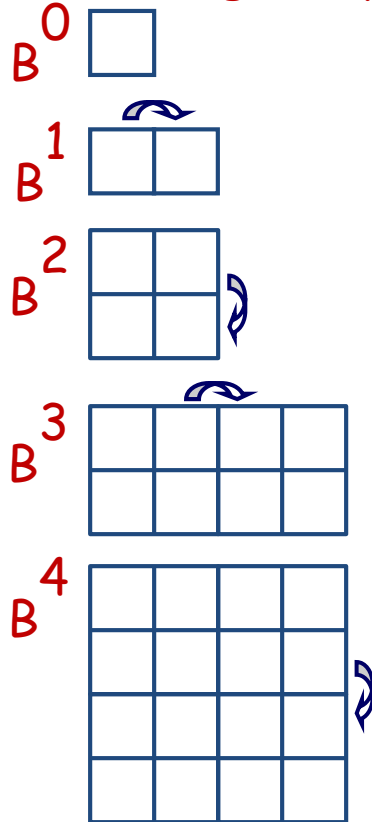

Boolean Cubes:

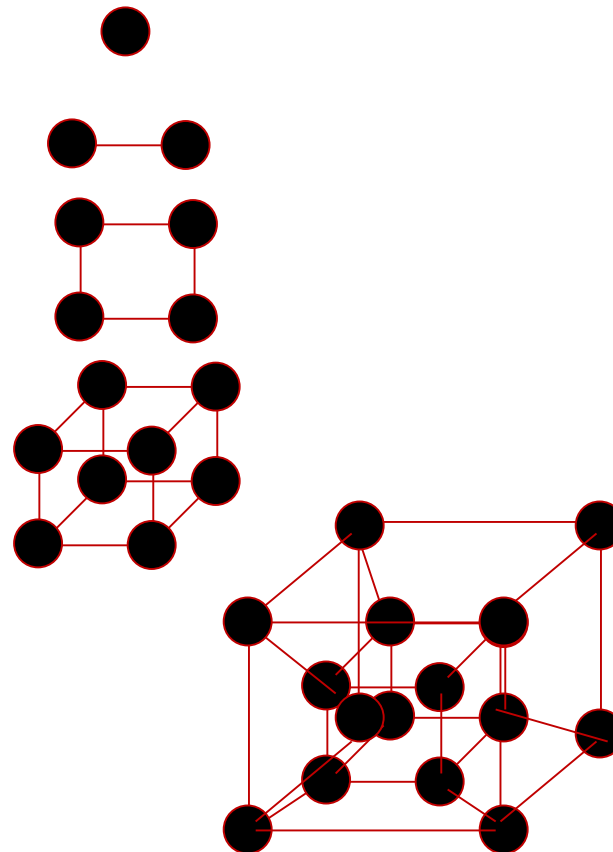

Two Variable Maps

✓ A 2-variable Karnaugh Map:

- Note that minterm m_0 and minterm m_1 are "adjacent" and differ in the value of the variable y
- Similarly, minterm m_0 and minterm m_2 differ in the x variable.
- Also, m_1 and m_3 differ in the x variable as well.
- Finally, m_2 and m_3 differ in the value of the variable y

$x \backslash y$	$y = 0$	$y = 1$
$x = 0$	$m_0 = \bar{x}\bar{y}$	$m_1 = \bar{x}y$
$x = 1$	$m_2 = x\bar{y}$	$m_3 = xy$

K-Map and Truth Tables

- ✓ The K-Map is just a different form of the truth table.
- ✓ Example - Two variable function:
 - We choose a,b,c and d from the set {0,1} to implement a particular function, $F(x,y)$.

Function Table

Input Values (x,y)	Function Value $F(x,y)$
0 0	a
0 1	b
1 0	c
1 1	d

K-Map

x \ y	y = 0	y = 1
x = 0	a	b
x = 1	c	d

K-Map Function Representation

- ✓ Example: $F(x,y) = x$

$F = x$	$y = 0$	$y = 1$
$x = 0$	0	0
$x = 1$	1	1

- ✓ For function $F(x,y)$, the two adjacent cells containing 1's can be combined using the Minimization Theorem:

$$F(x,y) = x\bar{y} + xy = x$$

K-Map Function Representation

✓ Example: $G(x,y) = \bar{x}y + x\bar{y} + xy$

$G=x+y$	$y = 0$	$y = 1$
$x = 0$	0	1
$x = 1$	1	1

✓ For $G(x,y)$, two pairs of adjacent cells containing 1's can be combined using the Minimization Theorem:

$$G(x,y) = (x\bar{y} + xy) + (\bar{x}y + xy) = x + y$$

Duplicate xy

Three Variable Maps

- ✓ A three-variable K-map:

$x \backslash yz$	$yz=00$	$yz=01$	$yz=11$	$yz=10$
$x=0$	m0	m1	m3	m2
$x=1$	m4	m5	m7	m6



- ✓ Where each minterm corresponds to the product terms:

$x \backslash yz$	$yz=00$	$yz=01$	$yz=11$	$yz=10$
$x=0$	$\bar{x} \bar{y} \bar{z}$	$\bar{x} \bar{y} z$	$\bar{x} y z$	$\bar{x} y \bar{z}$
$x=1$	$x \bar{y} \bar{z}$	$x \bar{y} z$	$x y z$	$x y \bar{z}$

- ✓ Note that if the binary value for an **index differs in one bit position**, the minterms are adjacent on the K-Map

Alternative Map Labeling

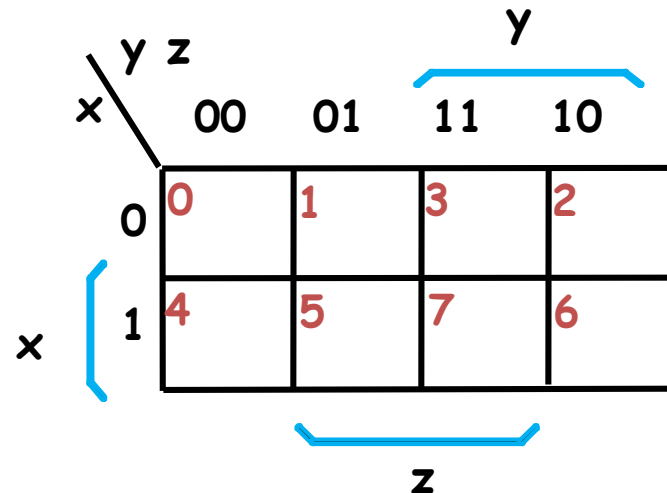 - ✓ Map use largely involves:
 - Entering values into the map, and
 - Reading off product terms from the map.
- ✓ Alternate labelings are useful:



Example Functions

- ✓ By convention, we represent the minterms of F by a "1" in the map and leave the minterms of blank \bar{F}

- ✓ Example:

$$F(x, y, z) = \sum_m (2, 3, 4, 5)$$

	y z			
			y	
x	0	1	3	2
			1	1
x	4	5	7	6
	1	1		

- ✓ Example:

- ✓ $F(x, y, z) = \sum_m (3, 4, 6, 7)$

- ✓ Learn the locations of the 8 indices based on the **variable order** shown (x, most significant and z, least significant) on the map boundaries


	y z			
			z	
x	0	1	3	2
			1	
x	4	5	7	6
	1		1	1
			z	

Combining Squares

- ✓ By combining squares, we reduce number of literals in a product term, reducing the literal cost, thereby reducing the other two cost criteria
- ✓ On a 3-variable K-Map:
 - One square represents a minterm with three variables
 - Two adjacent squares represent a cube that is product term with two variables
 - Four "adjacent" terms represent a cube that is product term with one variable
 - Eight "adjacent" terms is the function of all ones (no variables) is a tautology $f^1=1$.

 Example: Combining Squares

- ✓ Example: Let
- ✓ $F(x, y, z) = \sum_m (2, 3, 6, 7)$



- ✓ Applying the Minimization Theorem three times:

$$\begin{aligned}
 F(x, y, z) &= \bar{x} y z + x y z + \bar{x} y \bar{z} + x y \bar{z} \\
 &= yz + y\bar{z} \\
 &= y
 \end{aligned}$$



- ✓ Thus the four terms that form a 2×2 square correspond to the term "y".

Three-Variable Maps

- ✓ Reduced literal product terms for SOP standard forms correspond to cubes i.e. to **rectangles** on the K-maps containing cell counts that are powers of 2.
- ✓ Rectangles of 2 cells represent 2 adjacent minterms; of 4 cells represent 4 minterms that form a "pairwise adjacent" ring.
- ✓ Rectangles can contain non-adjacent cells as illustrated by the "**pairwise adjacent**" ring above.


Three-Variable Maps

 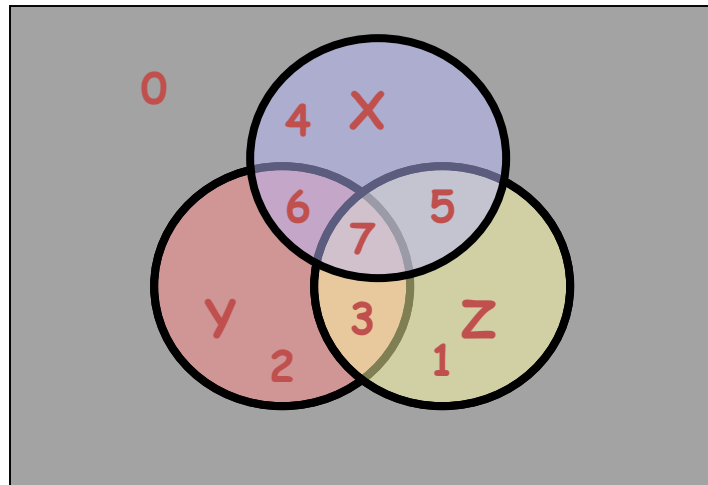- ✓ Topological warps of 3-variable K-maps that show *all* adjacencies:
 - Venn Diagram
 - Cylinder



Three-Variable Maps

- ✓ Example Shapes of 2-cell Rectangles:

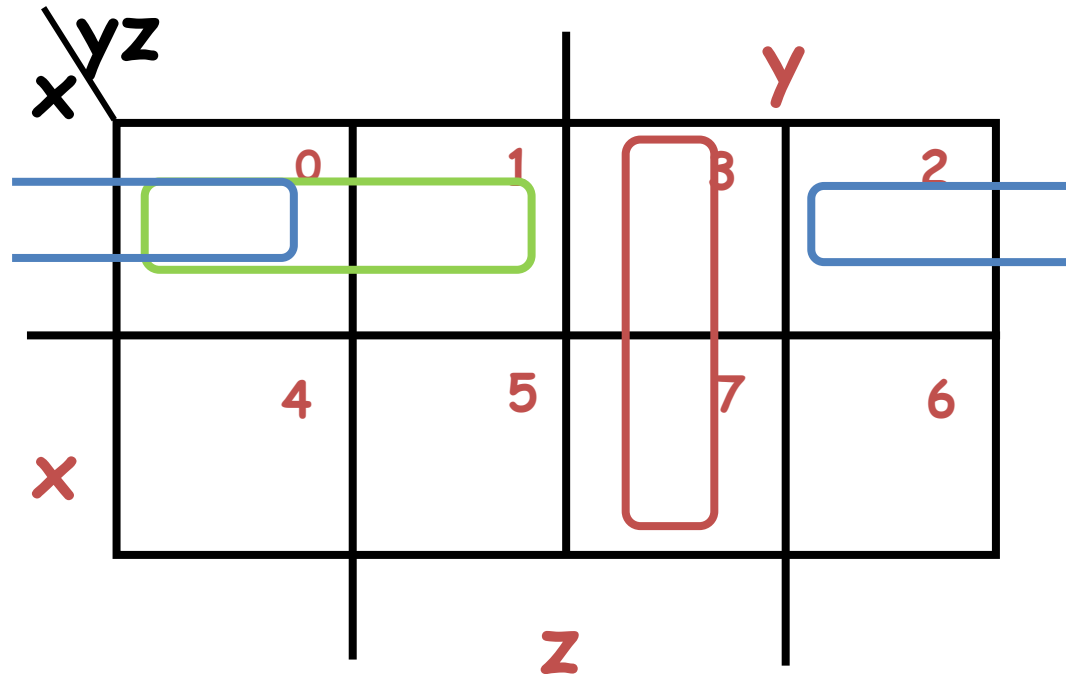


- ✓ Read off the product terms for the rectangles shown

$x'z'$ $x'y'$ yz

Three-Variable Maps

- ✓ Example Shapes of 4-cell Rectangles:

 


- ✓ Read off the product terms for the rectangles shown

z' z x' y'

Three Variable Maps

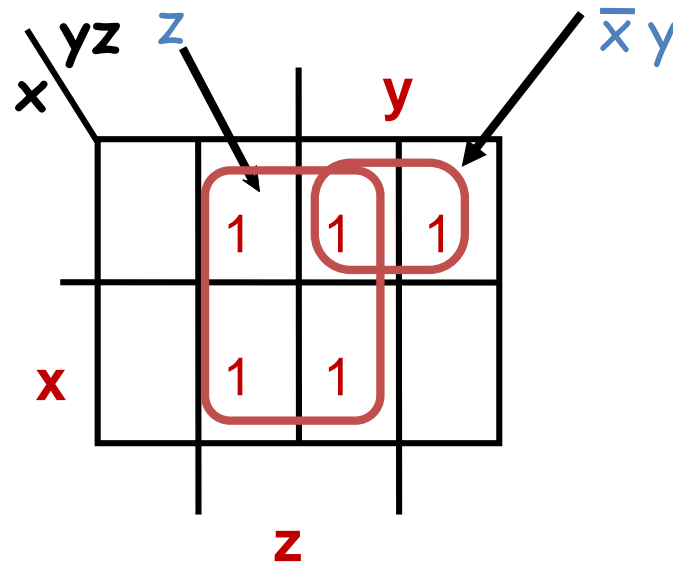- ✓ K-Maps can be used to simplify Boolean functions by a systematic methods. Terms are selected to cover the "1s" in the map.
- ✓ Example: Simplify $F(x, y, z) = \sum_m(1, 2, 3, 5, 7)$



$$F(x, y, z) = z + \bar{x}y$$

Three-Variable Map Simplification

- ✓ Use a K-map to find an optimum SOP equation for

$$F(x, y, z) = \sum_m (0, 1, 2, 4, 6, 7)$$

$$F = \bar{z} + \bar{x}\bar{y} + xy$$

	yz		
x	1	1	1
			y
x	1		1
			z

Four Variable Maps

- ✓ Map and location of minterms:

$wx \backslash yz$	$yz=00$	$yz=01$	$yz=11$	$yz=10$
$wx=00$	0	1	3	2
$wx=01$	4	5	7	6
$wx=11$	12	13	15	14
$wx=10$	8	9	11	10

W

Z


X

Four Variable Terms

- ✓ Four variable maps can have rectangles corresponding to:
 - A single 1 = 4 variables, (i.e. Minterm)
 - Two 1s = 3 variables,
 - Four 1s = 2 variables
 - Eight 1s = 1 variable,
 - Sixteen 1s = zero variables (i.e. Constant "1")


Four-Variable Maps

- ✓ Example Shapes of Rectangles:

 


Four-Variable Maps

- ✓ Example Shapes of Rectangles:

 

Four-Variable Map Simplification

 
$$F(W, X, Y, Z) = \sum_m (0, 2, 4, 5, 6, 7, 8, 10, 13, 15)$$



$$F = XZ + X'Z' + W'X$$

Four-Variable Map Simplification
 
$$F(W, X, Y, Z) = \sum_m(3, 4, 5, 7, 9, 13, 14, 15)$$




$$F = W' X Y' + W' Y Z + W X Y + W Y' Z$$

Systematic Simplification

- ✓ A **Prime Implicant** is a cube i.e. a product term obtained by combining the **maximum possible number of adjacent squares** in the map into a rectangle with the number of squares a power of 2.
- ✓ A prime implicant is called an **Essential Prime Implicant** if it is the **only** prime implicant that covers (includes) **one or more minterms**.
- ✓ Prime Implicants and Essential Prime Implicants can be determined by inspection of a K-Map.
- ✓ A set of prime implicants "***covers all minterms***" if, for each **minterm** of the function, at least one **prime implicant** in the set of prime implicants includes the minterm.

Example of Prime


✓ Find ALL Prime Implicants

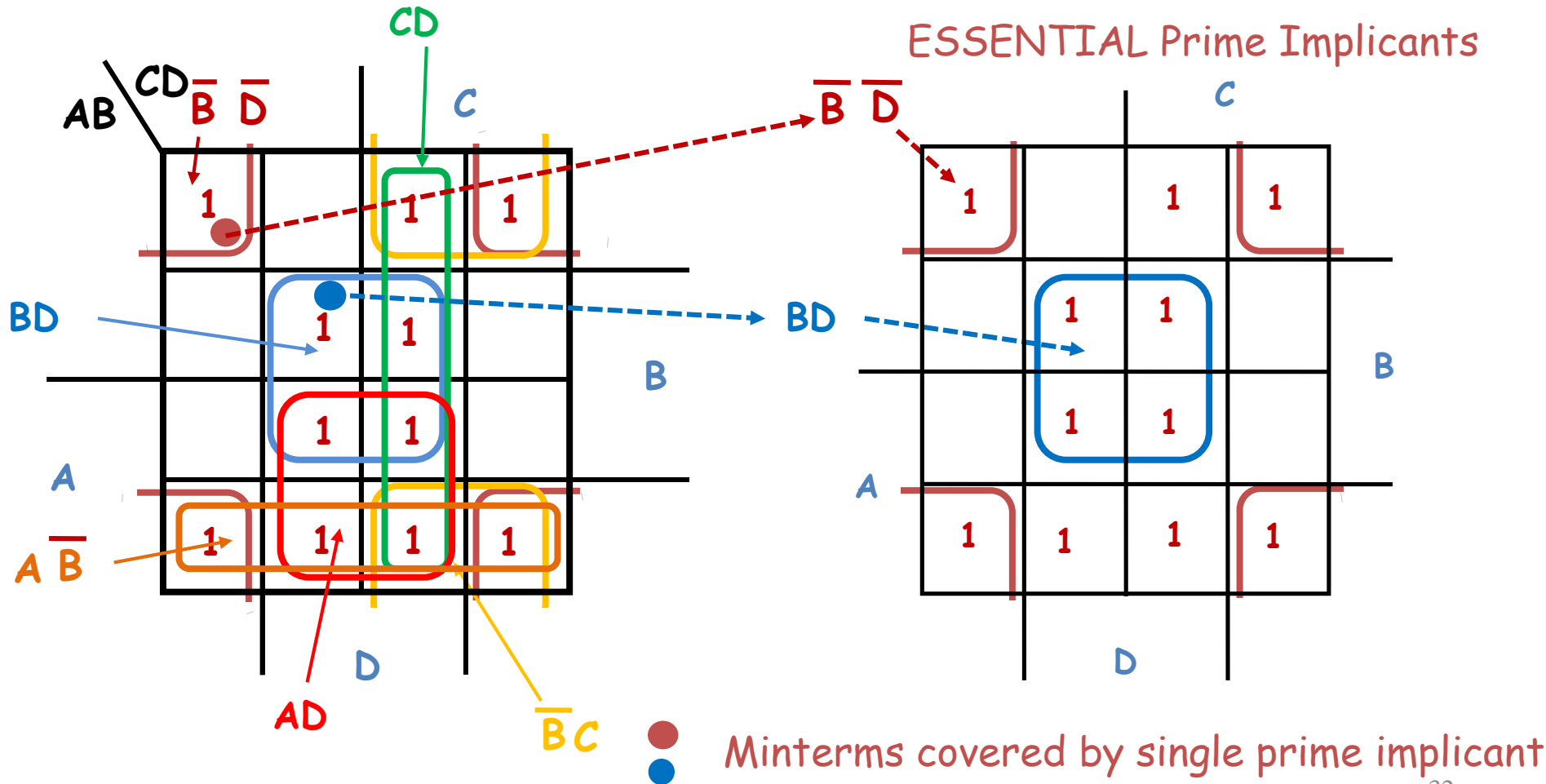

Prime Implicant Practice

✓ Find all prime implicants for:

 ✓ $F(A, B, C, D) = \sum_m (0, 2, 3, 8, 9, 10, 11, 12, 13, 14, 15)$




Prime implicants are: A , $\overline{B}C$, and $\overline{B}\overline{D}$

Another Example

✓ Find all prime implicants for:
 
$$F(A, B, C, D) = \sum_m (0, 2, 3, 4, 7, 12, 13, 14, 15)$$




$$AB, B\bar{C}\bar{D}, \bar{A}\bar{C}\bar{D}, \bar{A}B\bar{D}, \bar{A}\bar{B}C, \bar{A}C\bar{D}, BCD$$

$$\sum_m = AB + \bar{A}\bar{C}\bar{D} + \bar{A}C\bar{D} + \bar{A}\bar{B}C \quad \sum_c = \sum_m + \bar{A}B\bar{D} + BCD + B\bar{C}\bar{D} \quad 34$$

K-Maps, implicates

✓ Find all prime implicants for:
 
$$F = (w+y+z) (w'+x'+y) (x+y) (w+x+y') (w+x'+z) (w'+x+z)$$




$$\Pi_m = (w+x)(w'+y)(w+z)(x+z)$$

$$\Pi_c = \Pi_m (y+z)$$

K-Maps, implicates

✓ Find all prime implicates for:

 
$$F = (w+y+z)(w+x'+y)(w+y'+z')(x+y'+z)(w'+x'+z')(w'+x+y)(x+y'+z')$$



$$\begin{aligned} \Pi_m &= (x'+z') (y'+z') (w'+x) (x+z) (w+x'+y) \\ \Pi_c &= \Pi_m (w'+z') (w+y+z) (x+y') \end{aligned}$$

Five Variable or More K-Maps

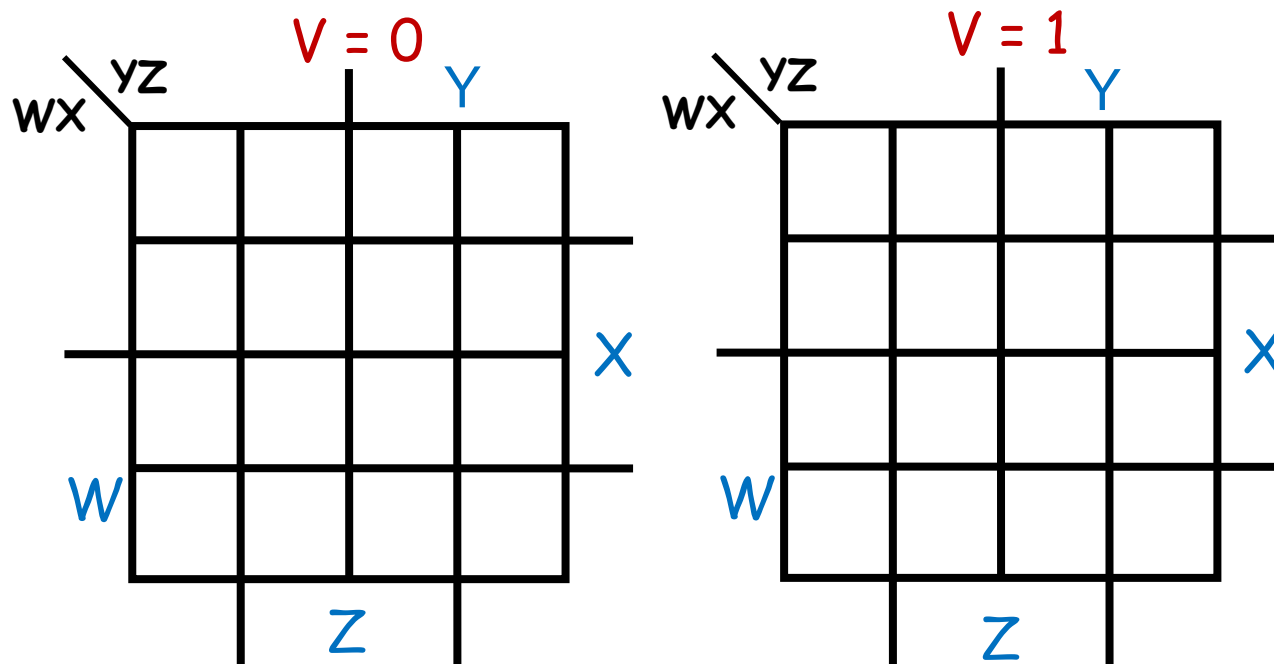
- ✓ For five variable problems, we use **two adjacent K-maps**. It becomes harder to visualize adjacent minterms for selecting PIs. You can extend the problem to six variables by using four K-Maps.



Five Variable K-Maps

- ✓ Find all prime implicants for:
 
$$G(v,w,x,y,z) = \sum_m(0,1,2,4,5,6,7,8,10,16,17,18,20, 21,24,25,26,27,29)$$



$$\sum_m = w'y' + x'z' + v'w'x + vy'z + vwx'$$

$$\sum_c = \sum_m + v'w'z'$$

Don't Cares in K-Maps

- ✓ Sometimes a function table or map contains entries for which it is known that:
 - the input values for the minterm will **never occur** or
 - the output value for the minterm is **not used**
- ✓ In these cases, the output value **need not be defined**
- ✓ Instead, the output value is defined as a **don't care**
- ✓ By placing "don't cares" (an "**x**" entry) in the function table or map, **the cost of the logic circuit may be lowered.**
- ✓ Example: A logic function having the binary codes for the BCD digits as its inputs. Only the codes for 0 through 9 are used. The six codes, 1010 through 1111 **never occur**, so the output values for these codes are **x** to represent "don't cares."

Incompletely Specified Functions

✓ $F = (f, d, r) : B^n \rightarrow \{0, 1, \mathbf{x}\}$

where \mathbf{x} represents "don't care".

- f = onset function - $f(x)=1 \leftrightarrow F(x)=1$
- r = offset function - $r(x)=1 \leftrightarrow F(x)=0$
- d = don't care function - $d(x)=1 \leftrightarrow F(x)=*$

(f, d, r) forms a partition of B^n . i.e.

- $f + d + r = B^n$
- $fd = fr = dr = \emptyset$ (pairwise disjoint)

Example: Logic Minimization

- ✓ Consider $F(a,b,c) = (f,d,r)$, where $f = \{\bar{a}b\bar{c}, \bar{a}bc, abc\}$ and $d = \{\bar{a}b\bar{c}, abc\}$, and the sequence of covers illustrated below:

- On
- Off
- Don't care

$$F^1 = \bar{a}b\bar{c} + \bar{a}bc + abc$$

Expand $abc \rightarrow a$



$$F^2 = a + \bar{a}b\bar{c} + \bar{a}bc$$

$\bar{a}bc$ is redundant


a is prime

$$F^3 = a + \bar{a}b\bar{c}$$

Expand $\bar{a}b\bar{c} \rightarrow b\bar{c}$




$$F^4 = a + b\bar{c}$$

 

 Example: BCD "5 or More"

- ✓ In the map below gives a function $F1(w,x,y,z)$ which is defined as "5 or more" over BCD inputs. With the don't cares used for the 6 non-BCD combinations:



$$F1(w, x, y, z) = \bar{w} x z + \bar{w} x y + w \bar{x} \bar{y}$$

$$F2(w, x, y, z) = w + xz + xy$$

$$G = 7$$

This is much lower in cost than $F1$ where the "don't cares" were treated as "0s" having $G = 12$

For this particular function, cost G for the POS solution for $F1(w,x,y,z)$ is not changed by using the don't cares.


$$F3(w, x, y, z) = (w + x)(w + y + z) \quad G = 7$$

Product of Sums Example


- ✓ Find the optimum POS solution:

$$F(A,B,C,D) = \sum_m(3,9,11,12,13,14,15) + \sum_d(1,4,6)$$

 - Hint: Use F' and complement it to get the result.



$$F = AB + B'D$$

 


$$F' = B'D' + A'B$$

$$F = (B + D)(A + B')$$


Selection Rule Example

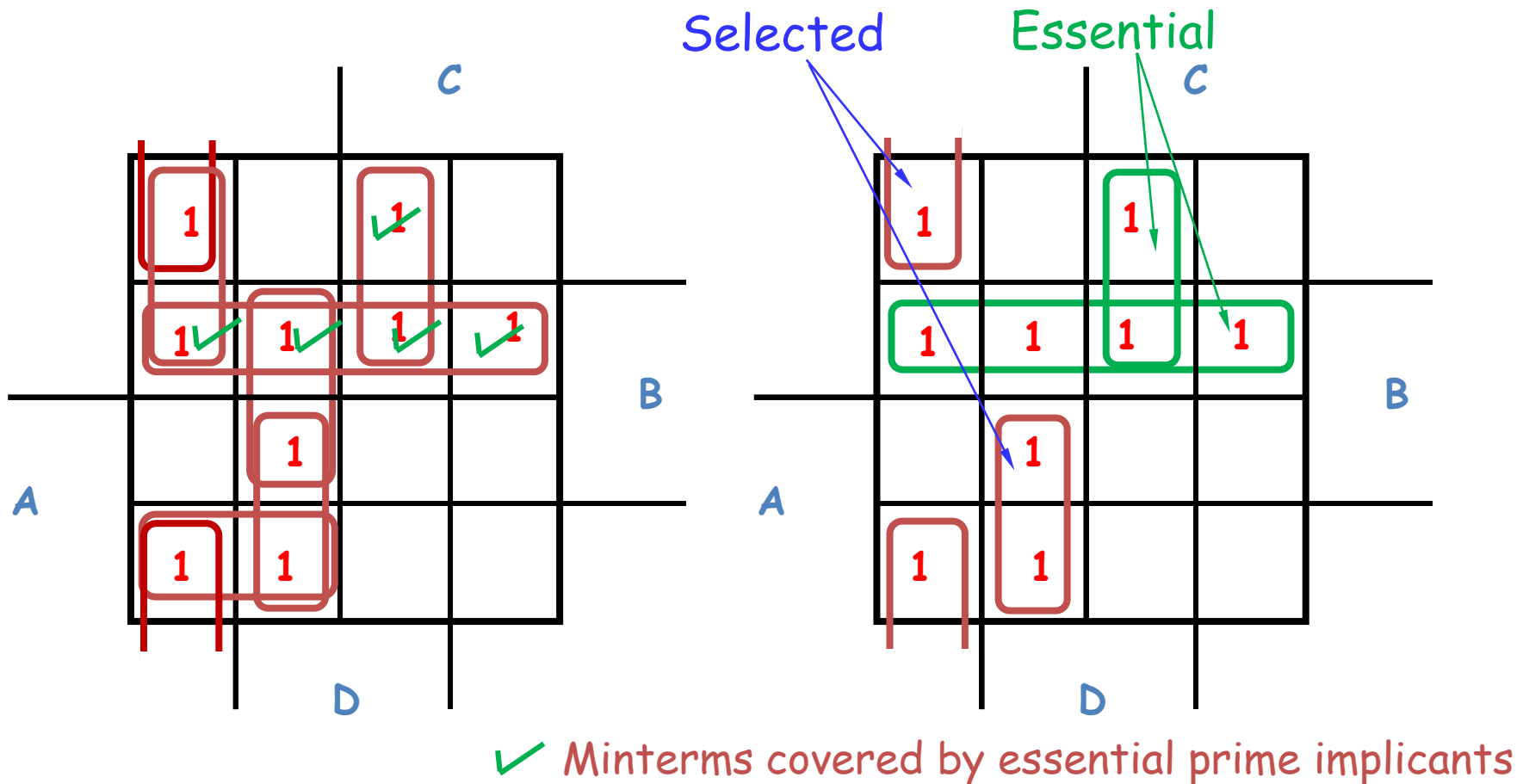- ✓ Simplify $F(A, B, C, D)$ given on the K-map.




Selection Rule Example with Don't Cares

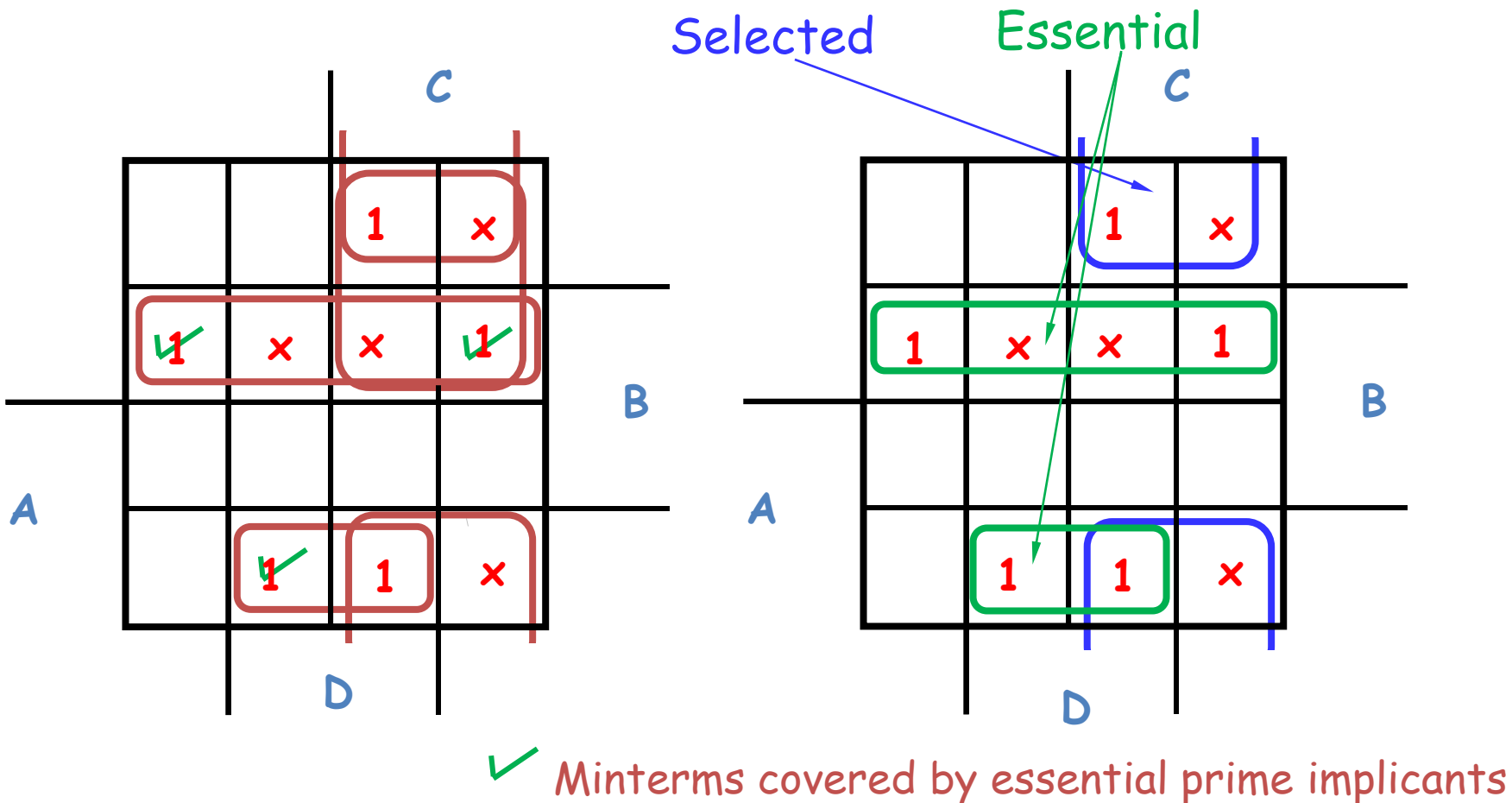- ✓ Simplify $F(A, B, C, D)$ given on the K-map.



Combinational Circuits

 - ✓ A combinational logic circuit has:
 - A set of m Boolean inputs,
 - A set of n Boolean outputs, and
 - n switching functions, each mapping the 2^m input combinations to an output such that the current output depends only on the current input values



Design Procedure

1. Specification

- Write a specification for the circuit

2. Formulation

- Derive a truth table or initial Boolean equations that define the required relationships between the inputs and outputs

3. Optimization

- Apply 2-level and multiple-level optimization
- Draw a logic diagram for the resulting circuit using ANDs, ORs, and inverters

4. Technology Mapping

- Map the logic diagram to the implementation technology selected

5. Verification

- Verify the correctness of the final design


Design Example BCD to Excess-3 code converter

1. Specification

- BCD to Excess-3 code converter
 - Transforms BCD code for the decimal digits to Excess-3 code for the decimal digits
- BCD code words for digits 0 through 9
 - 4-bit patterns 0000 to 1001, respectively
- Excess-3 code words for digits 0 through 9
 - 4-bit patterns consisting of 3 (binary 0011) added to each BCD code word
- Implementation:
 - multiple-level circuit
 - NAND gates (including inverters)

Specification of BCD-to-Excess3

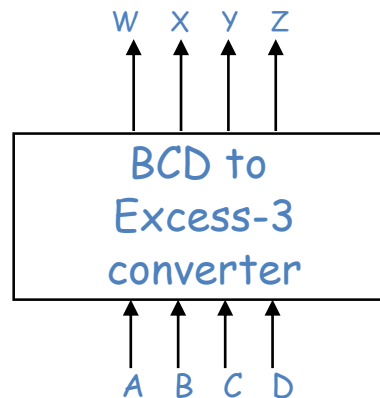- ✓ Inputs: a BCD input, A, B, C, D with A as the most significant bit and D as the least significant bit.
- ✓ Outputs: an Excess-3 output W, X, Y, Z that corresponds to the BCD input.
- ✓ Internal operation - circuit to do the conversion in combinational logic.



Formulation of BCD-to-Excess-3

- ✓ Excess-3 code is easily formed by adding a binary 3 to the binary or BCD for the digit.
- ✓ There are 16 possible inputs for both BCD and Excess-3.
- ✓ It can be assumed that only valid BCD inputs will appear so the six combinations not used can be treated as don't cares.

BCD-to-Excess-3 Code converter

Decimal Digit	Input BCD	Output Excess-3
0	0 0 0 0	0 0 1 1
1	0 0 0 1	0 1 0 0
2	0 0 1 0	0 1 0 1
3	0 0 1 1	0 1 1 0
4	0 1 0 0	0 1 1 1
5	0 1 0 1	1 0 0 0
6	0 1 1 0	1 0 0 1
7	0 1 1 1	1 0 1 0
8	1 0 0 0	1 0 1 1
9	1 0 0 1	1 1 0 0

Expressions for W X Y Z

✓ $W(A,B,C,D) = \Sigma m(5,6,7,8,9)$

+d(10,11,12,13,14,15)

✓ $X(A,B,C,D) = \Sigma m(1,2,3,4,9)$

+d(10,11,12,13,14,15)

✓ $Y(A,B,C,D) = \Sigma m(0,3,4,7,8)$

+d(10,11,12,13,14,15)

✓ $Z(A,B,C,D) = \Sigma m(0,2,4,6,8)$


+d(10,11,12,13,14,15)

Decimal Digit	Input BCD	Output Excess-3
0	0 0 0 0	0 0 1 1
1	0 0 0 1	0 1 0 0
2	0 0 1 0	0 1 0 1
3	0 0 1 1	0 1 1 0
4	0 1 0 0	0 1 1 1
5	0 1 0 1	1 0 0 0
6	0 1 1 0	1 0 0 1
7	0 1 1 1	1 0 1 0
8	1 0 0 0	1 0 1 1
9	1 0 0 1	1 1 0 0


Optimization - BCD-to-Excess-3

- ✓ Lay out K-maps for each output, W X Y Z

K-map for W $\Sigma_m(5,6,7,8,9)$

 

K-map for W

 


$$W = A + BC + BD$$


Optimization - BCD-to-Excess-3

- ✓ Lay out K-maps for each output, W X Y Z

K-map for X $\Sigma_m(1,2,3,4,9)$

 


K-map for X

 


$$X = BC'D' + B'C + B'D$$

Optimization - BCD-to-Excess-3

K-map for Y $\Sigma_m(0,3,4,7,8)$

 


K-map for Y

 


$$Y = C'D' + CD$$

Minimize K-Maps

K-map for Z $\Sigma_m(0,2,4,6,8)$

 

K-map for Z

 

$Z = D'$

Two level versus multi-level circuit implementation

✓ Have equations

- $W = A + BC + BD$
- $X = B'C + B'D + BC'D'$
- $Y = CD + C'D'$
- $Z = D'$

✓ Call $T = C + D$, then $T' = (C + D)' = C'D'$

- $W = A + BT$
- $X = B'T + BT'$
- $Y = CD + T'$
- $Z = D'$

Create the digital circuit

- ✓ Implementing the second set of equations where $T=C+D$ results in a lower gate count.
- ✓ This gate has a fanout of 3

