

Redundant States in Sequential Circuits


- ✓ Removal of redundant states is important because
 - Cost: the number of memory elements is directly related to the number of states
 - Complexity: the more states the circuit contains, the more complex the design and implementation becomes
 - Aids failure analysis: diagnostic routines are often predicated on the assumption that no redundant states exist

Equivalent States

- ✓ Let S_i and S_j be states of a **completely specified** sequential circuit. Let S_k and S_l be the next states of S_i and S_j , respectively for input I_p .

S_i and S_j are *equivalent* if and only if for every possible I_p the following conditions are satisfied:

 - the outputs produced by S_i and S_j are the same;
- the next states S_k and S_l are equivalent.



- States S_i and S_j are equivalent and are combined to one state by pointing all arrows that go to S_j to state S_i and removing S_j with its all arrows

Equivalence and Partitions

- ✓ **Equivalence relation:** let R be a relation on a set S . R is an equivalence relation on S if and only if it is reflexive, symmetric, and transitive.
- ✓ An equivalence relation on a set partitions the set into disjoint equivalence classes.
- ✓ A partition consists of one or more blocks, where each block comprises a subset of states that may be equivalent, but the states in a given block are definitely not equivalent to the states in the other blocks.
- ✓ The partitioning method initially assumes that all states are equivalent and then proceeds to determine those state which are not equivalent by analyzing each states k -successors.

Finding Equivalent States By Inspection

	<i>x</i>	
	0	1
<i>A</i>	<i>B</i> /0	<i>C</i> /1
<i>B</i>	<i>C</i> /0	<i>A</i> /1
<i>C</i>	<i>D</i> /1	<i>B</i> /0
<i>D</i>	<i>C</i> /0	<i>A</i> /1

(a)

	<i>x</i>	
	0	1
<i>A</i>	<i>B</i> /0	<i>C</i> /1
<i>B</i>	<i>C</i> /0	<i>A</i> /1
<i>C</i>	<i>B</i> /1	<i>B</i> /0

(b)

	<i>x</i>	
	0	1
<i>A</i>	<i>B</i> /0	<i>C</i> /1
<i>B</i>	<i>B</i> /0	<i>A</i> /1
<i>C</i>	<i>D</i> /1	<i>B</i> /0
<i>D</i>	<i>D</i> /0	<i>A</i> /1

(c)

	<i>x</i>	
	0	1
<i>A</i>	<i>B</i> /0	<i>C</i> /1
<i>B</i>	<i>D</i> /0	<i>A</i> /1
<i>C</i>	<i>D</i> /1	<i>B</i> /0
<i>D</i>	<i>B</i> /0	<i>A</i> /1

(e)

	<i>x</i>	
	0	1
<i>A</i>	<i>B</i> /0	<i>C</i> /1
<i>B</i>	<i>B</i> /0	<i>A</i> /1
<i>C</i>	<i>B</i> /1	<i>B</i> /0

(d)

Partitioning Minimization Procedure

✓ PROCEDURE:

- 1) all states belong to the initial partition p_1
- 2) p_1 is partitioned in blocks such that the states in each block generate the same output.
- 3) continue to perform new partitions by testing whether the k -successors of the states in each block are contained in one block. Those states whose k -successors are in different blocks cannot be in one block.
- 4) procedure ends when a new partition is the same as the previous partition

Finding Equivalent States by Partitioning

	Partition blocks	Action
Partition P_0	(ABCDE)	
Output for $x = 0$	11100	Separate (ABC) and (DE)
Output for $x = 1$	00011	Separate (ABC) and (DE)
Partition P_1	(ABC) (DE)	
Next state for $x = 0$	$\begin{array}{c c} CCB & DE \end{array}$	
Next state for $x = 1$	$\begin{array}{c c} BEE & BA \end{array}$	Separate (A) and (BC)
Partition P_2	(A) (BC) (DE)	
Next state for $x = 0$	$\begin{array}{c c c} C & CB & DE \end{array}$	
Next state for $x = 1$	$\begin{array}{c c c} B & EE & BA \end{array}$	Separate (D) and (E)
Partition P_3	(A) (BC) (D) (E)	
Next state for $x = 0$	$\begin{array}{c c c c} C & CB & D & E \end{array}$	
Next state for $x = 1$	$\begin{array}{c c c c} B & EE & B & A \end{array}$	
Partition $P_4 = P_3$	(A) (BC) (D) (E)	

States B and C are equivalent.


Implication Table

- ✓ The checking of each pair of states for possible equivalence in a table with a large number of states can be done systematically on an Implication Table.
- ✓ The Implication Table is a chart that consists of squares, one for every possible pair of states.

Present State	Next State		Output	
	X=0	X=1	X=0	X=1
<i>a</i>	<i>c</i>	<i>b</i>	0	1
<i>b</i>	<i>d</i>	<i>a</i>	0	1
<i>c</i>	<i>a</i>	<i>d</i>	1	0
<i>d</i>	<i>b</i>	<i>d</i>	1	0

$(c,d) \Leftrightarrow (a,b) \implies (c,d) \&\& (a,b)$

both pairs are equivalent

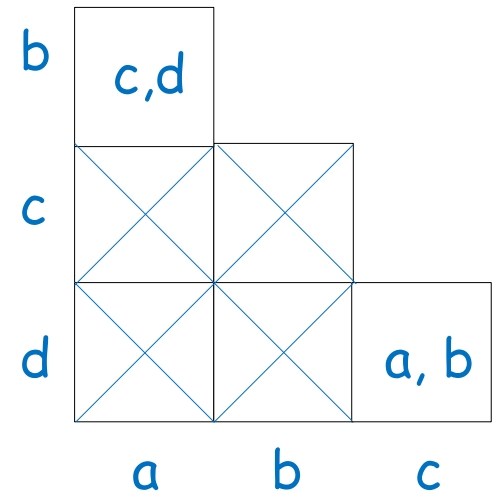


Implication Table

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
<i>a</i>	<i>d</i>	<i>b</i>	0	0
<i>b</i>	<i>e</i>	<i>a</i>	0	0
<i>c</i>	<i>g</i>	<i>f</i>	0	1
<i>d</i>	<i>a</i>	<i>d</i>	1	0
<i>e</i>	<i>a</i>	<i>d</i>	1	0
<i>f</i>	<i>c</i>	<i>b</i>	0	0
<i>g</i>	<i>a</i>	<i>e</i>	1	0


- the equivalent states
 - (a,b), (d,e), (d,g), (e,g)
- the reduced states
 - (a,b), (c), (d,e,g), (f)
- the state table:

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
<i>a</i>	<i>d</i>	<i>a</i>	0	0
<i>c</i>	<i>d</i>	<i>f</i>	0	1
<i>d</i>	<i>a</i>	<i>d</i>	1	0
<i>f</i>	<i>c</i>	<i>a</i>	0	0

 

Incompletely specified circuits

 - ✓ Finding compatible states by inspection



Merging of the Flow Table

- ✓ The state table may be incompletely specified: combinations of inputs or input sequences may never occur (Some next states and outputs are don't care).
- ✓ Multi-input **primitive flow tables** are always incompletely specified
 - Several synchronous circuits also have this property
- ✓ Incompletely specified states are not "equivalent" as in completely specified circuits. Instead, we are going to find **compatible** states

Equivalent and Compatible States

- ✓ **completely** specified state table \Rightarrow **equivalence**

If a and b are equivalent, and b and c are equivalent then also a and c are equivalent:

$$(a,b), (b, c) \Rightarrow (a, c)$$

- ✓ **uncompletely** specified state table \Rightarrow **compatibility**

If a and b are compatible, and b and c are compatible not necessarily a and c are compatible:

- ✓ **Compatibility relation:** let R be a relation on a set S . R is a compatibility relation on S if and only if it is **reflexive and symmetric**. A compatibility relation on a set partitions the set into compatibility classes. **They are typically not disjoint.**

y \	0	1
a	(A,0)	C,1
b	(B,-)	C,-
c	(C,1)	(C,1)


b	✓	
c	X	✓
	a	b

Incompletely specified circuits: partition method

- ✓ The partitioning minimization procedure which was applied to completely specified state tables can also be applied to incompletely specified state tables.
- ✓ To perform the partitioning process, we can assume that the unspecified outputs have a specific value.
- ✓ The partitioning method is equally applicable to Mealy type FSMs in the same way as for Moore-type FSMs.

Compatible Pairs (DG sequential circuit)

 - ✓ Implication tables are used to find compatible states.
 - We can adjust the dashes to fit any desired condition.
 - Must have no conflict in the output values to be merged.



	00	01	11	10
a	c,-	a ,0	b,-	-, -
b	-, -	a,-	b ,1	e,-
c	c ,0	a,-	-, -	d,-
d	c,-	-, -	b,-	d ,0
e	f,-	-, -	b,-	e ,1
f	f ,1	a,-	-, -	e,-

(a) Primitive flow table

The compatible pairs are :



b	✓				
c	✓	d, e X			
d	✓	d, e X	✓		
e	c, f X	✓	d, e X c, f X	X	
f	c, f X	✓	X	d, e X c, f X	✓
	a	b	c	d	e

(a, b)
(a, c)
(a, d)
(b, e)
(b, f)
(c, d)
(e, f)

 
 
(b) Implication table

Merger diagrams

- ✓ States are represented as dot in a circle
- ✓ Lines connect states couples compatible
- ✓ Maximal sets can be identified as those sets in which every states is connected to every other state by a line segment





Maximal sets with 3,4,5 and 6 states

  

Maximal Compatibles

- ✓ Maximal Compatibles: a group of compatibles that contains all the possible combinations of compatible states.
- ✓ n-state compatible \Rightarrow n-sided fully connected polygon.
 - All its diagonals connected.
 - Not all maximal compatibles are necessary
 - An isolated dot: a state that is not compatible to any other state

  - a line: a compatible pair
- a triangle: a compatible with three states
- an n-state compatible: an n-sided polygon with all its diagonals connected



Closed Covering Condition

- ✓ The condition that must be satisfied is that the set of chosen compatibles must:
 - **Cover all states.**
 - **Be closed:** the closure condition is satisfied if there are no implied states or if the implied states are included within a set
- ✓ In the example of the DG sequential circuit, the maximal compatibles are:
 $(a, b) (a, c, d), (b, e, f)$
- ✓ If we remove (a, b) , we get a set of two compatibles:
 $(a, c, d), (b, e, f)$:
 - All the six states are included in this set.
 - There are no implied states for $(a,c); (a,d);(c,d);(b,e);(b,f)$ and (e,f) [you can check the implication table]. The closure condition is satisfied

The original primitive flow table can be merged into two rows, one for each of the compatibles.

Closed Covering Condition (Example)


- From the aside implication table, we have the following compatible: pairs: (a, b) (a, d) (b, c) (c, d) (c, e) (d, e)
- From the merger diagram, we determine the maximal compatibles: (a, b) (a, d) (b, c) (c, d, e)
- If we choose the two compatibles: (a, b) (c, d, e)

Compatibles	(a, b)	(a, d)	(b, c)	(c, d, e)
Implied states	(b, c)	(b, c)	(d, e)	(a, d) (b, c)

Closure table

- All the 5 states are included in this set.
- The implied states for (a, b) are (b, c) . But (b, c) are not include in the chosen set. This set is not closed.
- A set of compatibles that will satisfy the closed covering condition is (a, d) (b, c) (c, d, e)
- Note that: the same state can be repeated more than once

b	$b, c \checkmark$			
c	\times	$d, e \checkmark$		
d	$b, c \checkmark$	\times	$a, d \checkmark$	
e	\times	\times	\checkmark	$b, c \checkmark$
	a	b	c	d

 

Minimization of compatible classes

Select a set of compatibility classes so that the following conditions are satisfied:

- ✓ **Completeness:** all states of the original machine must be covered
- ✓ **Consistency:** the chosen set of compatibility classes must be closed
- ✓ **Minimality:** the smallest number of compatibility classes is used

Bounding the number of states

- ✓ Unfortunately the process of selecting the set of compatibility classes that meets the three conditions **must be done by trial and error**.
- ✓ Let **U** be the **upper bound** on the number of states needed in the minimized circuit.

Then $U = \text{minimum}(\text{NSMC}, \text{NSOC})$

- where NSMC = the number of sets of maximal compatibles
- and NSOC = the number of states in the original circuit

- ✓ Let **L** be the **lower bound** on the number of states needed in the minimized circuit

Then $L = \text{maximum}(\text{NSMI}_1, \text{NSMI}_2, \dots, \text{NSMI}_i)$

- where NSMI_i = the number of states in the i^{th} group of the set of **maximal incompatibles** of the original circuit.

State Reduction Algorithm


- ✓ Step 1 -- find the maximal compatibles
- ✓ Step 2 -- find the maximal incompatibles
- ✓ Step 3 -- Find the upper and lower bounds on the number of states needed
- ✓ Step 4 -- Find a set of compatibility classes that is complete, consistent, and minimal
- ✓ Step 5 -- Produce the minimum state table

Example -- State reduction problem

	x	
	0	1
A	A/-	-/-
B	C/1	B/0
C	D/0	-/1
D	-/-	B/-
E	A/0	C/1


Compatibles pairs
 $(AB)(AC)(AD)(AE)(BD)(CD)(CE)$

Incompatibles pairs
 $(BC)(BE)(DE)$

 


Maximum
 Compatibles
 $(ABD)(ACD)(ACE)$

$U=3$

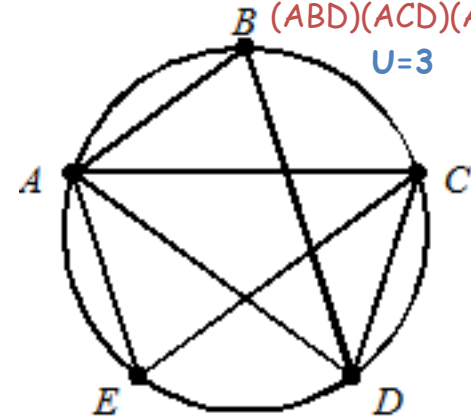

Maximum
 Incompatibles
 $(BE)(BC)(ED)$

$L=2$

 

	x	
	0	1
(ABD)	AC	B
(ACD)	AD	B
(ACE)	AD	C


Closure table

	x		
	0	1	
A'	B'/1	A'/0	$A' = (ABD)$
B'	A'/0	B'/1	$B' = (ACE)$


Reduced state table

Another state table reduction problem

	x	
	0	1
A	B/1	D/0
B	-/-	B/0
C	E/0	D/-
D	B/1	A/0
E	-/-	C/1
F	-/0	E/1

 

Compatibles pairs
(AB)(AD)(BC)(BD)

 


Closure table

	x	
	0	1
(ABD)	B	ABD
(C)	E	D
(E)	-	C
(F)	-	E

(d)

Maximum
Compatibles
(ABD)(C)(E)(F)
U=4

 Incompatibles pairs
(AC)(AE)(AF)(BE)(BF)(CD)(CE)(CF)(DE)(DF)(EF)



Maximum
Incompatibles
(ACEF)(CDEF)
(BEF)
L=4

	0	1
A'	A'/1	A'/0
B'	C'/0	A'/0
C'	-/-	B'/1
D'	-/0	C'/1




(f)
Reduced state table

Note that the resultant state table has considerable flexibility. This property will serve to simplify the hardware realization

	x			x	
	0	1		0	1
(ABD)	B	ABD	A'	A', B'/1	A'/0
(BC)	E	BD	B'	C'/0	A'/0
(E)	-	C	C'	-/-	B'/1
(F)	-	E	D'	-/0	C'/1

Yet another state reduction problem

	x	
	0	1
A	D/-	A/-
B	E/0	A/-
C	D/0	B/-
D	C/-	C/-
E	C/1	B/-

 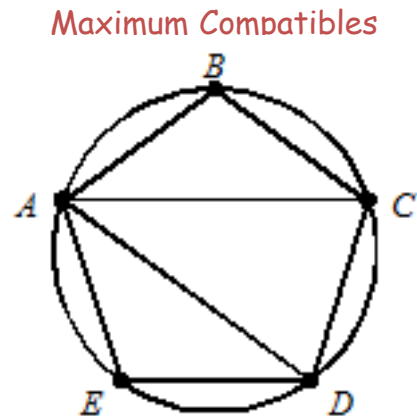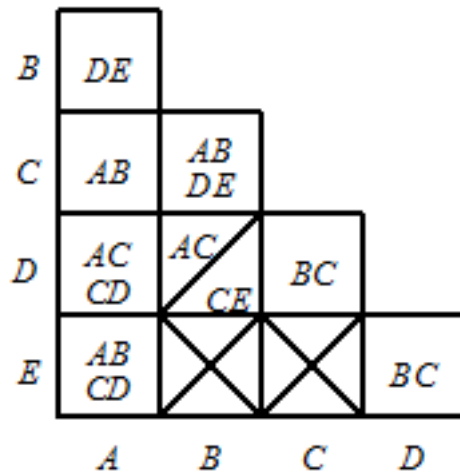

Maximum
Compatibles
(ABC)(ACD)(DE)
U=3

Maximum
Incompatibles
(BD)(BE)(CE)
L=2

	x	
	0	1
(ABC)	DE	AB
(ACD)	CD	ABC
(ADE)	CD	ABC

Closure table
Maximum
Compatible

	x	
	0	1
(ABC)	DE	AB
(DE)	C	BC


Closure table

	x	
	0	1
A'	B'/0	A'/-
B'	A'/1	A'/-

Reduced
state table


Generating Maximal Compatibles and Incompatibles

	x	
	0	1
A	A/-	C/1
B	B/-	A/-
C	G/-	E/0
D	C/1	C/-
E	A/1	C/-
F	D/-	A/-
G	G/-	G/-
H	H/-	D/-

 

Maximum Compatibles
 (AEGH)(BCG)(CDG)
 (CEG)(CFG)
U=5

B	AC							
C		BG AE						
D	AC	BC AC	CG CE					
E	√	AB AC	AG	AC				
F	AD AC	BD	DG AE	CD AC	AD AC			
G	CG	AG	EG	CG	AG CG	DG AG		
H	CD	AD	GH DE	CH CD	AH CD	DH AD	DG	
	A	B	C	D	E	F	G	

 

Maximum Incompatibles
 (ABDF)(AC)(BDEF)
 (CH)(BDFH)
L=4

Reduced state table

	x	
	0	1
A	A/-	C/1
B	B/-	A/-
C	G/-	E/0
D	C/1	C/-
E	A/1	C/-
F	D/-	A/-
G	G/-	G/-
H	H/-	D/-

- ✓ Closure table: treat maximum compatibles as states and find their sets of next states

	x			x	
	0	1		0	1
(AEGH)	AGH	CDG	A'	A'/1	C'/1
(BCG)	BG	AEG	B'	B'/-	A'/0
(CDG)	CG	CEG	C'	B', C', D', E'/1	D'/0
(CEG)	AG	CEG	D'	A'/1	D'/0
(CFG)	DG	AEG	E'	C'/-	A'/0

Closure table

Reduced state table

- ✓ All maximal compatibles are used as states of the reduced machine. Hence, the final five states are:

$$\begin{aligned}
 A' &= (AEGH), & D' &= (CEG) \\
 B' &= (BCG), & E' &= (CFG) \\
 C' &= (CDG)
 \end{aligned}$$

State Assignment

- ✓ Primary Objective of Synchronous Networks
 - Simplification of Logic and Improvement of Performance
 - Improvement of Testability
 - Minimization of Power Consumption.
- ✓ Primary Objective of Asynchronous Networks
 - Prevention of Critical Races
 - Simplification of Logic

Race-Free State Assignment


- ✓ Objective: choose a proper binary state assignment to **prevent critical races**
- ✓ Only **one variable can change** at any given time when a state transition occurs
- ✓ States between which transitions occur will be given **adjacent assignments**
 - Two binary values are said to be adjacent if they differ in only one variable
- ✓ To ensure that a transition table has no critical races, **every possible state transition should be checked**
 - A tedious work when the flow table is large
 - Only 3-row and 4-row examples are demonstrated

3-Row Flow-Table Example

- ✓ Three states require two binary variables (in the flow table outputs are omitted for simplicity)
- ✓ Representation by a **transition diagram**
- ✓ a and c are not adjacent in such an assignment!
 - **Impossible** to make all states adjacent if only 3 states are used

	$x_1 x_2$			
	00	01	11	10
a	a	b	c	a
b	a	b	b	c
c	a	c	c	c

(a) Flow table

 


(b) Transition diagram

3-Row Flow-Table Example

- ✓ A race-free assignment can be obtained if we **add an extra row** to the flow table
- ✓ Only provide a race-free transition between the stable states
- ✓ The transition from a to c must now go through d
 $00 \Rightarrow 10 \Rightarrow 11$ (no race condition)
- ✓ Note that **no stable state can be introduced in row d**

	x_1x_2			
	00	01	11	10
a	a	b	d	a
b	a	b	b	c
c	d	c	c	c
d	a	-	c	-

 

	x_1x_2			
	00	01	11	10
a = 00	00	01	10	00
b = 01	00	01	01	11
c = 11	10	11	11	11
d = 10	00	-	11	-

don't care but cannot be 10
(cannot stable)






Shared-Row Method

- ✓ The shared row is not assigned to any specific **stable state**
- ✓ Used to convert a critical race into a cycle that goes through adjacent transitions between two stable states
- ✓ May require more extra rows

State adjacencies for assignments

UNIQUE STATE ASSIGNMENTS

States	Assignments		
	1 y_1y_2	2 y_1y_2	3 y_1y_2
<i>A</i>	00	00	00
<i>B</i>	01	11	10
<i>C</i>	11	01	01
<i>D</i>	10	10	11

   

Unique State Assignments

Present state	x		Assignments		
	0	1	1	2	3
A	A/0	B/0	$y_1 y_2$	$y_1 y_2$	$y_1 y_2$
B	A/0	C/0	A	B	C
C	C/0	D/0	B	C	D
D	C/1	A/0	C	D	A

$$D_1 = y_1 \bar{x} + y_2 x$$

$$D_2 = y_1 \bar{x} + \bar{y}_1 x$$

$$D_1 = y_1 \bar{x} + \bar{y}_2 x$$

$$D_2 = \bar{y}_1 \bar{x} + y_1 x$$

$$D_1 = y_2 \bar{x} + \bar{y}_2 x$$

$$D_2 = y_2 \bar{x} + y_1 x$$

NUMBER OF STATE ASSIGNMENTS.

N_S	N_{FF}	N_{SA}	N_{UA}
1	0	—	—
2	1	2	1
3	2	24	3
4	2	24	3
5	3	6,720	140
6	3	20,160	420
7	3	40,320	840
8	3	40,320	840
9	4	4.15×10^9	10,810,800
10	4	2.91×10^{10}	75,675,600


$$N_{UA} = \frac{(2^{N_{FF}} - 1)!}{(2^{N_{FF}} - N_S)! N_{FF}!}$$

4-Row Flow-Table Example

- ✓ A flow table with 4 states requires an assignment of two state variables.
- ✓ If there were no transitions in the diagonal direction (from a to c or from b to d), it would be possible to find adjacent assignment for the remaining 4 transitions.
- ✓ In general in order to satisfy the adjacency requirement, at least 3 binary variables are needed.

	00	01	11	10
a	b	a	d	a
b	b	d	b	a
c	c	a	b	c
d	c	d	d	c

(a) Flow table

 


(b) Transition diagram

4-Row Flow-Table Example


- The following state assignment map is suitable for any table.
 - $a, b, c,$ and d are the original states.
 - $e, f,$ and g are extra states.
 - States placed in adjacent squares in the map will have adjacent assignments
 - Please note that state variable order in figures is $y_3y_1y_2$**

	00	01	11	10
a	b	a	d	a
b	b	d	b	a
c	c	a	b	c
d	c	d	d	c

(a) Flow table

 

(a) Binary assignment

 

(b) Transition diagram

4-Row Flow-Table Example

✓ To produce cycles:

- The transition from **a** to **d** must be directed through the extra state **e**
- The transition from **c** to **a** must be directed through the extra state **g**
- The transition from **d** to **c** must be directed through the extra state **f**

	00	01	11	10
a	b	a	d	a
b	b	d	b	a
c	c	a	b	c
d	c	d	d	c

(a) Flow table


	00	01	11	10
000 = a	b	a	e	a
001 = b	b	d	b	a
011 = c	c	g	b	c
010 = g	-	a	-	-
110 -	-	-	-	-
111 = f	e	-	-	c
101 = d	f	d	d	f
100 = e	-	-	d	-

	$y_1 y_2$			
y_3	00	01	11	10
0	a	b	c	g
1	e	d	f	

Although the flow table has 7 rows, there are only 4 stable states.

Multiple Row Method

 - ✓ Multiple-row method is easier. May not as efficient as in above shared-row method
- ✓ Each stable state is duplicated with exactly the same output. Behaviors are still the same
- ✓ While choosing the next states, choose the adjacent one among the two possibilities



(a) Binary assignment

	00	01	11	10
000 = a_1	b_1	a_1	d_1	a_1
111 = a_2	b_2	a_2	d_2	a_2
001 = b_1	b_1	d_2	b_1	a_1
110 = b_2	b_2	d_1	b_2	a_2
011 = c_1	c_1	a_2	b_1	c_1
100 = c_2	c_2	a_1	b_2	c_2
010 = d_1	c_1	d_1	d_1	c_1
101 = d_2	c_2	d_2	d_2	c_2


(b) Flow table

Don't Care Assignment

	00	01	11	10
<i>a</i>	\textcircled{a}	<i>b</i>	-	<i>c</i>
<i>b</i>	\textcircled{b}	\textcircled{b}	<i>c</i>	<i>d</i>
<i>c</i>	-	<i>d</i>	\textcircled{c}	\textcircled{c}
<i>d</i>	<i>a</i>	\textcircled{d}	\textcircled{d}	\textcircled{d}

Needed Transitions

 column 00: $d \rightarrow a$
column 01: $a \rightarrow b, c \rightarrow d$
column 11: $b \rightarrow c$
column 10: $a \rightarrow c, b \rightarrow d$




- ✓ All possible transitions between pairs of rows are needed
- ✓ Fill in don't care to eliminate races
- ✓ Direct transitions for columns 01, 10 (No don't care)

Don't Care Assignment


	00	01	11	10
<i>a</i>	(<i>a</i>)	<i>b</i>	-	<i>c</i>
<i>b</i>	(<i>b</i>)	(<i>b</i>)	<i>c</i>	<i>d</i>
<i>c</i>	-	<i>d</i>	(<i>c</i>)	(<i>c</i>)
<i>d</i>	<i>a</i>	(<i>d</i>)	(<i>d</i>)	(<i>d</i>)

column 00: $d \rightarrow a$
 column 01: $a \rightarrow b, c \rightarrow d$
 column 11: $b \rightarrow c$
 column 10: $a \rightarrow c, b \rightarrow d$

Needed Transitions

 

 - ✓ All possible transitions between pairs of rows are needed
- ✓ Fill in don't care to eliminate races
- ✓ Direct transitions for columns 01, 10 (No don't care)





	00	01	11	10
00 <i>a</i>	(<i>a</i>)	<i>b</i>	<i>c</i>	<i>c</i>
01 <i>b</i>	(<i>b</i>)	(<i>b</i>)	<i>a</i>	<i>d</i>
10 <i>c</i>	<i>a</i>	<i>d</i>	(<i>c</i>)	(<i>c</i>)
11 <i>d</i>	<i>c</i>	(<i>d</i>)	(<i>d</i>)	(<i>d</i>)

In column 00: $d \Rightarrow a$ changed to $d \Rightarrow c \Rightarrow a$.
 In column 11: $b \Rightarrow c$ changed to $b \Rightarrow a \Rightarrow c$.

Extra raw flow table

I	I			
	I ₁	I ₂	I ₃	I ₄
a	C,1	B,0	A,1	C,-
b	C,1	B,0	A,1	A,-
c	C,1	A,-	C,0	D,0
d	E,0	D,1	C,0	D,0
e	E,0	D,1	F,-	E,1
f	D,-	D,1	B,-	F,0

	I ₁	I ₂	I ₃	I ₄
a	C,1	G,0	A,1	C,-
b	C,1	B,0	G,1	A,-
c	C,1	A,-	C,0	D,0
d	E,0	D,1	C,0	D,0
e	E,0	D,1	H,-	E,1
f	D,-	D,1	B,-	F,0
g	-, -	B,-	A,-	-, -
h	-, -	-, -	F,-	-, -


 
 


		y ₁ y ₂			
		00	01	11	10
y ₃	0	G → B		F ← H	
	1	A → C		D ← E	

Alternative solution: transition changes

	I			
	I ₁	I ₂	I ₃	I ₄
a	C,1	B,0	A,1	C,-
b	C,1	B,0	A,1	A,-
c	C,1	A,-	C,0	D,0
d	E,0	D,1	C,0	D,0
e	E,0	D,1	F,-	E,1
f	D,-	D,1	B,-	F,0

	I			
	I ₁	I ₂	I ₃	I ₄
a	C,1	B,0	A,1	C,-
b	A*,1	B,0	A,1	A,-
c	C,1	A,-	C,0	D,0
d	E,0	D,1	C,0	D,0
e	E,0	D,1	F,-	E,1
f	E*,-	D,1	B,-	F,0

   


Summary


- ✓ Shared row method
- ✓ Multiple row method
- ✓ Don't care assignment
- ✓ Universal states assignment
- ✓ Transition changes
- ✓ Other approaches¹

¹ VP Nelson et al., not presented here

Hazards in combinational circuits

 





(a) AND-OR circuit

 

    
(b) NAND circuit

✓ Static 1-hazard (sum of products)

- The remedy
 - the circuit moves from one product term to another
 - additional redundant gate




(a) $Y = x_1x_2 + x'_2x_3$

 

(b) $Y = x_1x_2 + x'_2x_3 + x_1x_3$

Hazards in sequential circuits

✓ An asynchronous example:

 

(a) Logic diagram

		$x_1 x_2$			
		00	01	11	10
y	0	0	0	1	0
	1	1	0	1	1

(b) Transition table



111 → 110
111 → 010

		$x_1 x_2$			
		00	01	11	10
y	0			1	
	1	1		1	1

  (c) Map for Y

Remove Hazards with Latches

- ✓ The implementation of the asynchronous circuits with SR latches can remove static hazards




- ✓ SR Latch (NOR type)
 - Allow 1-hazard (a momentary 0 has no effect)
 - The network realizing S and R must be free of 0-hazards.
- ✓ S'R' Latch (NAND type)
 - Allow 0-hazard (a momentary 1 has no effect)
 - The network realizing S and R must be free of 1-hazards.
- ✓ Note that a sum-of-products implementation is **automatically free of static 0-hazards** and a product-of-sums implementation is free of static 1-hazards.


Hazard-Free Realization

✓ S-R Latch (NOR type):

 S-R Flip-Flop Driven by
2-level AND-OR Networks



 Equivalent Network Structure
(in general faster)



Essential Hazards

- ✓ Besides static and dynamic hazards, another type of hazard in asynchronous circuits is called: **Essential Hazard**
- ✓ It is caused by unequal delays along two or more paths that originate from the same input
- ✓ Cannot be corrected by adding redundant gates
- ✓ Can only be corrected by adjusting the amount of delay in the affected path
 - **Each feedback path should be examined carefully !!**

Design Example

Recommended Design Procedure:

1. State the design specifications.
2. Derive a Primitive Flow Table.
3. Reduce the Flow Table by merging rows.
4. Make a race-free binary state assignment.
5. Obtain the transition table and output map.
6. Obtain the logic diagram using **SR** latches.

Design Example

1) Design Specifications:

The objective is to design a negative-edge-triggered T flip-flop. The circuit has two inputs T (toggle) and C (clock) and one output Q. The output state is complemented if $T=1$ and the clock changes from 1 to 0 (negative-edge-triggering). Otherwise, under all input condition, the output remains unchanged.


- A Negative-Edge-Triggered T FF
- Two inputs : T, C
- Flip-Flop changes state when $T = 1$ and C changes from 1 to 0
- Q remains constant under all other conditions
- T and C do not change simultaneously

Design Example

2) Primitive Flow Table

State	Inputs		Output
	<i>T</i>	<i>C</i>	<i>Q</i>
<i>a</i>	1	1	0
<i>b</i>	1	0	1
<i>c</i>	1	1	1
<i>d</i>	1	0	0
<i>e</i>	0	0	0
<i>f</i>	0	1	0
<i>g</i>	0	0	1
<i>h</i>	0	1	1

	<i>TC</i>			
	00	01	11	10
<i>a</i>	-, -	<i>f</i> , -	(<i>a</i>), 0	<i>b</i> , -
<i>b</i>	<i>g</i> , -	-, -	<i>c</i> , -	(<i>b</i>), 1
<i>c</i>	-, -	<i>h</i> , -	(<i>c</i>), 1	<i>d</i> , -
<i>d</i>	<i>e</i> , -	-, -	<i>a</i> , -	(<i>d</i>), 0
<i>e</i>	(<i>e</i>), 0	<i>f</i> , -	-, -	<i>d</i> , -
<i>f</i>	<i>e</i> , -	(<i>f</i>), 0	<i>a</i> , -	-, -
<i>g</i>	(<i>g</i>), 1	<i>h</i> , -	-, -	<i>b</i> , -
<i>h</i>	<i>g</i> , -	(<i>h</i>), 1	<i>c</i> , -	-, -

 

Design Example


3) Merging of the Flow Table

Implication Table

b	a, c X						
c	X b, d X						
d	b, d X	X a, c X					
e	b, d X	e, g X b, d X	f, h X	✓			
f	✓	e, g X a, c X	f, h X a, c X	✓	✓		
g	f, h X	✓	b, d X	e, g X b, d X	X	e, g X f, h X	
h	f, h X a, c X	✓	✓	d, e X c, f X	e, g X f, h X	X	✓
	a	b	c	d	e	f	g

Compatible pairs:

 $(a, f) (b, g) (b, h) (c, h) (d, e) (d, f) (e, f) (g, h)$




The maximal compatibles pairs are:

$(a, f) (b, g, h) (c, h) (d, e, f)$

$U=4$

Maximal Incompatibles

 

L=4

b	a, c ×						
c	× b, d ×						
d	b, d ×	× a, c ×					
e	b, d ×	e, g × b, d ×	f, h ×	✓			
f	✓	e, g × a, c ×	f, h × a, c ×	✓	✓		
g	f, h ×	✓	b, d ×	e, g × b, d ×	×	e, g × f, h ×	
h	f, h × a, c ×	✓	✓	d, e × c, f ×	e, g × f, h ×	×	✓
	a	b	c	d	e	f	g

Design Example

- ✓ In this particular example, the minimal collection of compatibles is also the maximal compatibles set that satisfy also the closed condition:

(a, f) (b, g, h) (c, h) (d, e, f)

	TC			
	00	01	11	10
a, f	e, -	(f), 0	(a), 0	b, -
b, g, h	(g), 1	(h), 1	c, -	(b), 1
c, h	g, 1	(h), 1	(c), 1	d, -
d, e, f	(e), 0	(f), 0	a, -	(d), 0

(a)


	TC			
	00	01	11	10
a	d, -	(a), 0	(a), 0	b, -
b	(b), 1	(b), 1	c, -	(b), 1
c	b, -	(c), 1	(c), 1	d, -
d	(d), 0	(d), 0	a, -	(d), 0

(b)

Design Example

 4) State Assignment and Transition Table

- ✓ No diagonal lines in the transition diagram: No need to add extra states (race-free binary state assignment!)



	TC			
$y_1 y_2$	00	01	11	10
$a = 00$	10	00	00	01
$b = 01$	01	01	11	01
$c = 11$	01	11	11	10
$d = 10$	10	10	00	10

(a) Transition table

	TC			
$y_1 y_2$	00	01	11	10
00	0	0	0	X
01	1	1	1	1
11	1	1	1	X
10	0	0	0	0

(b) Output map $Q = y_2$

Design Example

5) Logic Diagram

		TC			
		00	01	11	10
y_1y_2	00	1	0	0	0
	01	0	0	1	0
	11	0	X	X	X
	10	X	X	0	X

(a) $S_1 = y_2 TC + y_2' TC'$

		TC			
		00	01	11	10
y_1y_2	00	0	X	X	X
	01	X	X	0	X
	11	1	0	0	0
	10	0	0	1	0

(b) $R_1 = y_2 T' C' + y_2' TC$

		TC			
		00	01	11	10
y_1y_2	00	0	0	0	1
	01	X	X	X	X
	11	X	X	X	0
	10	0	0	0	0

(c) $S_2 = y_1' TC'$

		TC			
		00	01	11	10
y_1y_2	00	X	X	X	0
	01	0	0	0	0
	11	0	0	0	1
	10	X	X	X	X

(d) $R_2 = y_1 TC'$

