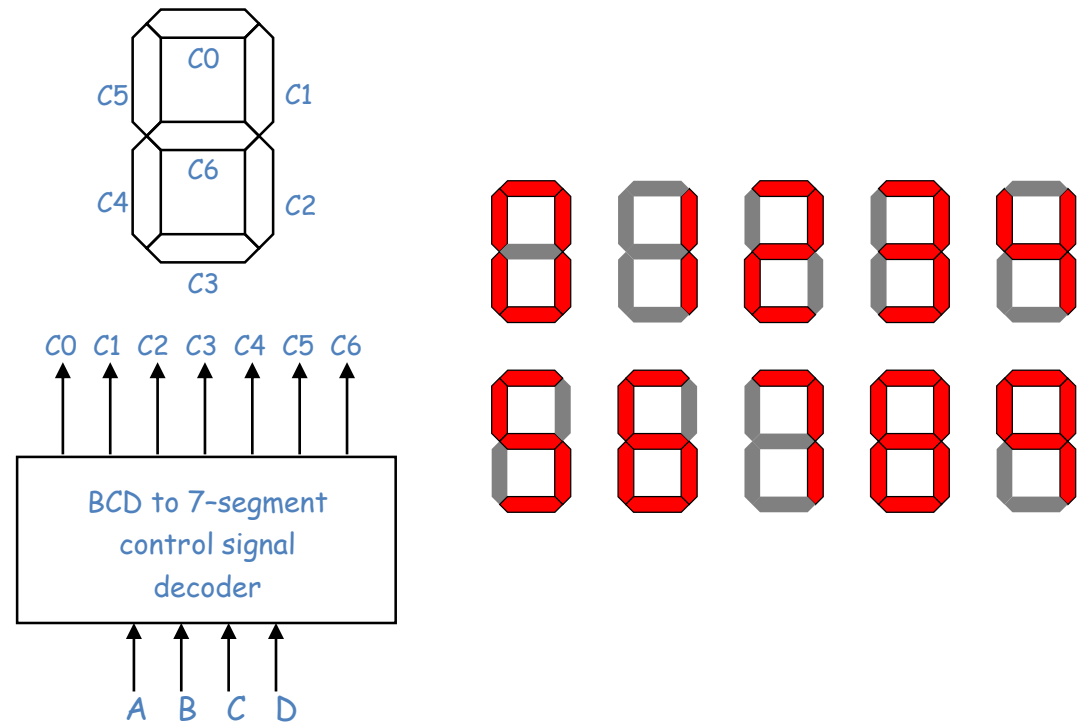


# BCD to 7-segment display controller


## ✓ Specification

- Digital readouts on many digital products often use LED seven-segment displays.
- Input is a 4 bit BCD digit (A, B, C, D)
- Output is the control signals for the display (7 outputs C0 - C6)



# Formulation


- ✓ Construct a truth table

 


Decimal Digit	Input BCD	Seven-Segment Decoder Outputs						
		C0	C1	C2	C3	C4	C5	C6
0	0 0 0 0	1	1	1	1	1	1	0
1	0 0 0 1	0	1	1	0	0	0	0
2	0 0 1 0	1	1	0	1	1	0	1
3	0 0 1 1	1	1	1	1	0	0	1
4	0 1 0 0	0	1	1	0	0	1	1
5	0 1 0 1	1	0	1	1	0	1	1
6	0 1 1 0	1	0	1	1	1	1	1
7	0 1 1 1	1	1	1	0	0	0	0
8	1 0 0 0	1	1	1	1	1	1	1
9	1 0 0 1	1	1	1	1	0	1	1
All other inputs		0	0	0	0	0	0	0

# Optimization


$$C0 = A'C + AB'C' + A'BD + B'C'D'$$

 


$$C1 = A'B' + B'C' + A'C'D' + A'CD$$

 

$$C2 = A'B + A'D + B'C'$$

 

 
$$C3 = AB'C' + A'B'C + A'C'D' + A'BC'D + B'C'D'$$




# Optimization


$$C4 = A'CD' + B'C'D'$$

 

$$C5 = AB'C' + A'BC' + A'BD' + A'C'D'$$

 

$$C6 = AB'C' + A'BC' + A'CD' + A'B'C'$$

 

# Optimization

---

- ✓ Create a K-map for each output and get:

$$C0 = A'C + AB'C' + A'BD + B'C'D'$$

$$C1 = A'B + B'C' + A'C'D' + A'CD$$

$$C2 = A'B + A'D + B'C'$$

$$C3 = AB'C' + A'B'C + A'CD' + A'BC'D + B'C'D'$$

$$C4 = A'CD' + B'C'D'$$


$$C5 = AB'C' + A'BC' + A'BD' + A'C'D'$$

$$C6 = AB'C' + A'BC' + A'CD' + A'B'C$$

- ✓ Direct implementation would require 26 AND gates and 7 OR gates.
- ✓ By sharing terms, can actualize with 11 less AND gates maintaining just 2 levels.
 
# Formulation


- ✓ Construct a truth table with don't care




Decimal Digit	Input BCD	Seven-Segment Decoder Outputs						
		C0	C1	C2	C3	C4	C5	C6
0	0 0 0 0	1	1	1	1	1	1	0
1	0 0 0 1	0	1	1	0	0	0	0
2	0 0 1 0	1	1	0	1	1	0	1
3	0 0 1 1	1	1	1	1	0	0	1
4	0 1 0 0	0	1	1	0	0	1	1
5	0 1 0 1	1	0	1	1	0	1	1
6	0 1 1 0	1	0	1	1	1	1	1
7	0 1 1 1	1	1	1	0	0	0	0
8	1 0 0 0	1	1	1	1	1	1	1
9	1 0 0 1	1	1	1	1	0	1	1
All other inputs		X	X	X	X	X	X	X

# Optimization


$$C0 = A + C + BD + B'D'$$

 


$$C2 = B + C' + D$$

 

$$C1 = B' + C'D' + CD$$

 


$$C3 = A + B'D' + B'C + CD' + BC'D$$

 


# Optimization


$$C4 = B'D' + CD'$$

 

$$C5 = A + BC' + BD' + C'D'$$

 

$$C6 = A + BC' + B'C + CD'$$

 



# Optimization Exploiting DC

---

- ✓ Create a K-map for each output and get
  - $C0 = A + C + BD + B'D'$
  - $C1 = B' + C'D' + CD$
  - $C2 = B + C' + D$
  - $C3 = A + B'C + B'D' + CD' + BC'D$
  - $C4 = B'D' + CD'$
  - $C5 = A + C'D' + BD' + BC'$
  - $C6 = A + B'C + BC' + CD'$
- ✓ Direct implementation would require 16 AND gates and 7 OR gates.
- ✓ By sharing terms, can actualize with 7 less AND gates maintaining just 2 levels.