

# BCD-to-Excess-3 Code converter

---

- ✓ BCD is a code for the decimal digits 0-9
- ✓ Excess-3 is also a code for the decimal digits

Decimal Digit	Input BCD	Output Excess-3
0	0 0 0 0	0 0 1 1
1	0 0 0 1	0 1 0 0
2	0 0 1 0	0 1 0 1
3	0 0 1 1	0 1 1 0
4	0 1 0 0	0 1 1 1
5	0 1 0 1	1 0 0 0
6	0 1 1 0	1 0 0 1
7	0 1 1 1	1 0 1 0
8	1 0 0 0	1 0 1 1
9	1 0 0 1	1 1 0 0

# Specification of BCD-to-Excess3

---

- ✓ Inputs: a BCD input,  $A, B, C, D$  with  $A$  as the most significant bit and  $D$  as the least significant bit.
- ✓ Outputs: an Excess-3 output  $W, X, Y, Z$  that corresponds to the BCD input.
- ✓ Internal operation - circuit to do the conversion in combinational logic.

# Formulation of BCD-to-Excess-3


---

- ✓ Excess-3 code is easily formed by adding a binary 3 to the binary or BCD for the digit.
- ✓ There are 16 possible inputs for both BCD and Excess-3.
- ✓ It can be assumed that only valid BCD inputs will appear so the six combinations not used can be treated as don't cares.
 
# Placing 1 on K-maps

---

- ✓ Where are the minterms located on a K-Map?




# Expressions for W X Y Z

---

- ✓  $W(A,B,C,D) = \Sigma m(5,6,7,8,9)$   
 $+d(10,11,12,13,14,15)$
- ✓  $X(A,B,C,D) = \Sigma m(1,2,3,4,9)$   
 $+d(10,11,12,13,14,15)$
- ✓  $Y(A,B,C,D) = \Sigma m(0,3,4,7,8)$   
 $+d(10,11,12,13,14,15)$
- ✓  $Z(A,B,C,D) = \Sigma m(0,2,4,6,8)$   
 $+d(10,11,12,13,14,15)$
 
# Optimization - BCD-to-Excess-3


✓ Lay out K-maps for each output, W X Y Z



✓ A step in the digital circuit design process.

# Minimize K-Maps


- ✓ W minimization

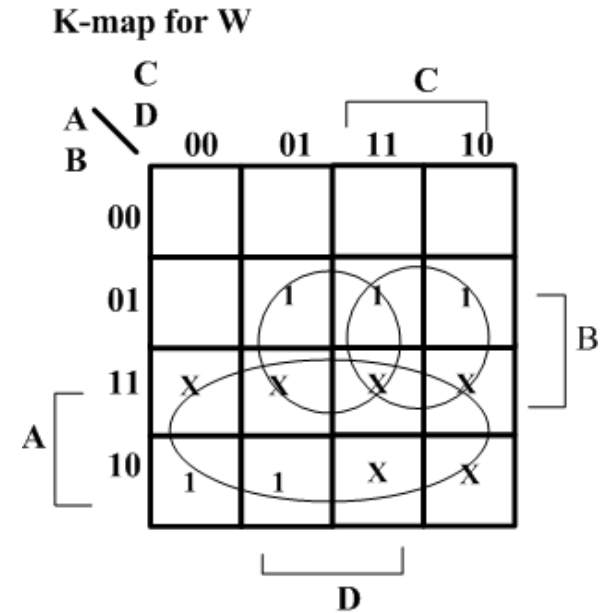

$$W = A + BC + BD$$

# Minimize K-Maps

✓ X minimization

 


$$X = BC'D' + B'C + B'D$$



# Minimize K-Maps


✓ Y minimization

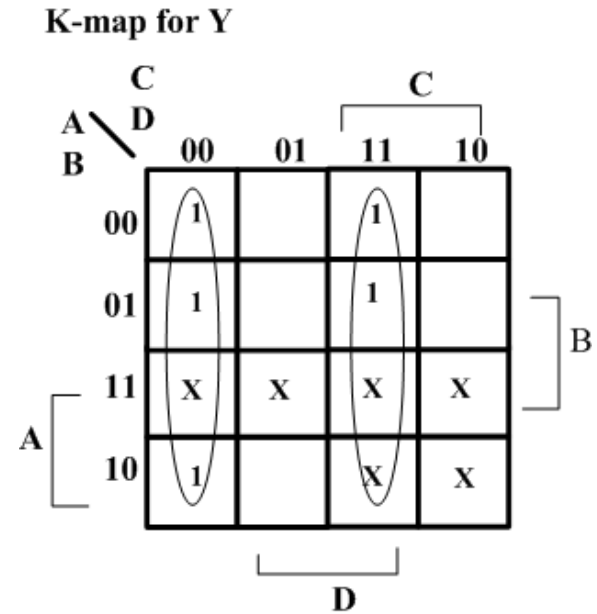

$$Y = CD + C'D'$$

# Minimize K-Maps

✓ Z minimization

 

$$Z = D'$$

# Two level circuit implementation

---

## ✓ Have equations

- $W = A + BC + BD = A + B(C+D)$
- $X = B'C + B'D + BC'D' = B'(C+D) + BC'D'$
- $Y = CD + C'D'$
- $Z = D'$

## ✓ Factoring out $(C+D)$ and call it $T$


## ✓ Then $T' = (C+D)' = C'D'$

- $W = A + BT$
- $X = B'T + BT'$
- $Y = CD + T'$
- $Z = D'$
 
# Create the digital circuit

---

- ✓ Implementing the second set of equations where  $T=C+D$  results in a lower gate count.
- ✓ This gate has a fanout of 3



# BCD-to-Seven-Segment Decoder

---


## ✓ Specification

- Digital readouts on many digital products often use LED seven-segment displays.
- Each digit is created by lighting the appropriate segments. The segments are labeled a,b,c,d,e,f,g
- The decoder takes a BCD input and outputs the correct code for the seven-segment display.
 
# Specification

---


- ✓ Input: A 4-bit binary value that is a BCD coded input.
- ✓ Outputs: 7 bits, a through g for each of the segments of the display.
- ✓ Operation: Decode the input to activate the correct segments.



# Formulation

---

✓ Construct a truth table

 

Decimal Digit	Input BCD	Seven-Segment Decoder Outputs						
		a	b	c	d	e	f	g
0	0 0 0 0	1	1	1	1	1	1	0
1	0 0 0 1	0	1	1	0	0	0	0
2	0 0 1 0	1	1	0	1	1	0	1
3	0 0 1 1	1	1	1	1	0	0	1
4	0 1 0 0	1	0	1	1	0	1	1
5	0 1 0 1	1	0	1	1	0	1	1
6	0 1 1 0	1	0	1	1	1	1	1
7	0 1 1 1	1	1	1	0	0	0	0
8	1 0 0 0	1	1	1	1	1	1	1
9	1 0 0 1	1	1	1	1	0	1	1
All other inputs		0	0	0	0	0	0	0

# Optimization

---

✓ Create a K-map for each output and get

- $A = A'C + A'BD + B'C'D' + AB'C'$
- $B = A'B' + A'C'D' + A'CD + AB'C'$
- $C = A'B + A'D + B'C'D' + AB'C'$
- $D = A'CD' + A'B'C + B'C'D' + AB'C' + A'BC'D$
- $E = A'CD' + B'C'D'$
- $F = A'BC' + A'C'D' + A'BD' + AB'C'$
- $G = A'CD' + A'B'C + A'BC' + AB'C'$



# Note on implementation

---

- ✓ Direct implementation would require 27 AND gates and 7 OR gates.
- ✓ By sharing terms, can actualize and implementation with 14 less gates maintaining just 2 levels.
- ✓ Normally decoder in a device name indicates that the number of outputs is less than the number of inputs.