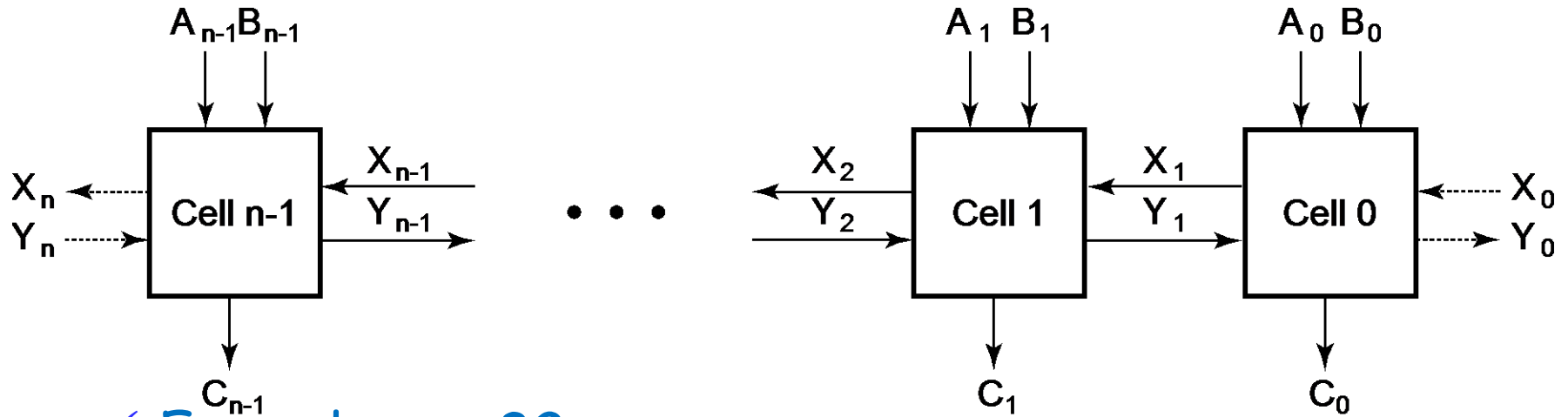


Iterative Combinational Circuits

- ✓ Arithmetic functions
 - Operate on **binary vectors**
 - Use the **same subfunction in each bit position**
- ✓ Can design functional block for sub-function and repeat to obtain functional block for overall function
- ✓ **Cell** - sub-function block
- ✓ **Iterative array** - an array of interconnected cells
- ✓ An iterative array can be in a **single** dimension (1D) or **multiple** dimensions (**wavefront** and **systolic array**)

Block Diagram of a 1D Iterative Array



✓ Example: $n = 32$

- Number of inputs = ?
- Truth table rows = ?
- Equations with huge number of terms

✓ Iterative array takes advantage of the regularity to make design feasible

Functional Blocks: Addition

✓ Addition Development:

- **Half-Adder (HA)**, a 2-input bit-wise addition functional block,
- **Full-Adder (FA)**, a 3-input bit-wise addition functional block,
- **Ripple Carry Adder**, an iterative array to perform binary addition
- **Carry-Look-Ahead Adder (CLA)**, a hierarchical structure to improve performance.

Functional Block: Half-Adder

- ✓ A 2-input, 1-bit width binary adder that performs the following computations:

$$\begin{array}{r} X \\ + Y \\ \hline C S \end{array} \quad \begin{array}{r} 0 \\ + 0 \\ \hline 0 0 \end{array} \quad \begin{array}{r} 0 \\ + 1 \\ \hline 0 1 \end{array} \quad \begin{array}{r} 1 \\ + 0 \\ \hline 0 1 \end{array} \quad \begin{array}{r} 1 \\ + 1 \\ \hline 1 0 \end{array}$$

- ✓ A half adder adds two bits to produce a two-bit sum
- ✓ The sum is expressed as a **sum bit**, S and a **carry bit**, C

- ✓ The half adder can be specified a truth table for S and C \Rightarrow

X	Y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Logic Simplification: Half-Adder

- ✓ The K-Map for S , C is:

	y	
S		
	0	1
X	1	3

	y	
C		
	0	1
X	2	1

- ✓ This is a pretty trivial map! By inspection:

$$S = X \cdot \bar{Y} + \bar{X} \cdot Y = X \oplus Y$$

$$S = (X + Y) \cdot (\bar{X} + \bar{Y})$$

- ✓ and

$$C = X \cdot Y$$

$$C = \overline{\overline{(X \cdot Y)}}$$

- ✓ These equations lead to several implementations.

Five Implementations: Half-Adder

- ✓ We can derive following sets of equations for a half-adder:

$$(a) \begin{aligned} S &= X \cdot \bar{Y} + \bar{X} \cdot Y \\ C &= X \cdot Y \end{aligned}$$

$$(d) \begin{aligned} S &= (X + Y) \cdot \bar{C} \\ \bar{C} &= (\bar{X} + \bar{Y}) \end{aligned}$$

$$(b) \begin{aligned} S &= (X + Y) \cdot (\bar{X} + \bar{Y}) \\ C &= X \cdot Y \end{aligned}$$

$$(e) \begin{aligned} S &= X \oplus Y \\ C &= X \cdot Y \end{aligned}$$


$$(c) \begin{aligned} S &= \overline{(C + \bar{X} \cdot \bar{Y})} \\ C &= X \cdot Y \end{aligned}$$

- ✓ (a), (b), and (e) are SOP, POS, and XOR implementations for S.
- ✓ In (c), the C function is used as a term in the AND-NOR implementation of S, and in (d), the \bar{C} function is used in a POS term for S.

Implementations: Half-Adder


- ✓ The most common half adder implementation is:
(e)

$$S = X \oplus Y$$
$$C = X \cdot Y$$

 

- ✓ A NAND only implementation is:
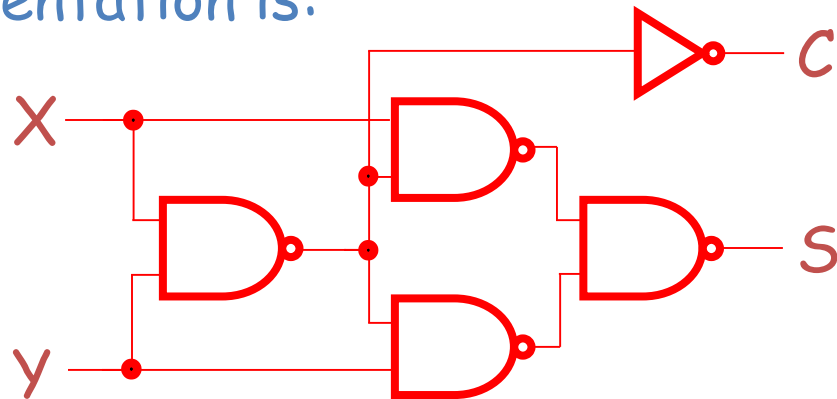
$$S = \overline{(X + Y)} \cdot \bar{C}$$
$$C = \overline{(\overline{(X \cdot Y)})}$$



Functional Block: Full-Adder

- ✓ A full adder is similar to a half adder, but includes a **carry-in bit from lower stages**. Like the half-adder, it computes a sum bit, S and a carry bit, C .

- For a carry-in (Z) of 0, it is the same as the half-adder:

	Z	0	0	0	0
	X	0	0	1	1
	$+ Y$	$+ 0$	$+ 1$	$+ 0$	$+ 1$
	$C S$	00	01	01	10

- For a carry- in (Z) of 1:

	Z	1	1	1	1
	X	0	0	1	1
	$+ Y$	$+ 0$	$+ 1$	$+ 0$	$+ 1$
	$C S$	01	10	10	11

Logic Optimization: Full-Adder

✓ Full-Adder Truth Table:

X	Y	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

✓ Full-Adder K-Map:

S	Y			
	0	1	3	2
X	1 ₄	1 ₁	1 ₇	
	Z			

C	Y			
	0	1	3	2
X		1 ₅	1 ₃	1 ₆
	Z			

Equations: Full-Adder

- ✓ From the K-Map, we get:

$$S = X \bar{Y} \bar{Z} + \bar{X} Y \bar{Z} + \bar{X} \bar{Y} Z + X Y Z$$

$$C = X Y + X Z + Y Z = X Y + (X + Y) Z$$

- ✓ The S function is the three-bit XOR function (Odd Function):

$$S = X \oplus Y \oplus Z$$


- ✓ The Carry bit C is 1 if both X and Y are 1 (the sum is 2), or if the sum is 1 and a carry-in (Z) occurs. Thus C can be re-written as:

$$C = X Y + (X \oplus Y) Z$$

- ✓ The term $X \cdot Y$ is carry generate.
- ✓ The term $X \oplus Y$ is carry propagate.

Implementation: Full Adder

 - ✓ Full Adder Schematic
- ✓ Here X , Y , and Z , and C (from the previous pages) are A , B , C_i and C_o , respectively. Also,
 G = generate and
 P = propagate.
- ✓ Note: This is really a combination of a 3-bit odd function (for S) and Carry logic (for C_o):




(G = Generate) OR (P = Propagate AND C_i = Carry In)

$$C_{i+1} = G + P \cdot C_i$$

Sequential Adder

 - ✓ 1-bit memory and 2 4-bit memory
- ✓ Only one full-adder!
- ✓ 4 clocks to get the output
- ✓ The 1-bit memory defines the circuit state (0 or 1)




Binary Adders

- ✓ To add multiple operands, we “bundle” logical signals together into vectors and use **functional blocks that operate on the vectors**
- ✓ Example: **4-bit ripple carry adder**: Adds input vectors $A(3:0)$ and $B(3:0)$ to get a sum vector $S(3:0)$
- ✓ Note: carry **out** of cell i becomes carry **in** of cell $i+1$

Description	Subscript 3 2 1 0	Name
Carry In	0 1 1 0	C_i
Augend	1 0 1 1	A_i
Addend	0 0 1 1	B_i
Sum	1 1 1 0	S_i
Carry out	0 0 1 1	C_{i+1}

4-bit Ripple-Carry Binary Adder


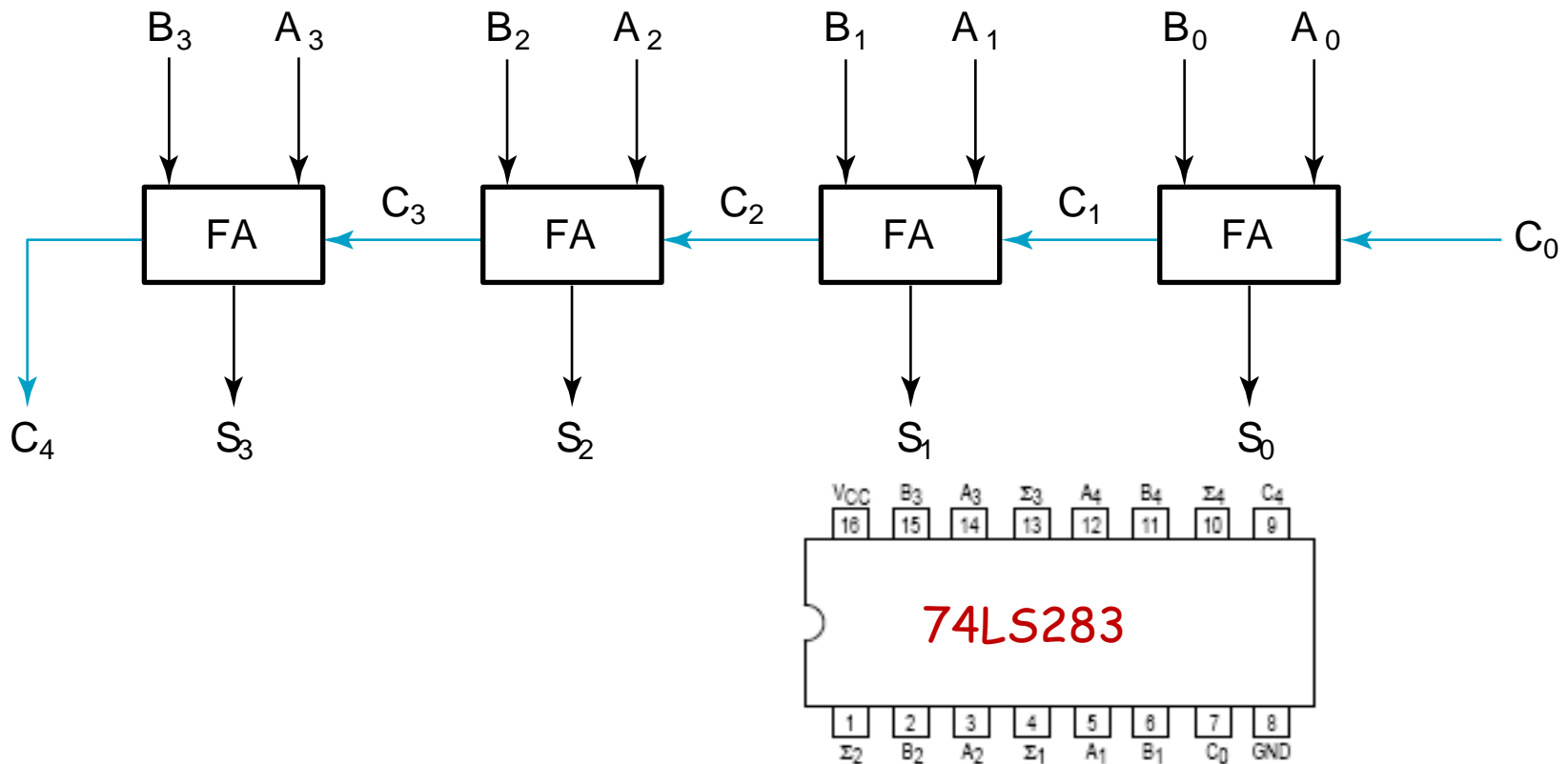
- ✓ A four-bit Ripple Carry Adder made from four 1-bit Full Adders:



Ripple-Carry Adders

✓ Critical Delay

 
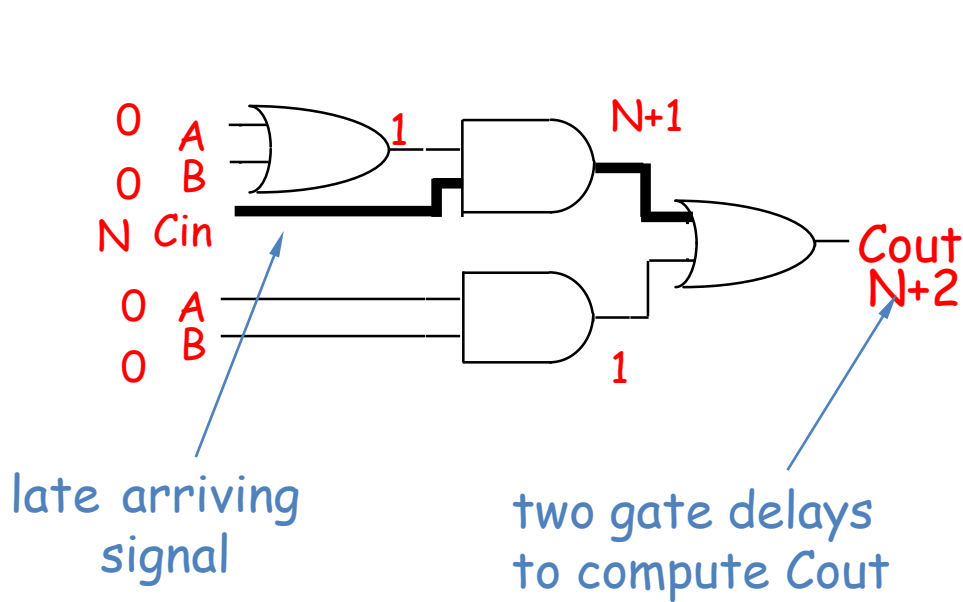
- The propagation of carry from low to high order stages




Ripple-Carry Adders (cont'd)

✓ Critical delay

  - The propagation of carry from low to high order stages
- 1111 + 0001 is the worst case addition
- Carry must propagate through all bits




Ripple-Carry Adders (cont'd)

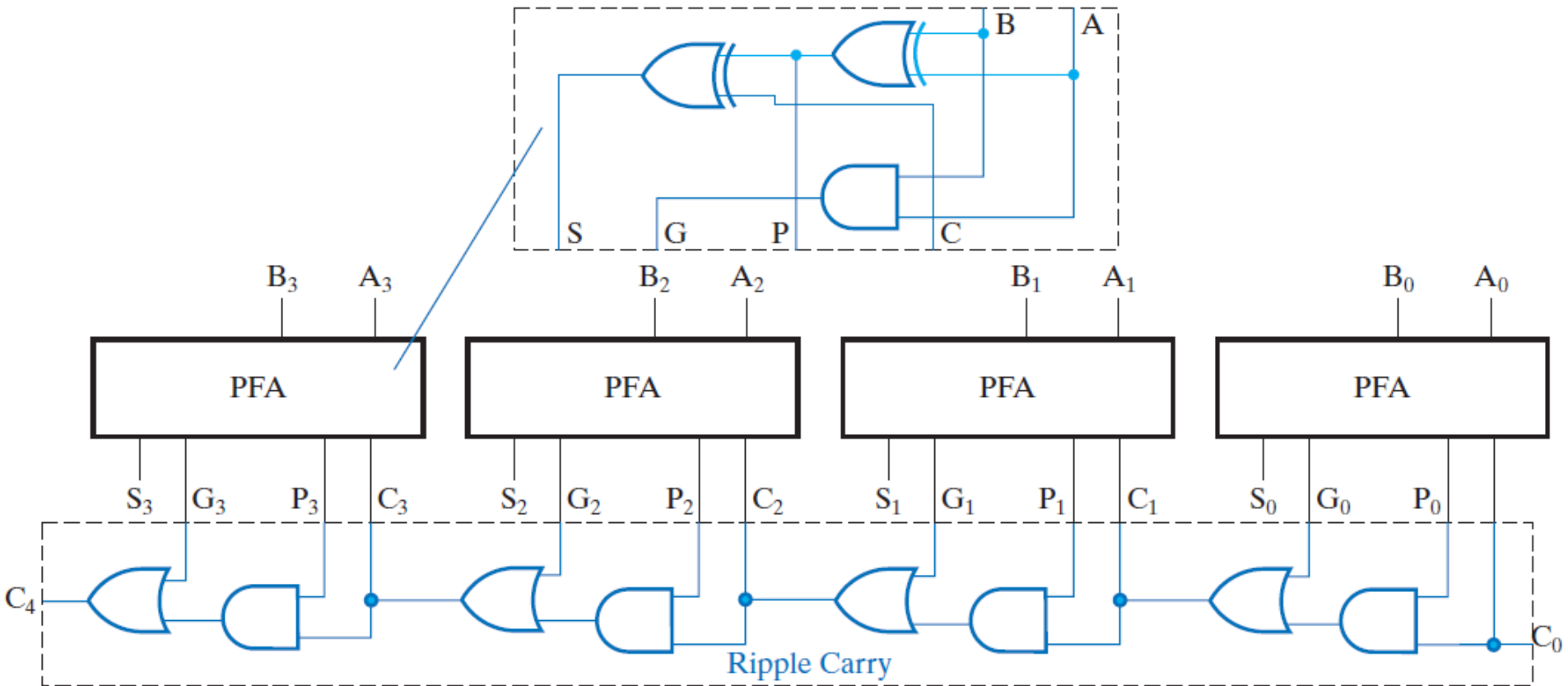

Carry-Lookahead Logic

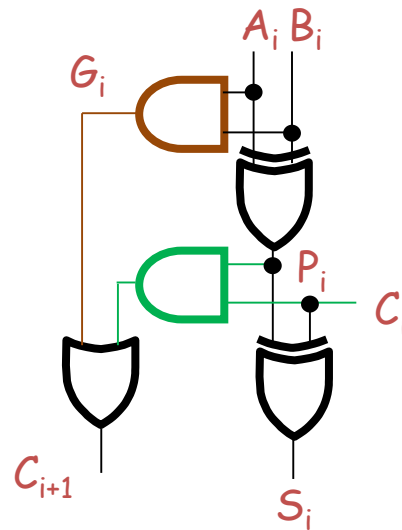
- ✓ Carry generate: $G_i = A_i B_i$
 - Must generate carry when $A = B = 1$
- ✓ Carry propagate: $P_i = A_i \text{ xor } B_i$
 - Carry-in will equal carry-out here
- ✓ Sum and Cout can be re-expressed in terms of generate/propagate:
 - $S_i = A_i \text{ xor } B_i \text{ xor } C_i$
 $= P_i \text{ xor } C_i$
 - $C_{i+1} = G_i + C_i P_i$



Carry-Lookahead Logic (cont'd)

- ✓ Re-express the carry logic as follows:
 - $C_1 = G_0 + P_0C_0$
 - $C_2 = G_1 + P_1C_1 = G_1 + P_1G_0 + P_1P_0C_0$
 - $C_3 = G_2 + P_2C_2 = G_2 + P_2G_1 + P_2P_1G_0 + P_2P_1P_0C_0$
 - $C_4 = G_3 + P_3C_3 = G_3 + P_3G_2 + P_3P_2G_1 + P_3P_2P_1G_0 + P_3P_2P_1P_0C_0$
- ✓ Each of the carry equations can be implemented with two-level logic
 - All inputs are now directly derived from data inputs and not from intermediate carries
 - this allows computation of all sum outputs to proceed in parallel

Carry-Lookahead Implementation (cont'd)

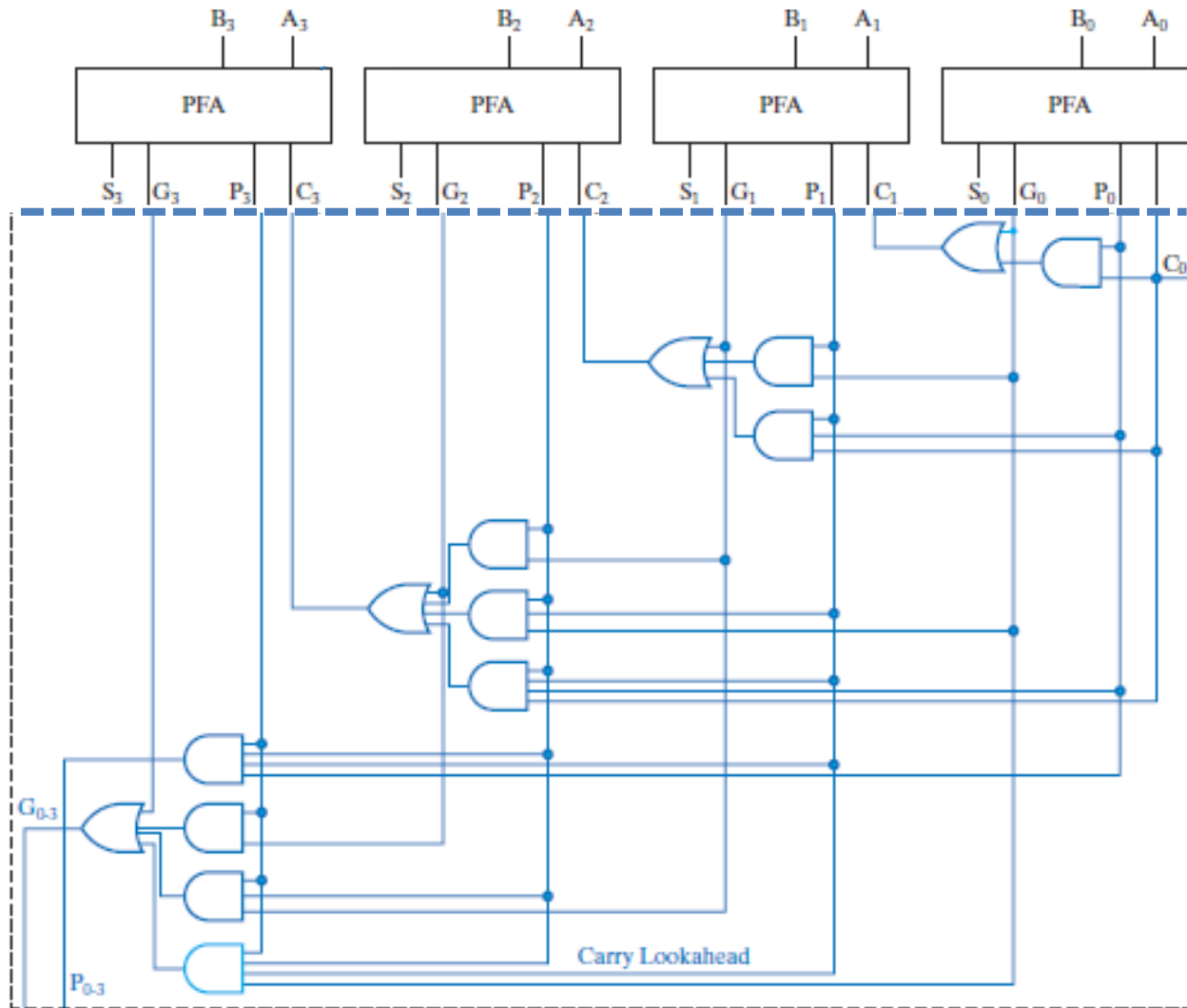


2's Complement Adder/Subtractor

- ✓ Subtraction can be done by addition of the 2's Complement.
 1. Complement each bit (1's Complement.)
 2. Add 1 to the result.

- ✓ The circuit shown computes $A + B$ and $A - B$:


- ✓ For $S = 1$, subtract, the 2's complement of B is formed by using XORs to form the 1's comp and adding the 1 applied to C_0 .

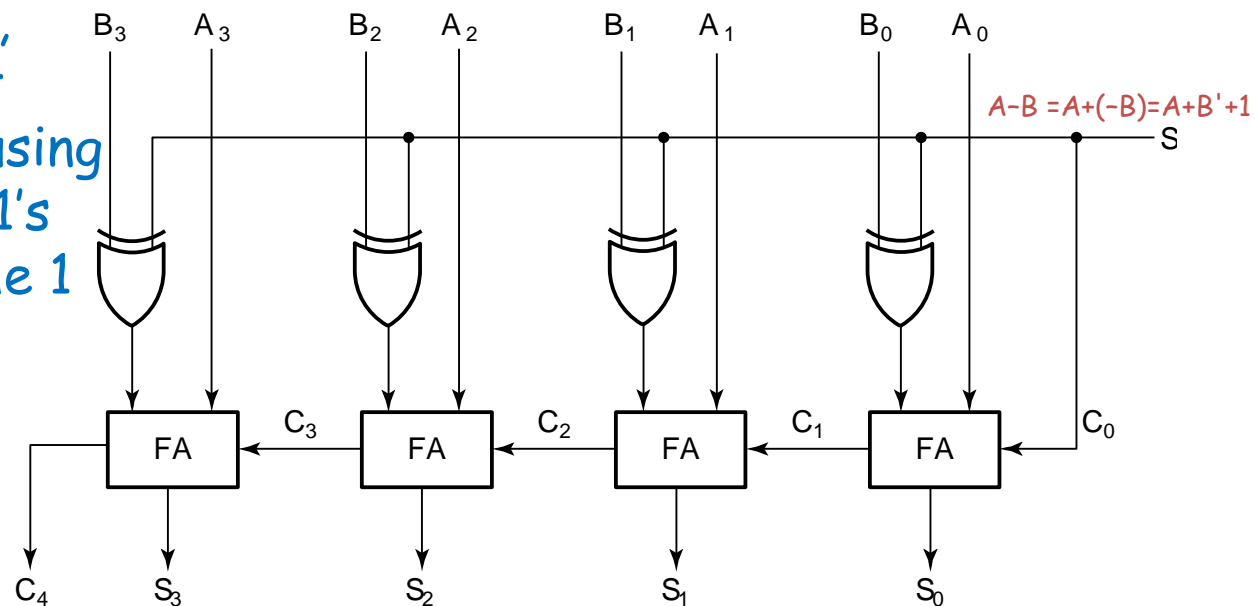- ✓ For $S = 0$, add, B is passed through unchanged



Carry-Select Adder

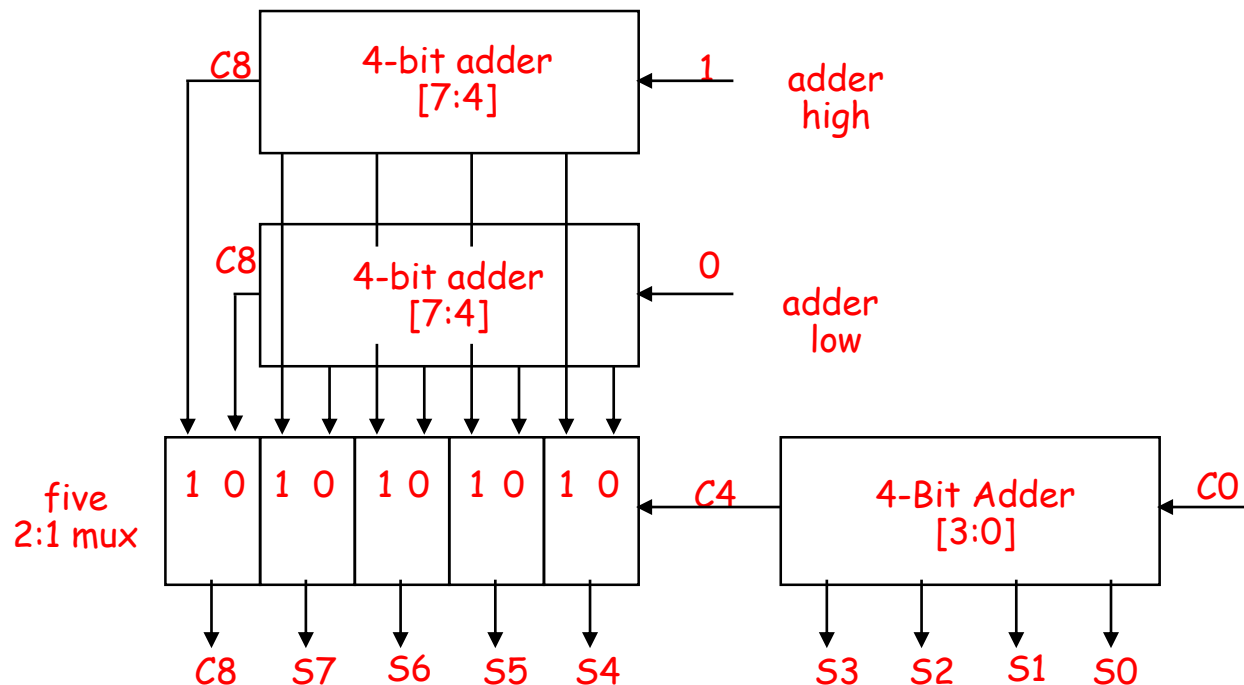
- ✓ Redundant hardware to make carry calculation go faster
 - Compute two high-order sums in parallel while waiting for carry-in
 - One assuming carry-in is 0 and another assuming carry-in is 1
 - Select correct result once carry-in is finally computed



Carry-Lookahead Adder with Cascaded Carry-Lookahead Logic

✓ Carry-lookahead adder

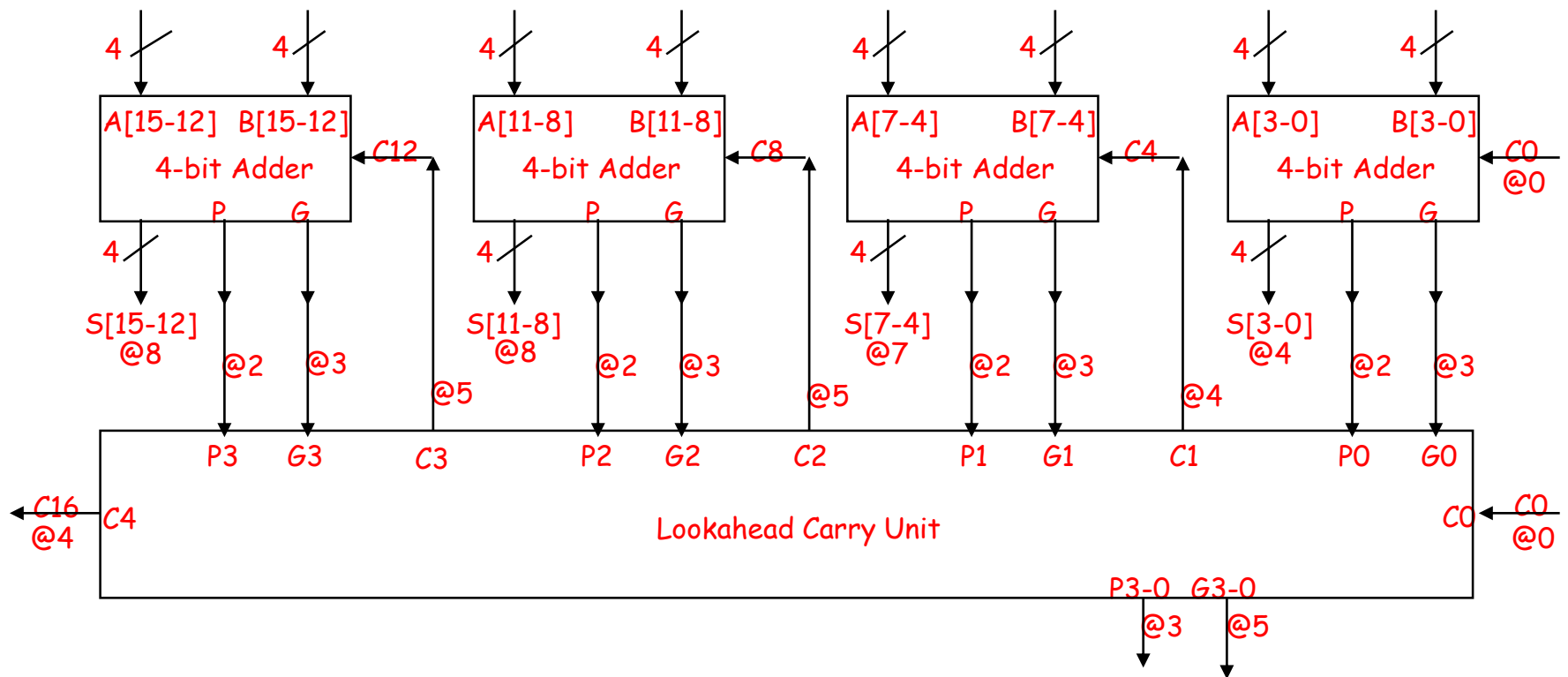- 4 four-bit adders with internal carry lookahead
- Second level carry lookahead unit extends lookahead to 16 bits



Overflow Detection


- ✓ **Overflow** occurs if $n + 1$ bits are required to contain the result from an n -bit addition or subtraction
- ✓ **Overflow** can occur for:
 - Addition of two operands with the same sign
 - Subtraction of operands with different signs
- ✓ Signed number overflow cases with correct result sign

$$\begin{array}{r} 0 \quad 0 \quad 1 \quad 1 \\ + \underline{0} \quad -\underline{1} \quad -\underline{0} \quad +\underline{1} \\ \hline 0 \quad 0 \quad 1 \quad 1 \end{array}$$

- ✓ Detection can be performed by examining the result signs which should match the signs of the top operand

Overflow Detection

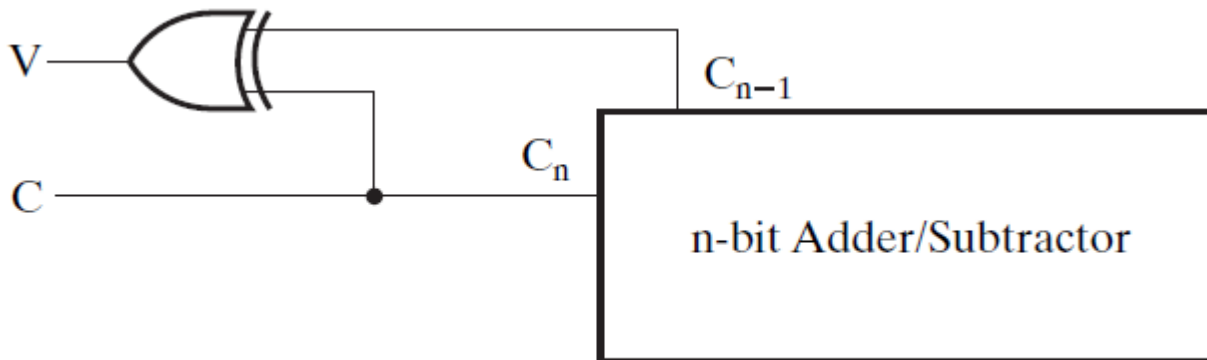- ✓ The simplest way to implement overflow is $V = C_n \oplus C_{n-1}$ where C_n and C_{n-1} are the carries in 2's complement respectively from e to the sign bit:
- $C_n = 0$ and $C_{n-1} = 1$ means $A_n = B_n = 0$ and $S_n = 1$
 - $C_n = 1$ and $C_{n-1} = 0$ means $A_n = B_n = 1$ and $S_n = 0$



Other Arithmetic Functions

- ✓ Convenient to design the functional blocks by *contraction* - removal of redundancy from circuit to which input fixing has been applied
- ✓ Functions
 - Incrementing
 - Decrementing
 - Multiplication by Constant
 - Division by Constant
 - Zero Fill and Extension


Design by Contraction

- ✓ Contraction is a technique for simplifying the logic in a functional block to implement a different function
- ✓ The new function must be realizable from the original function by applying rudimentary functions to its inputs
 - Contraction is treated here only for application of 0s and 1s (not for X and \bar{X})
 - After application of 0s and 1s, equations or the logic diagram are simplified.


Design by Contraction Example: Incrementer

✓ Contraction of a ripple carry adder to incrementer for $n = 3$

- Set B = 001

 


(a)
counting up

 

(b)



- The middle cell can be repeated to make an incrementer with $n > 3$.

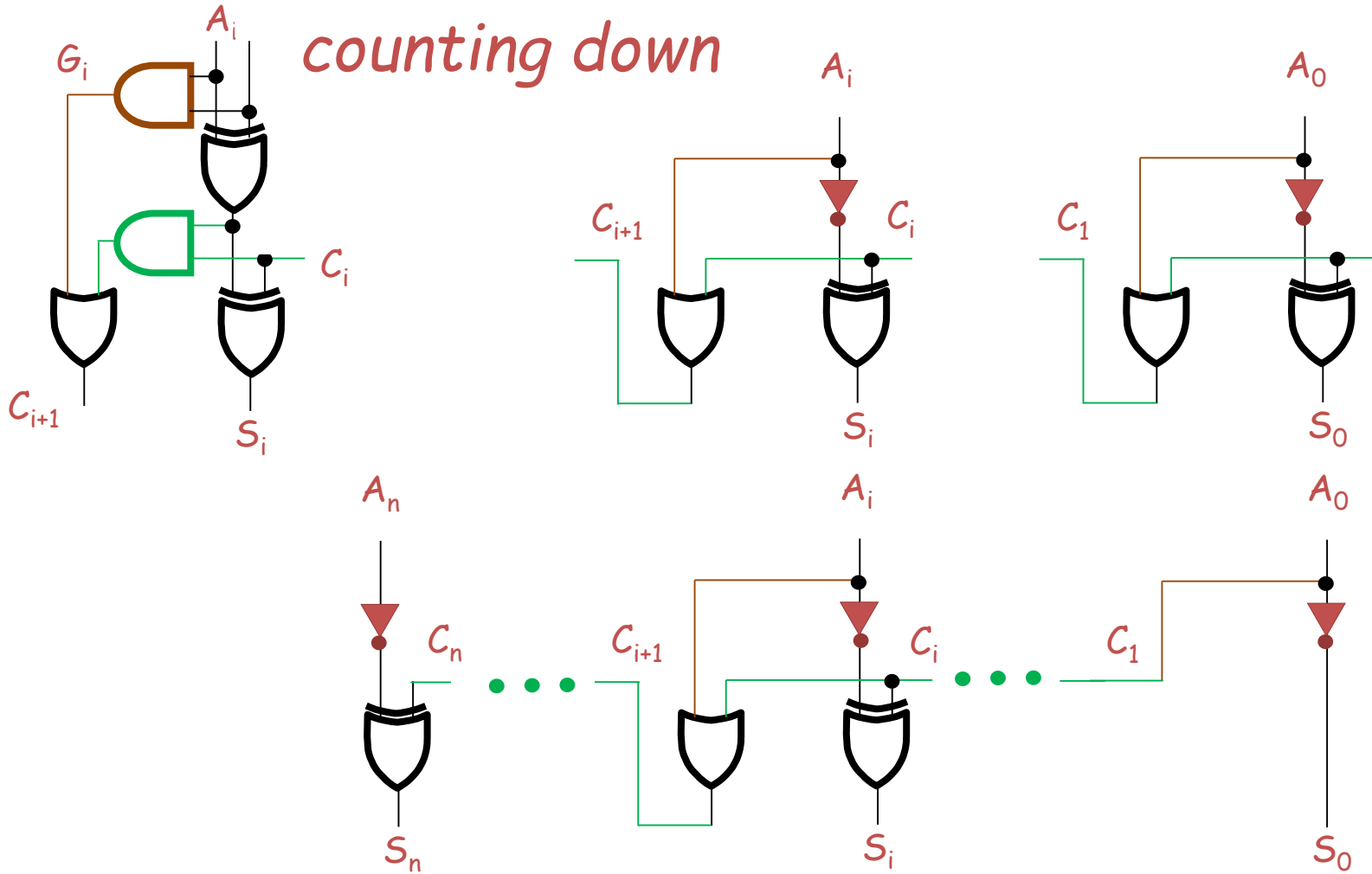Decrementer $D=A-1_{10}$; $D=A+11\cdots111_2$




Multiplication/Division by 2^n

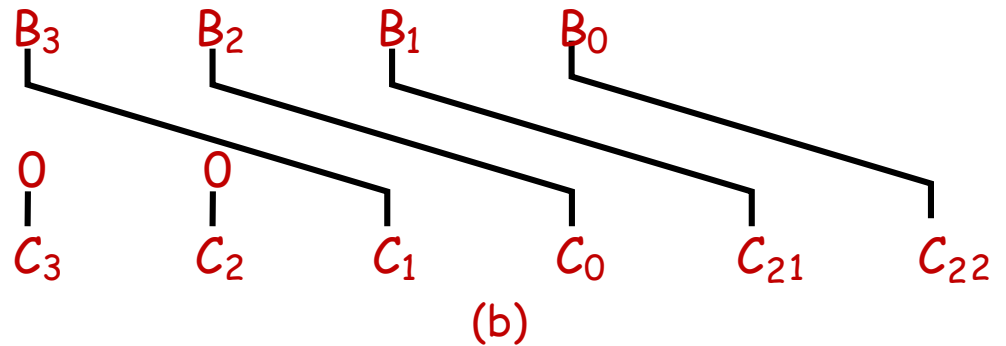 - ✓ (a) Multiplication by 100_2
 - Shift left by 2
- ✓ (b) Division by 100_2
 - Shift right by 2
 - Remainder preserved



Multiplication by a Constant

✓ Multiplication of $B(3:0)$ by 101

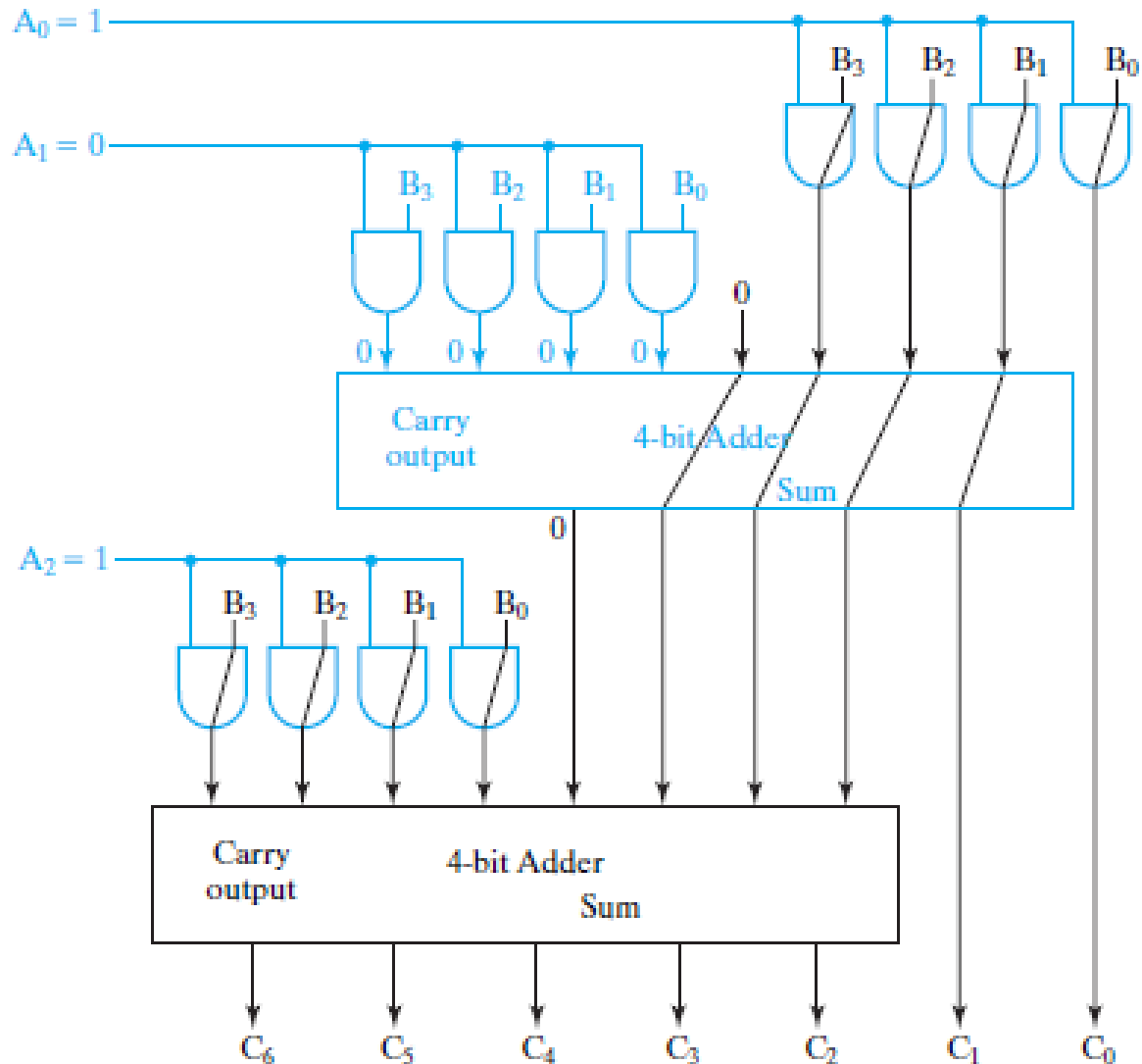

Comparator

- ✓ Used to implement comparison operators ($=$, \neq)

