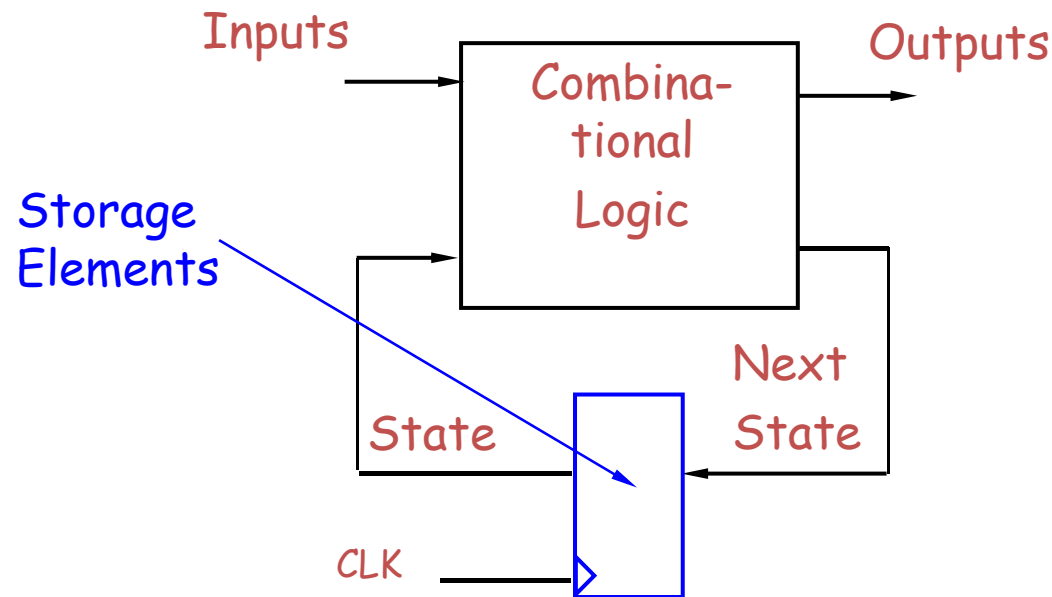


# Sequential Synchronous Circuit Analysis

---

## ✓ General Model

- Current State at time  $t$  is stored in an array of flip-flops.
- Next State at time  $t+1$  is a Boolean function of State and Inputs.
- Outputs at time  $t$  are a Boolean function of State( $t$ ) and (Mealy) of Inputs ( $t$ ).



# Example 1: Analysis

---


- ✓ Input:  $x(t)$
- ✓ Output:  $y(t)$
- ✓ State:  $(A(t), B(t))$
- ✓ What is the Output Function?

$$y(t) = \bar{x}(t)(B(t) + A(t))$$

- ✓ What is the Next State Function?

$$A(t+1) = A(t)x(t) + B(t)x(t)$$

$$B(t+1) = \bar{A}(t)x(t)$$

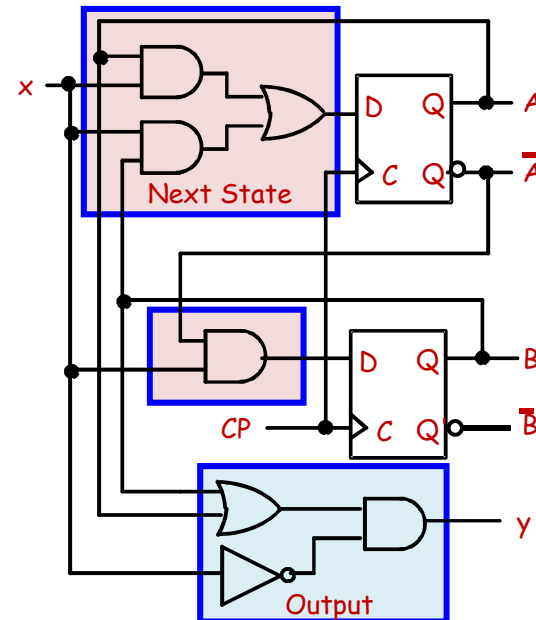

# State Table Characteristics

---

- ✓ **State table** - a multiple variable table with the following four sections:
  - **Present State** - the values of the **state variables** for each allowed state.
  - **Input** - the input combinations allowed.
  - **Next-state** - the value of the **state at time (t+1)** based on the **present state** and the **input**.
  - **Output** - the value of the output as a function of the **present state** and (Mealy) the **input**.
- ✓ **From the viewpoint of a truth table:**
  - the inputs are **Input, Present State**
  - and the outputs are **Output, Next State**

# Example 1: Alternate State Table

$$A(t+1) = A(t) x(t) + B(t) x(t)$$

$$B(t+1) = \bar{A}(t) x(t)$$

$$y(t) = \bar{x}(t) (B(t) + A(t))$$

The time sequence of inputs, outputs, and flip-flop states can be enumerated in a **state table** (sometimes called **transition table**).

$$A+ = A x + B x$$

$$B+ = \bar{A} x$$

$$y = \bar{x} (B + A)$$

**Table 5-2**  
State Table for the Circuit

Present State		Input	Next State		Output
A	B		A	B	
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			

**Table 5-3**  
Second Form of the State Table

Present State	Next State		Output	
	x = 0	x = 1	x = 0	x = 1
AB	AB	AB	y	y
00	00	01	0	0
01	00	11	1	0
10	00	10	1	0
11	00	10	1	0


# Example 1

- ✓ Where in time are inputs, outputs and states defined?


$$A^+ = A x + B x$$

$$B^+ = \bar{A} x$$

$$y = \bar{x} (B + A)$$

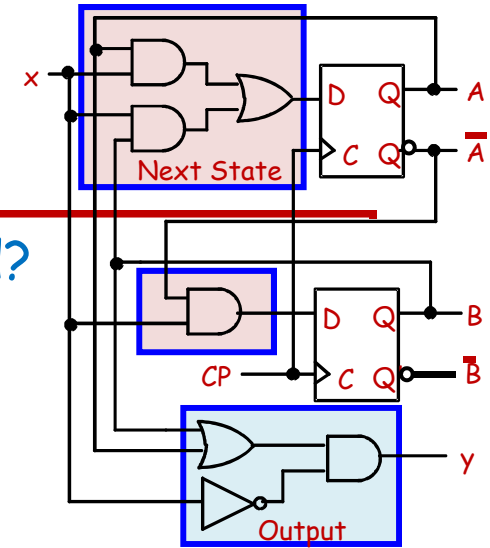

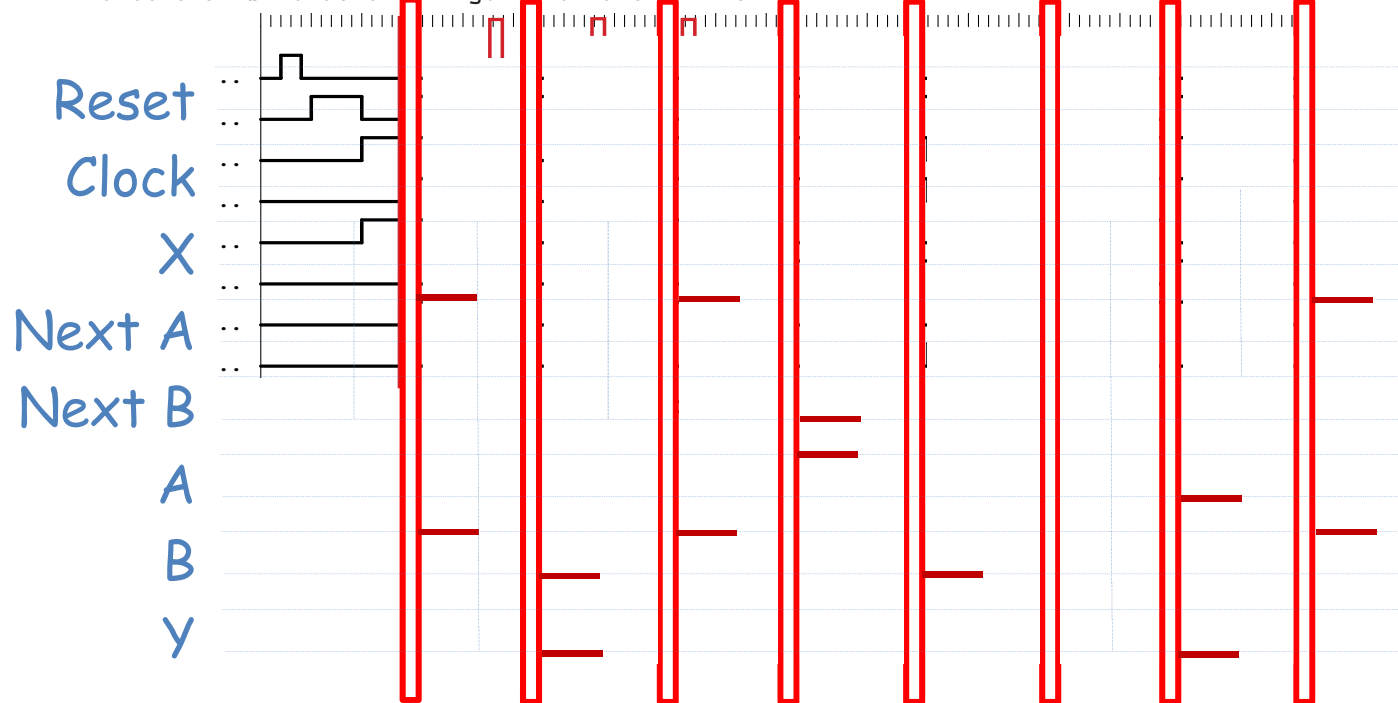Functional Simulation - Fig. 4-18 Mano & Kime



# State Diagrams

---

- ✓ The sequential circuit function can be represented in *graphical form* as a *state diagram* with the following components:
  - A *circle* with the *state name* in it for each state
  - A *directed arc* from the *Present State* to the *Next State* for each state transition
  - A *label* on each *directed arc* with the *Input* values which causes the *state transition*, and
  - A *label*:
    - On each *circle* with the *output* value produced:  
**Moore** type
    - or
    - On each *directed arc* with the *output* value produced:  
**Mealy** type.


# Example 1: State Diagram

- ✓ Diagram gets confusing for large circuits
- ✓ For small circuits, usually easier to understand than the state table

$$A+ = A x + B x$$

$$B+ = \bar{A} x$$

$$y = \bar{x} (B + A)$$

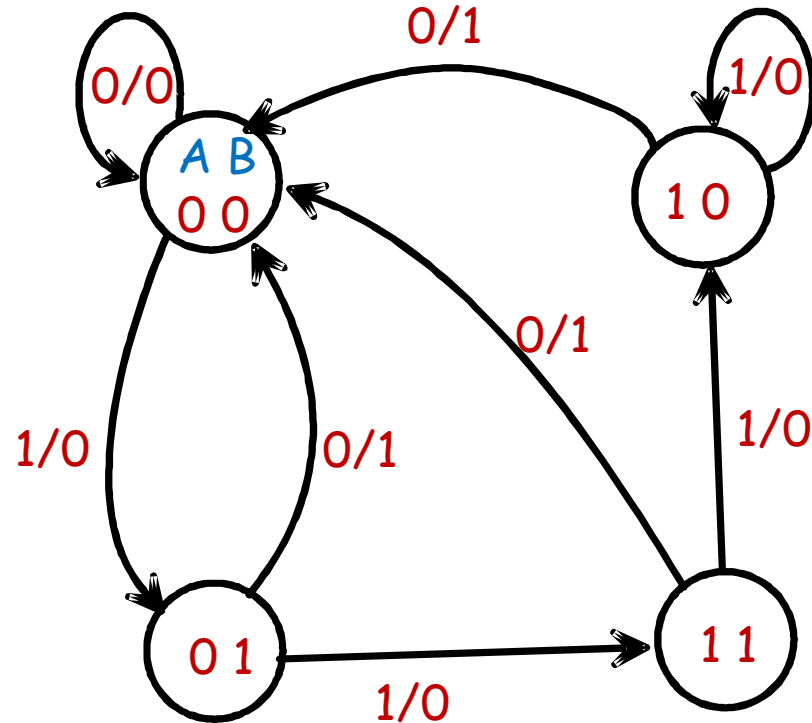

1/0 : means input  $x = 1$   
output  $y = 0$


Mealy

Table 5-3  
Second Form of the State Table

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
$AB$	$AB$	$AB$	$y$	$y$
00	00	01	0	0
01	00	11	1	0
10	00	10	1	0
11	00	10	1	0

# Analysis with JK Flip-Flops

---

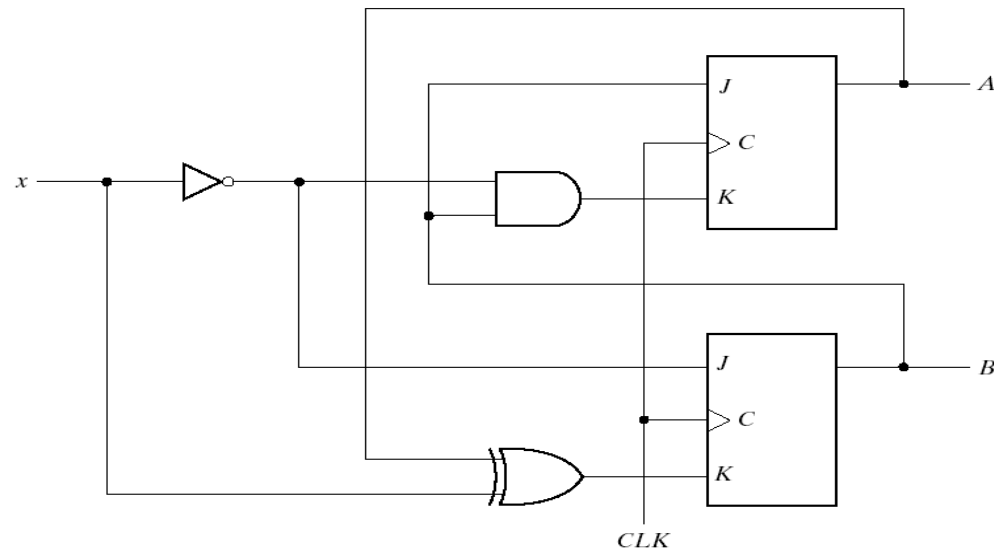

$$J_A = B \quad K_A = B \bar{x}$$

$$J_B = \bar{x} \quad K_B = \bar{A}x + A\bar{x} = A \oplus x$$



# Analysis with JK Flip-Flop

- ✓ The circuit can be specified by the flip-flop input equations:

$$J_A = B \quad K_A = B \bar{x}$$

$$J_B = \bar{x} \quad K_B = \bar{A}x + A\bar{x} = A \oplus x$$

**Table 5-4**  
*State Table for Sequential Circuit with JK Flip-Flops*

Present State		Input	Next State		Flip-Flop Inputs			
A	B		A	B	$J_A$	$K_A$	$J_B$	$K_B$
0	0	0						
0	0	1						
0	1	0						
0	1	1						
1	0	0						
1	0	1						
1	1	0						
1	1	1						

# Analysis with JK Flip-Flops

---

$$A^+ = J\bar{A} + \bar{K}A$$
$$B^+ = J\bar{B} + \bar{K}B$$

$$J_A = B$$

$$K_A = B\bar{x}$$

$$J_B = \bar{x}$$

$$K_B = \bar{A}x + A\bar{x} = A \oplus x$$

- ✓ Substituting the values of  $J_A$  and  $K_A$  from the input equations, we obtain the state equation for A:

$$A = B\bar{A} + (\overline{B\bar{x}})A = \bar{A}B + A\bar{B} + Ax$$

- ✓ The state equation provides the bit values for the column under next state of A in the state table. Similarly, the state equation for flip-flop B can be derived from the characteristic equation by substituting the values of  $J_B$  and  $K_B$ :

$$B = \bar{x}\bar{B} + (\overline{A \oplus x})B = \bar{B}\bar{x} + ABx + \bar{A}B\bar{x}$$

# Analysis with JK Flip-Flops

- ✓ The state diagram of the sequential circuit is:

$$A = B\bar{A} + (\overline{Bx})A = \bar{A}B + A\bar{B} + Ax$$

$$B = \bar{x}\bar{B} + (\overline{A \oplus x})B = \bar{B}\bar{x} + ABx + \bar{A}B\bar{x}$$

**Table 5-4**  
*State Table for Sequential Circuit with JK*

Present State		Input	Next State	
A	B	x	A	B
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		


Moore

# Analysis With T Flip-Flops

---

- ✓ Characteristic equation:

$$Q = T \oplus Q$$

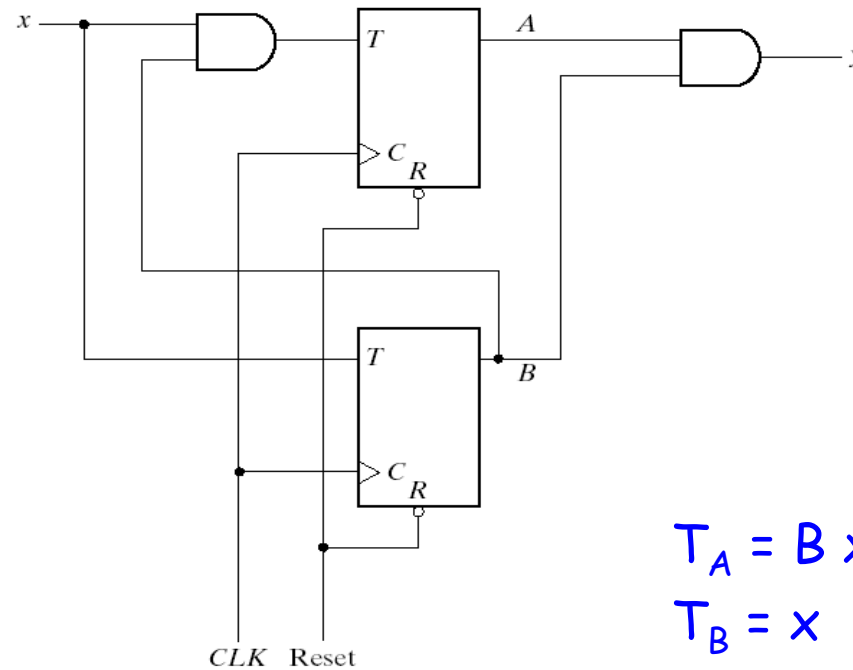

$$T_A = B x$$

$$T_B = x$$

$$y = A B$$

Moore

# Analysis With T Flip-Flops

- ✓ Consider the previous sequential circuit. It has two flip-flops A and B, one input x, and one output y. It can be described algebraically by two input equations and an output equation:

$$T_A = B x$$

$$T_B = x$$

$$y = A B$$

$$A = (\overline{Bx})A + (Bx)\overline{A}$$

$$= A\overline{B} + A\overline{x} + \overline{A}Bx$$

$$B = x \oplus B$$

**Table 5-5**

*State Table for Sequential Circuit with T Flip-Flops*

Present State		Input <u>x</u>	Next State		Output <u>y</u>
A	B		A	B	
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			

# Analysis With T Flip-Flops

---

- ✓ Characteristic equation:

$$Q(t + 1) = T \oplus Q$$

**Table 5-5**  
*State Table for Sequential Circuit with T Flip-Flops*

Present State		Input	Next State		Output
A	B		A	B	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	1	0
0	1	1	1	0	0
1	0	0	1	0	0
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	1

# Sequential Circuit Analysis

---

✓ Initialization: reset to (0, 0, 0)


✓ Equations:

$$A = B C$$

$$B = \bar{B} C + B \bar{C}$$

$$C = \bar{A} \bar{C}$$

$$Z = A$$

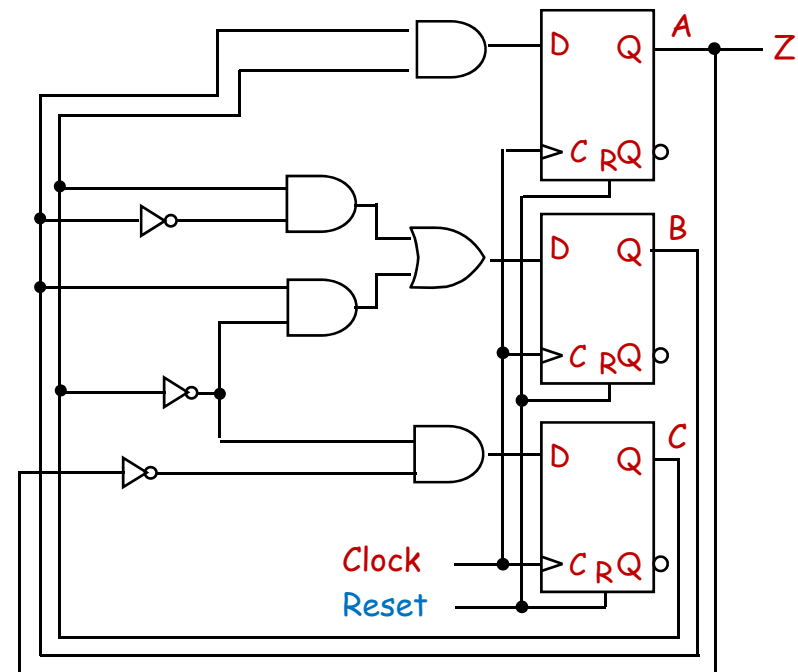

Moore

## Example 2: State Table

---


$$A = B C$$
$$B = \bar{B} C + B \bar{C}$$
$$C = \bar{A} \bar{C}$$

$$Z = A$$

$A \ B \ C$ <small>(<math>t</math>)</small>	$A' \ B' \ C'$ <small>(<math>t+1</math>)</small>	$Z$
0 0 0	0 0 1	0
0 0 1	0 1 0	0
0 1 0	0 1 1	0
0 1 1	1 0 0	0
1 0 0	0 0 0	1
1 0 1	0 1 0	1
1 1 0	0 1 0	1
1 1 1	1 0 0	1



## Example 2: State Diagram

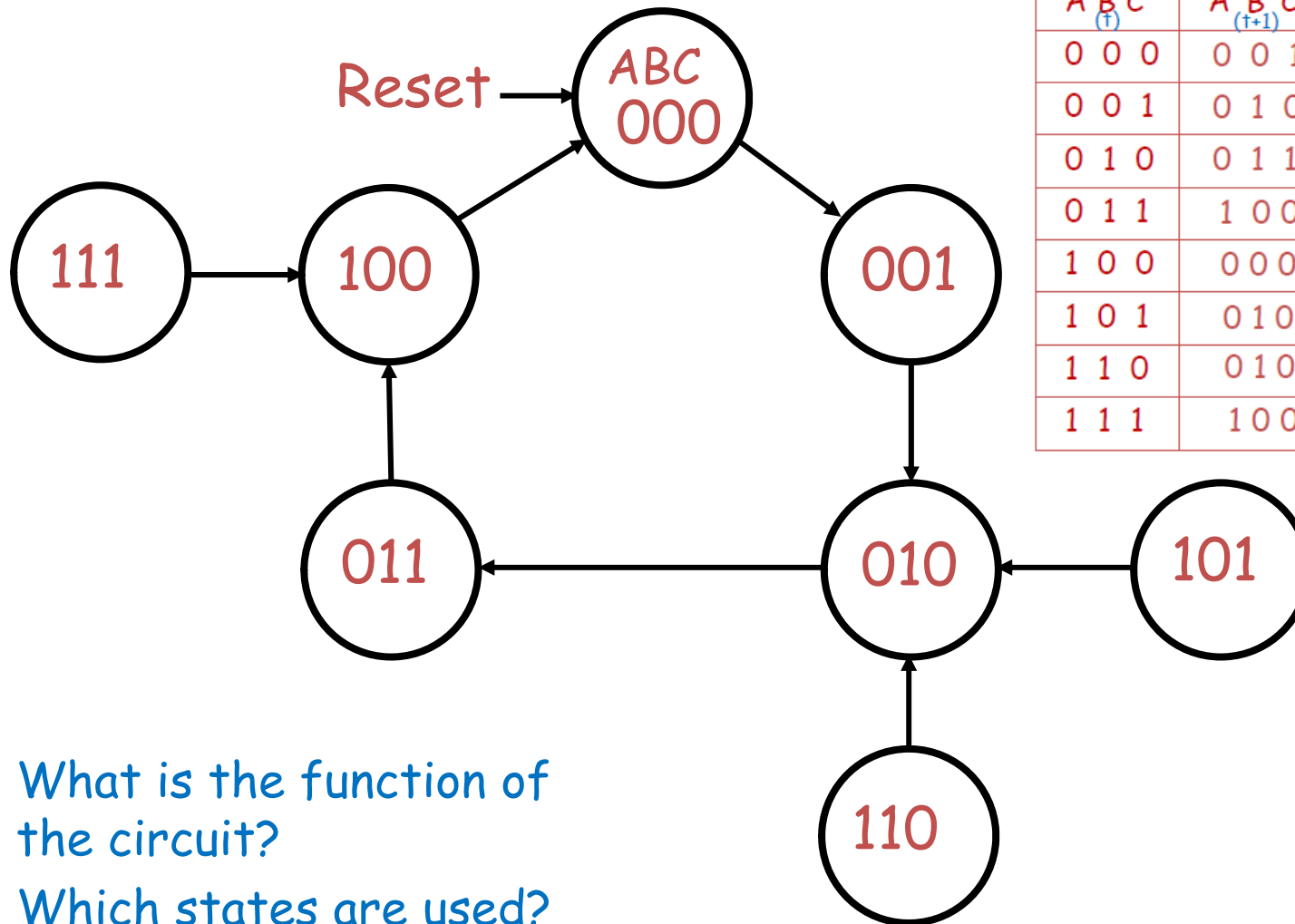


A B C (t)	A' B' C' (t+1)	Z
0 0 0	0 0 1	0
0 0 1	0 1 0	0
0 1 0	0 1 1	0
0 1 1	1 0 0	0
1 0 0	0 0 0	1
1 0 1	0 1 0	1
1 1 0	0 1 0	1
1 1 1	1 0 0	1

- ✓ What is the function of the circuit?
- ✓ Which states are used?

Moore

# Analysis with D Flip-Flop

---

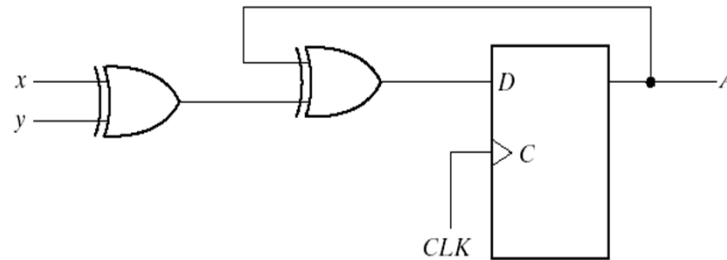

- ✓ The circuit we want to analyze is described by the input equation

$$D_A = A \oplus x \oplus y$$

- ✓ The  $D_A$  symbol implies a D flip-flop with output  $A$ . The  $x$  and  $y$  variables are the inputs to the circuit. No output equations are given, so the output is implied to come from the output of the flip-flop.

Moore

# Analysis with D Flip-Flop

---

- ✓ The binary numbers under  $A \times y$  are listed from 000 through 111. The next state values are obtained from the state equation

$$D_A = A \oplus x \oplus y$$

- ✓ The state diagram consists of two circles-one for each state

Present state	Inputs		Next state
$A$	$x$	$y$	$A$
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

# Equivalent State Definitions


---

- ✓ Two states are **equivalent** if their response for **each possible input sequence** is an identical output sequence.
- ✓ Alternatively, two states are equivalent if **their outputs** produced for each **input symbol** is identical and their **next states** for each **input symbol** are the same or equivalent.
- ✓ Two states that are not equivalent are **distinguishable**


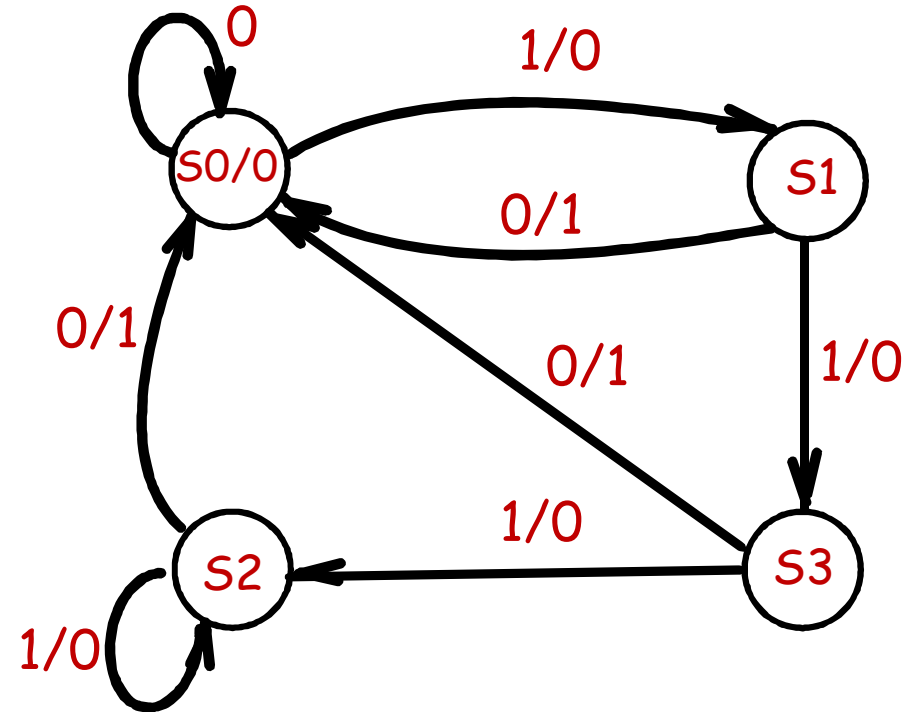
# Equivalent State Example

---


- ✓ For states  $S_3$  and  $S_2$ ,
  - the output for input 0 is 1 and input 1 is 0, and
  - the next state for input 0 is  $S_0$  and for input 1 is  $S_2$ .
  - states  $S_3$  and  $S_2$  are **equivalent**.



# Equivalent State Example

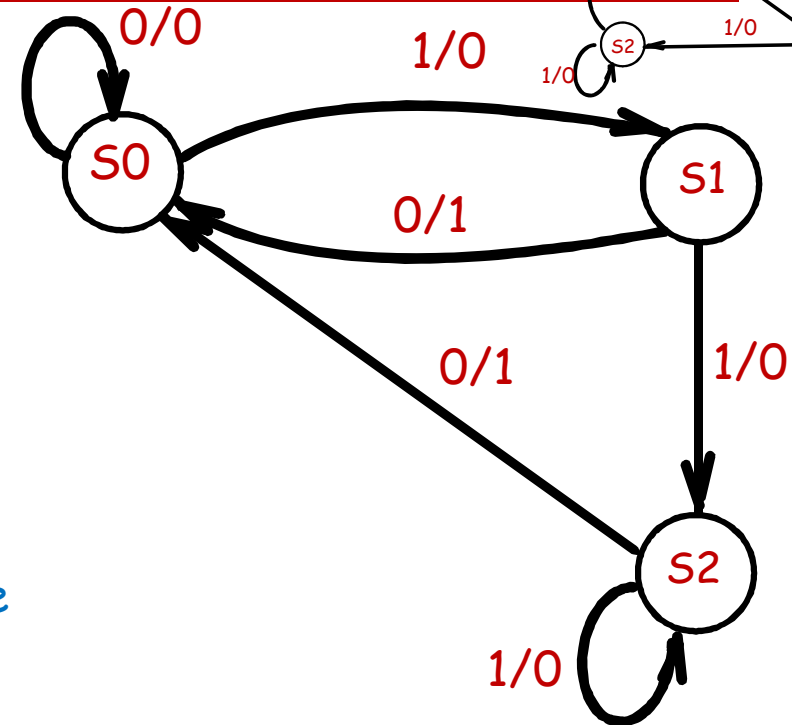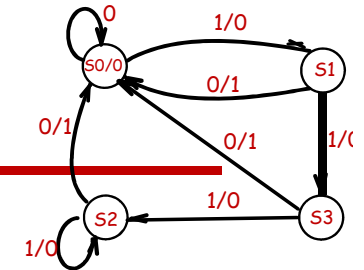

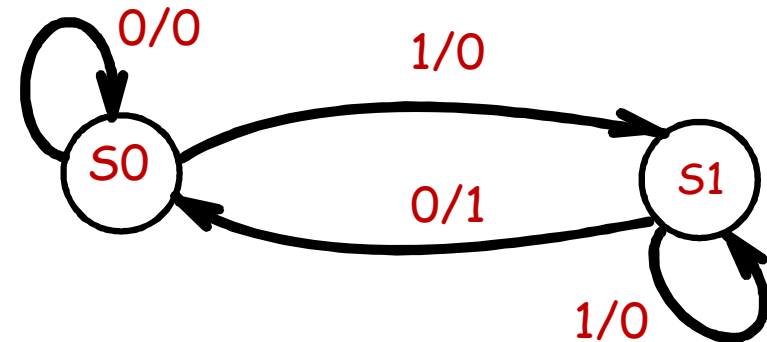- ✓ Replacing S3 and S2 by a single state gives state diagram:
  
- ✓ Examining the new diagram, states S1 and S2 are equivalent since
  - their outputs for input 0 is 1 and input 1 is 0, and
  - their next state for input 0 is S0 and for input 1 is S2,
  
- ✓ Replacing S1 and S2 by a single state gives state diagram:



# Moore and Mealy Models


---

- ✓ Sequential Circuits or Sequential Machines are also called **Finite State Machines (FSMs)**.
- ✓ Two formal models exist:
  - **Moore Model**
    - Named after E.F. Moore
    - Outputs are a function **ONLY of states**
    - Usually specified on the states.
  - **Mealy Model**
    - Named after G. H. Mealy
    - Outputs are a function of **inputs AND states**
    - Usually specified on the state transition arcs.

# Moore and Mealy Example Diagrams & Tables


- ✓ Mealy Model State Diagram maps inputs and state to outputs

Present State	Next State		Output	
	x=0	x=1	x=0	x=1
0	0	1	0	0
1	0	1	0	1

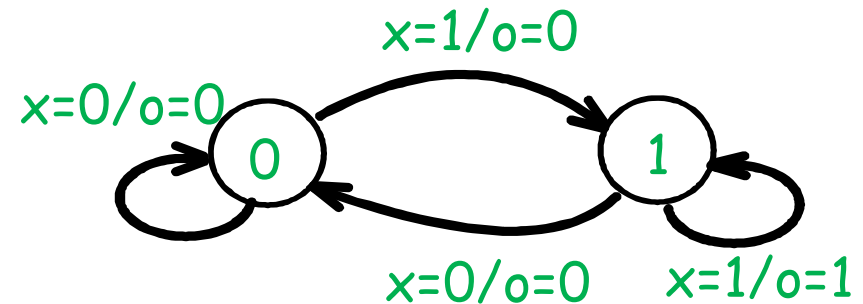

- ✓ Moore Model State Diagram maps states to outputs

Present State	Next State		Output
	x=0	x=1	
0	0	1	0
1	0	2	0
2	0	2	1

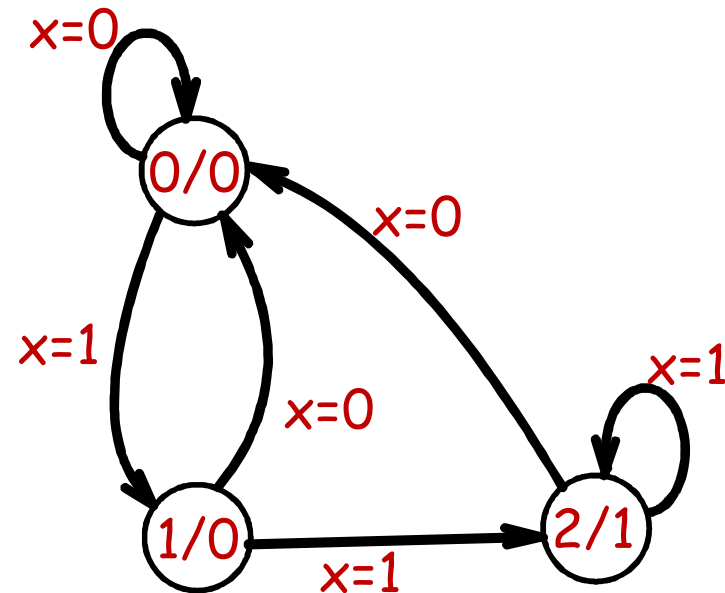



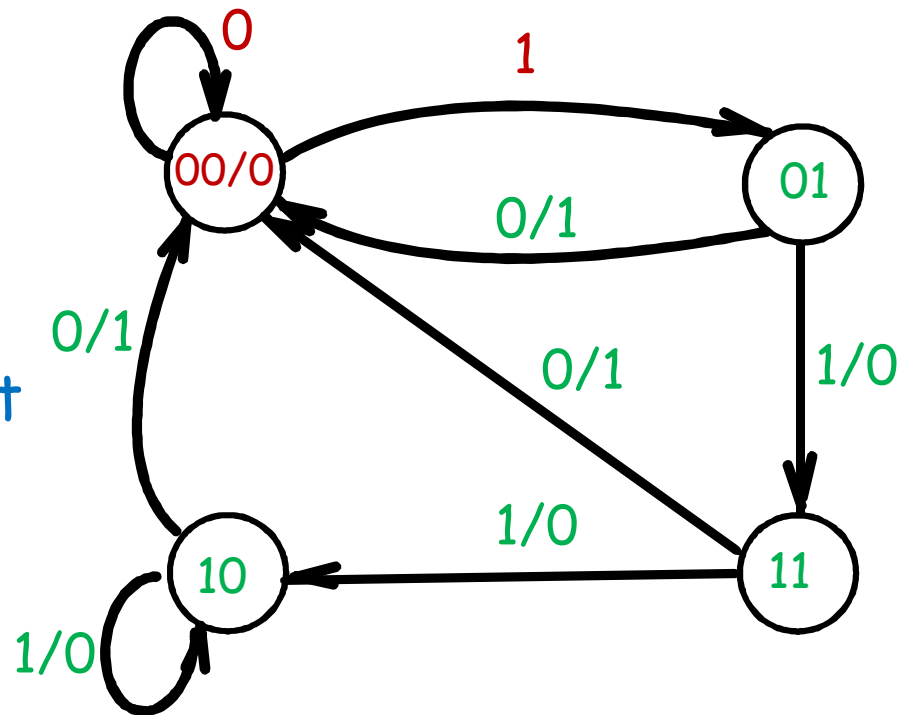
# Mixed Moore and Mealy Outputs

---

- ✓ In real designs, some outputs may be Moore type and other outputs may be Mealy type.
- ✓ Example: Figure can be modified to illustrate this
  - State 00: Moore
  - States 01, 10, and 11: Mealy
- ✓ This simplifies output specification




# State Reduction

---


Example :

	next state											
state	a	a	b	c	d	e	f	f	g	f	g	a
input	0	1	0	1	0	1	1	0	1	0	0	
output	0	0	0	0	0	1	1	0	1	0	0	
	$t_0$	$t_1$	$t_2$	$t_3$	...							

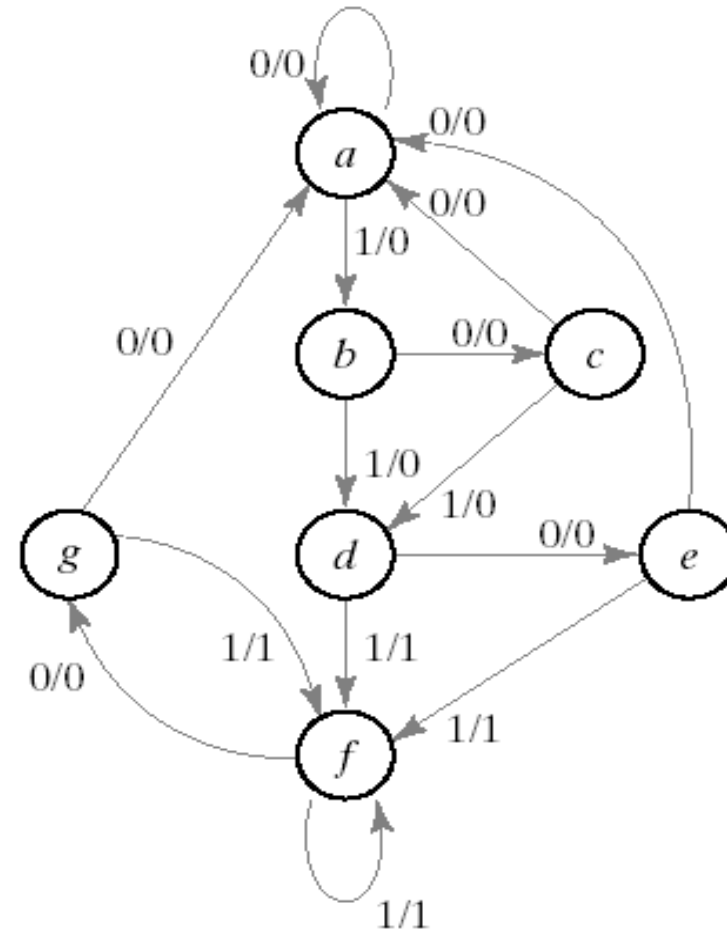

# State Reduction

- ✓ We now proceed to reduce the number of states for this example. First, we need the **state table**; it is more convenient to apply procedures for state reduction using a table rather than a diagram. The state table of the circuit is listed in Table 5-6 and is obtained directly from the state diagram.

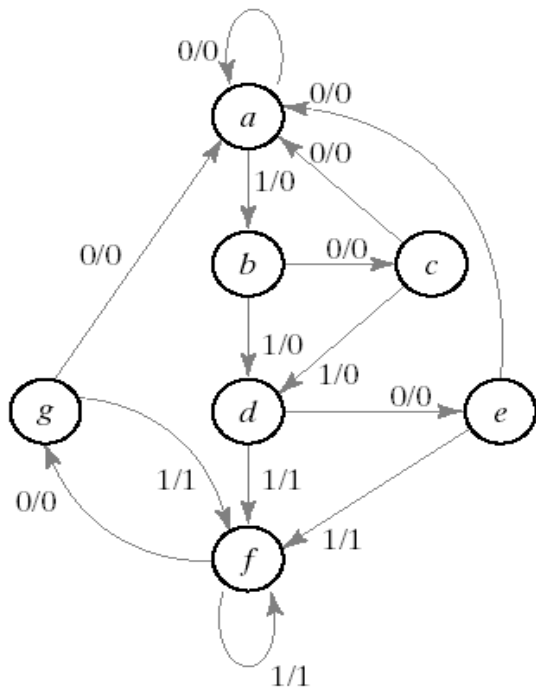

**Table 5-6**  
*State Table*

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
<i>a</i>	<i>a</i>	<i>b</i>	0	0
<i>b</i>	<i>c</i>	<i>d</i>	0	0
<i>c</i>	<i>a</i>	<i>d</i>	0	0
<i>d</i>	<i>e</i>	<i>f</i>	0	1
<i>e</i>	<i>a</i>	<i>f</i>	0	1
<i>f</i>	<i>g</i>	<i>f</i>	0	1
<i>g</i>	<i>a</i>	<i>f</i>	0	1

# State Reduction

- ✓ States *g* and *e* are two such states: they both go to states *a* and *f* and have outputs of 0 and 1 for  $x=0$  and  $x=1$ , respectively. Therefore, states *g* and *e* are equivalent and one of these states can be removed. The procedure of removing a state and replacing it by its equivalent is demonstrated in Table 5-7. The row with present *g* is removed and state *g* is replaced by state *e* each time it occurs in the next-state columns.

**Table 5-7**  
*Reducing the State Table*

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
<i>a</i>	<i>a</i>	<i>b</i>	0	0
<i>b</i>	<i>c</i>	<i>d</i>	0	0
<i>c</i>	<i>a</i>	<i>d</i>	0	0
<i>d</i>	<i>e</i>	<i>f</i>	0	1
<i>e</i>	<i>a</i>	<i>f</i>	0	1
<i>f</i>	<i>e</i>	<i>f</i>	0	1

# State Reduction

- ✓ Present state **f** now has next states **e** and **f** and outputs 0 and 1 for  $x=0$  and  $x=1$ , respectively. The same next states and outputs appear in the row with present state **d**. Therefore, states **f** and **d** are equivalent and state **f** can be removed and replaced by **d**. The final reduced table is shown in Table 5-8. The state diagram for the reduced table consists of only five states.

**Table 5-8**  
*Reduced State Table*


Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
<i>a</i>	<i>a</i>	<i>b</i>	0	0
<i>b</i>	<i>c</i>	<i>d</i>	0	0
<i>c</i>	<i>a</i>	<i>d</i>	0	0
<i>d</i>	<i>e</i>	<i>d</i>	0	1
<i>e</i>	<i>a</i>	<i>d</i>	0	1

# State Reduction

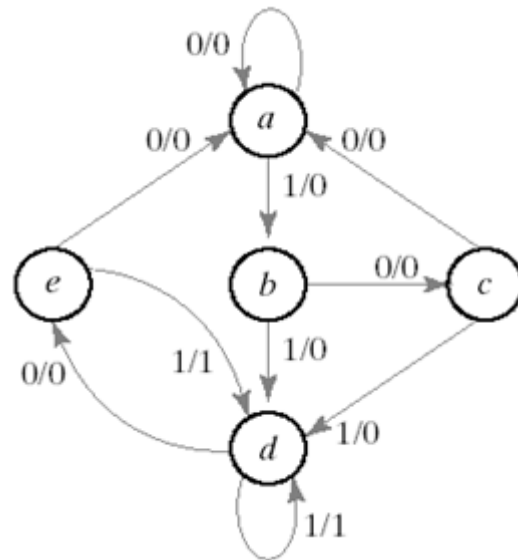Example :


state a a b c d e f f g f g a  
 input 0 1 0 1 0 1 1 0 1 0 0  
 output 0 0 0 0 0 1 1 0 1 0 0

state a a b c d e d d e d e a  
 output 0 0 0 0 0 1 1 0 1 0 0



$(e, g) \Rightarrow e$


$(d, f) \Rightarrow d$

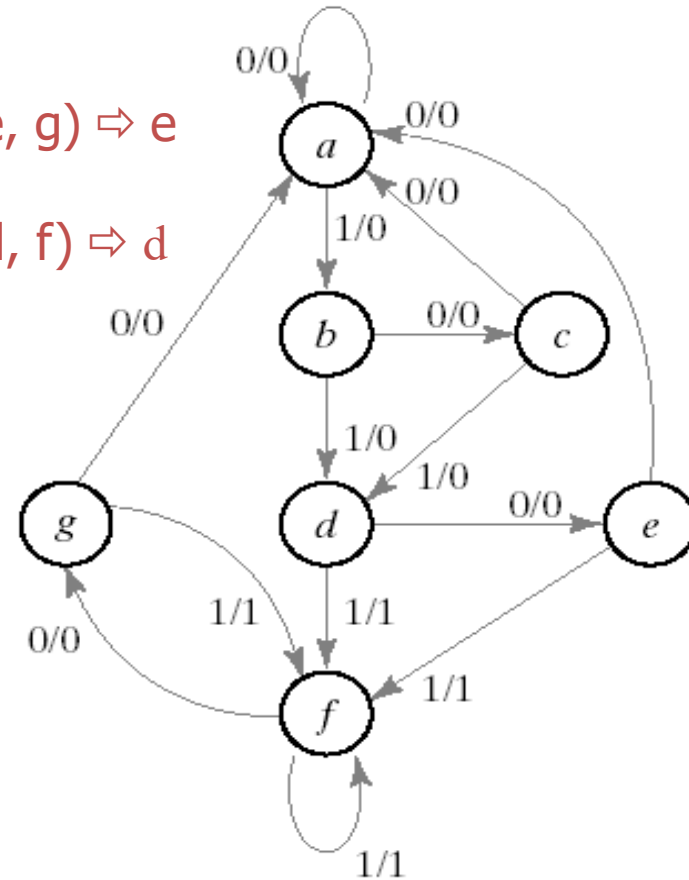

# State Assignment

**Table 5-9**  
Three Possible Binary State Assignments

State	Assignment 1	Assignment 2	Assignment 3
	Binary	pseudo Gray code	One-hot
<i>a</i>	000	000	00001
<i>b</i>	001	001	00010
<i>c</i>	010	011	00100
<i>d</i>	011	010	01000
<i>e</i>	100	110	10000

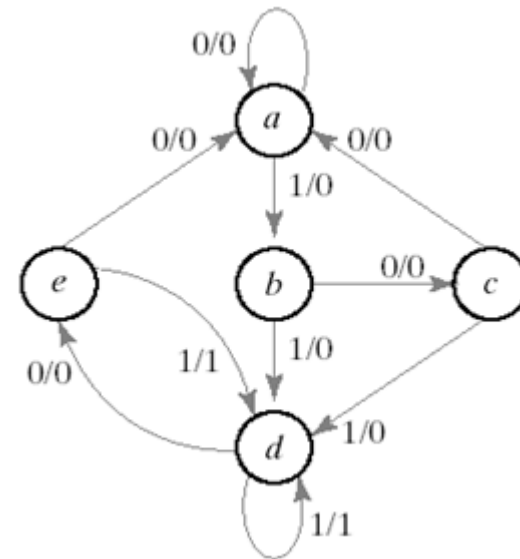

**Table 5-10**  
Reduced State Table with Binary Assignment 1

Present State	Next State		Output	
	<i>x</i> = 0	<i>x</i> = 1	<i>x</i> = 0	<i>x</i> = 1
000	000	001	0	0
001	010	011	0	0
010	000	011	0	0
011	100	011	0	1
100	000	011	0	1