

# Counters

---



- ✓ **Counters** are sequential circuits which "count" through a specific state sequence.
  - They can **count up**, **count down**, or **count through other fixed sequences**.
- ✓ Two distinct types are in common usage:
  - **Ripple Counters**
    - Clock connected to the flip-flop clock input on the LSB bit flip-flop
    - For all other bits, a flip-flop output is connected to the clock input, thus circuit is not truly synchronous!
    - Output change is delayed more for each bit toward the MSB.
    - Resurgent because of low power consumption
  - **Synchronous Counters**
    - Clock is directly connected to the flip-flop clock inputs
    - Logic is used to implement the desired state sequencing

# Ripple Counter

---
 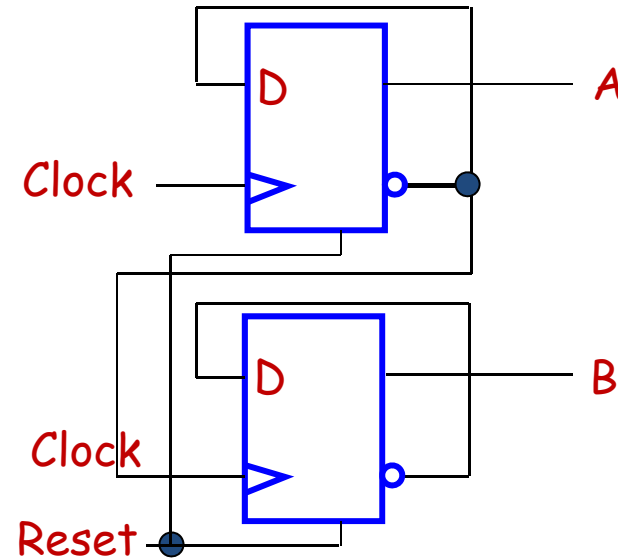
## ✓ How does it work?


- When there is a **positive edge** on the clock input of A, **A complements**
- The **clock input** for flip-flop B is the **complemented output** of flip-flop A
- When flip **A changes from 1 to 0**, there is a **positive edge** on the clock input of B causing **B to complement**


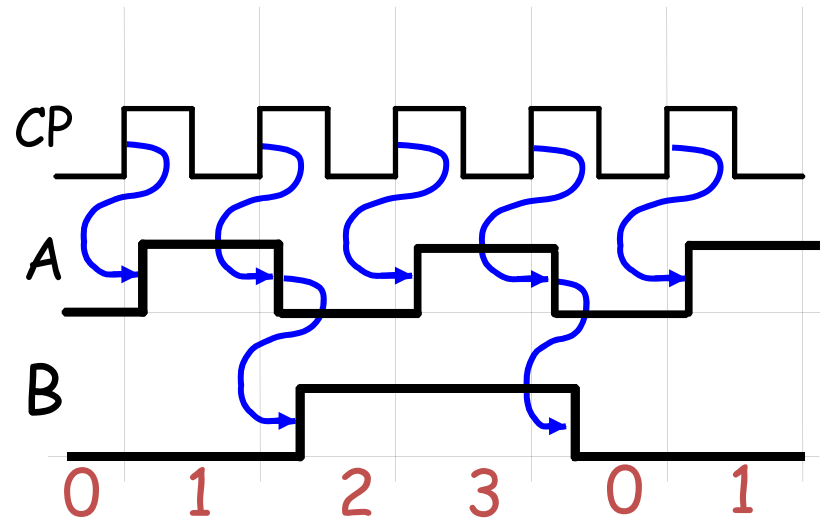
## Ripple Counter (continued)

---

- ✓ The arrows show the cause-effect relationship from the prior slide



- ✓ The corresponding sequence of states  $\Rightarrow$

$$(B,A) = (0,0), (0,1), (1,0), (1,1), (0,0), (0,1), \dots$$

- ✓ Each additional bit, C, D, ... behaves like bit B, changing half as frequently as the bit before it.
- ✓ For 3 bits:  $(C,B,A) = (0,0,0), (0,0,1), (0,1,0), (0,1,1), (1,0,0), (1,0,1), (1,1,0), (1,1,1), (0,0,0), \dots$

## Ripple Counter (continued)


---

- ✓ These circuits are called **ripple counters** because each edge sensitive transition (positive in the example) causes a change in the **next flip-flop's state**.
- ✓ The **changes ripple upward** through the chain of flip-flops, i. e., each transition occurs after a clock-to-output **delay** from the stage before.
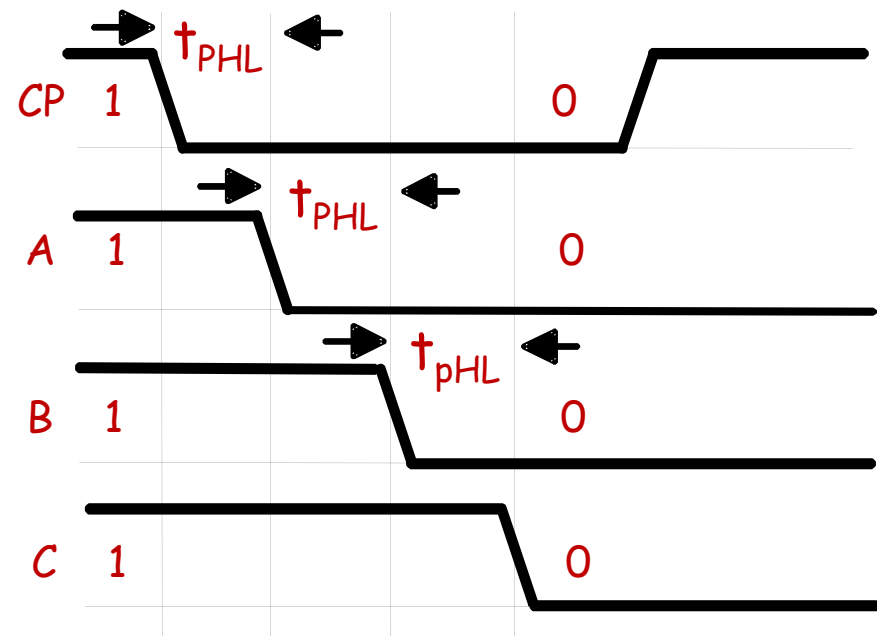
## Ripple Counter (continued)

✓ Starting with  $C = B = A = 1$ , equivalent to  $(C, B, A) = 7$  base 10, the next clock increments the count to  $(C, B, A) = 0$  base 10. In fine timing detail:


- The clock to output delay  $t_{PHL}$  causes an increasing delay from clock edge for each stage transition.
- Thus, the count "ripples" from least to most significant bit.
- For  $n$  bits, total worst case delay is  $n t_{PHL}$ .


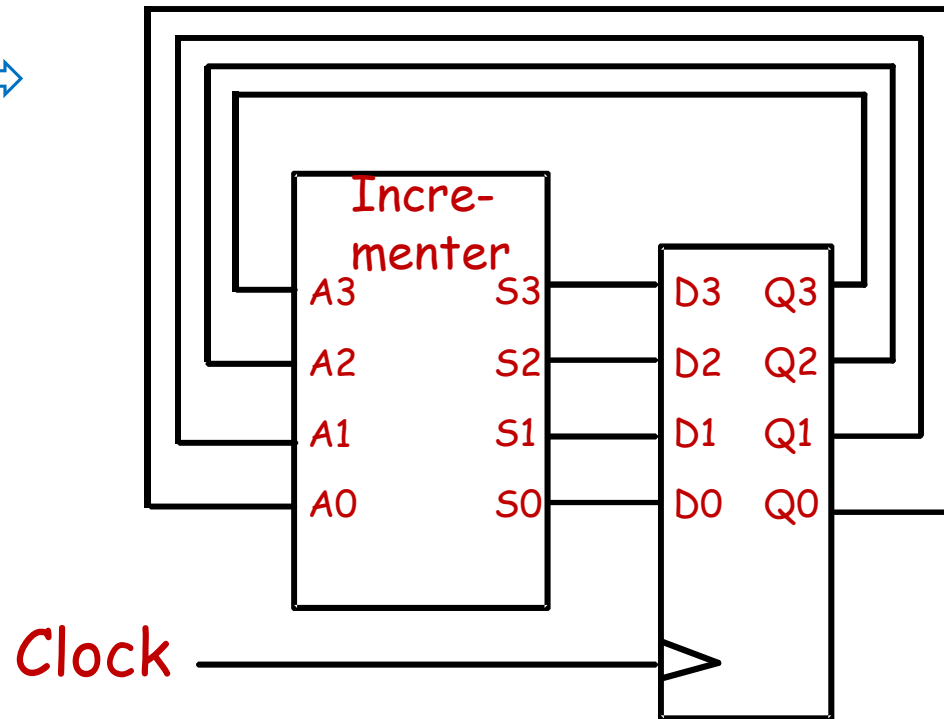
# Synchronous Counters

---

- ✓ To eliminate the "ripple" effects, use a common clock for each flip-flop and a combinational circuit to generate the next state.
- ✓ For an up-counter, use an **incrementer** ⇒



# Synchronous Counters (continued)

✓ Internal details  $\Rightarrow$  Incrementer

✓ Internal Logic


- XOR complements each bit
- AND chain causes complement of a bit if all bits toward LSB from it equal 1

✓ Count Enable

- Forces all outputs of AND chain to 0 to "hold" the state

✓ Carry Out

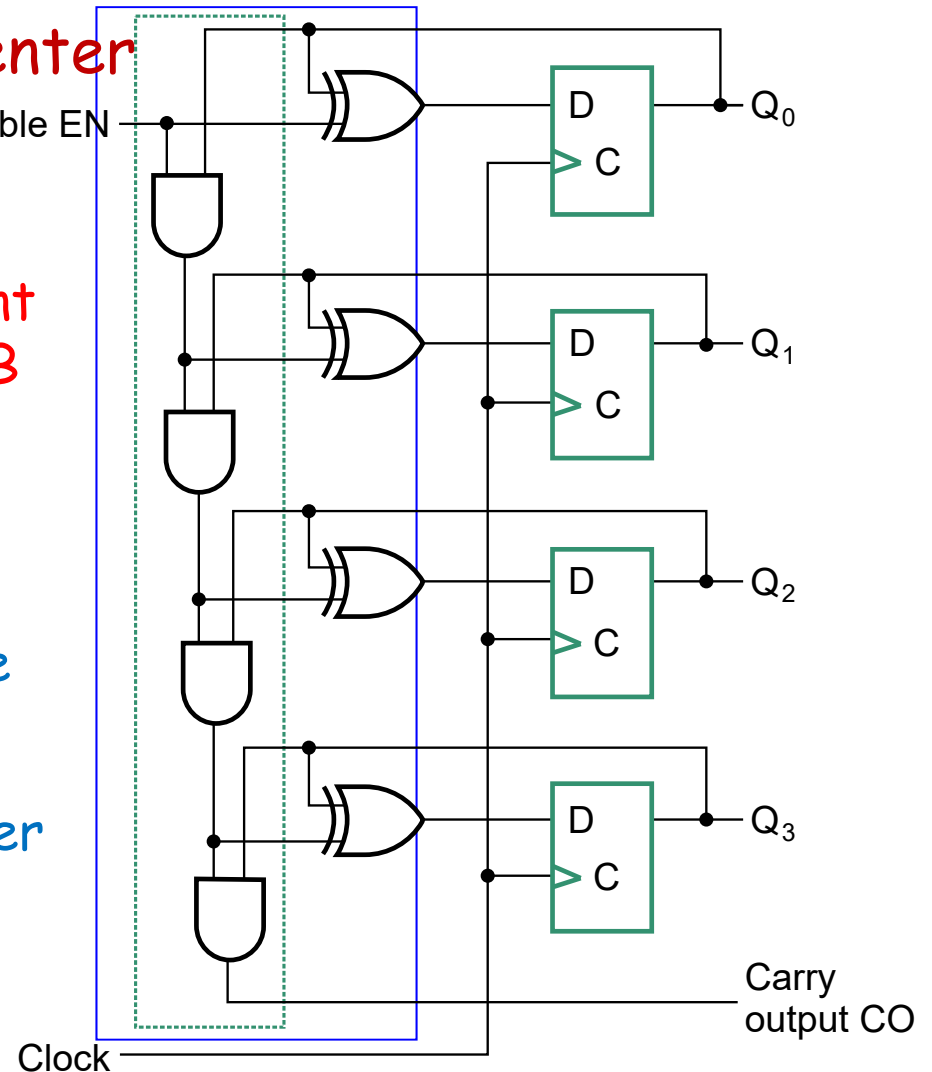
- Added as part of incrementer
- Connect to Count Enable of additional 4-bit counters to form larger counters




(a) Logic Diagram-Serial Gating
 
# Synchronous Counters (continued)

- ✓ Carry chain
  - series of AND gates through which the carry "ripples"
  - Yields long path delays
  - Called *serial gating*
- ✓ Replace AND carry chain with ANDs  $\Rightarrow$  in parallel
  - Reduces path delays
  - Called *parallel gating*
  - Like carry lookahead
  - Lookahead can be used on COs and ENs to prevent long paths in large counters
- ✓ Symbol for Synchronous Counter



Symbol

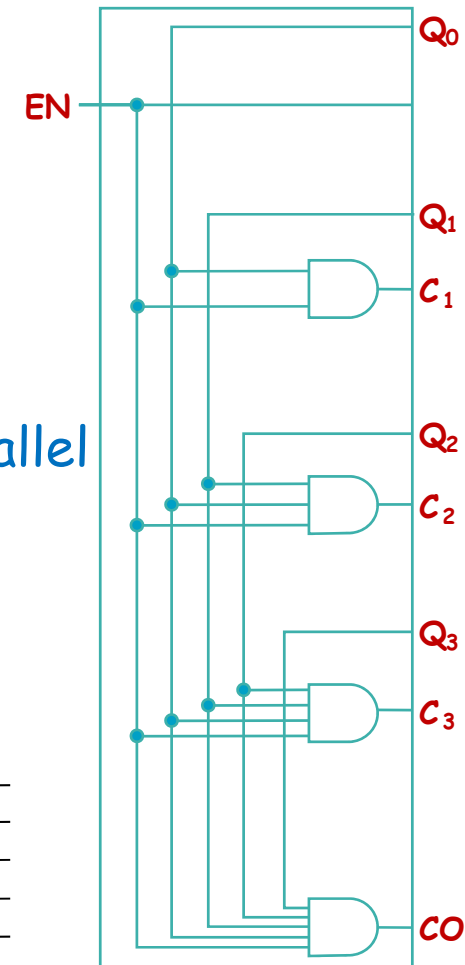

Logic Diagram-Parallel Gating



# Other Counters

---

## ✓ Counters:

- **Down Counter** - counts downward instead of upward
- **Up-Down Counter** - counts up or down depending on value a control input such as **Up/Down**
- **Parallel Load Counter** - Has parallel load of values available depending on control input such as Load


## ✓ Divide-by-n (Modulo n) Counter

- Count is remainder of division by  $n$ ;  $n$  may not be a power of 2
- Count is arbitrary sequence of  $n$  states specifically designed state-by-state
- Includes modulo 10 which is the **BCD counter**

# Counter with Parallel Load

- ✓ Add path for input data
  - enabled for Load = 1
- ✓ Add logic to:
  - disable count logic for Load = 1
  - disable feedback from outputs for Load = 1
  - enable count logic for Load = 0 and Count = 1
- ✓ The resulting function table:

Load	Count	Action
0	0	Hold Stored Value
0	1	Count Up Stored Value
1	X	Load D

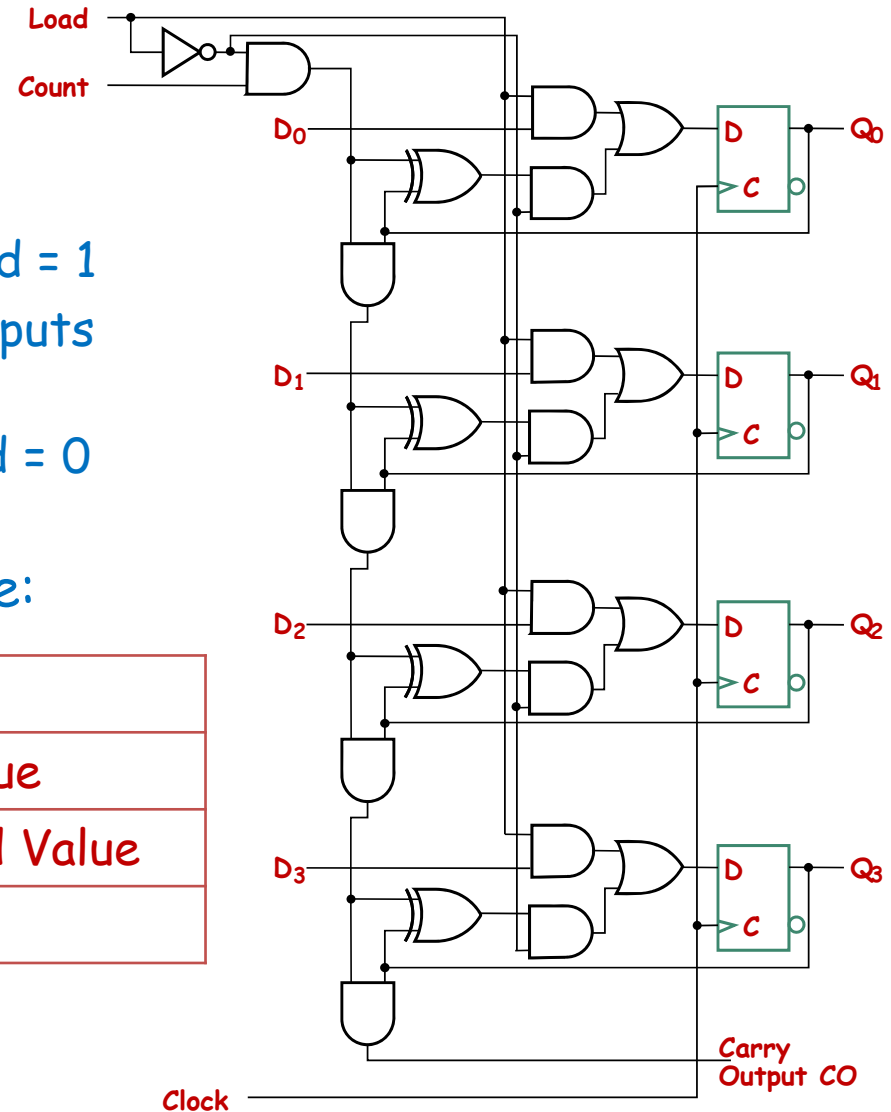

# Design Example: Synchronous BCD

---

- ✓ Use the sequential logic model to design a synchronous BCD counter with D flip-flops
- ✓ Input combinations 1010 through 1111 are don't cares

Current State				Next State			
Q8	Q4	Q2	Q1	Q8	Q4	Q2	Q1
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	0
0	0	1	0	0	0	1	1
0	0	1	1	0	1	0	0
0	1	0	0	0	1	0	1
0	1	0	1	0	1	1	0
0	1	1	0	0	1	1	1
0	1	1	1	1	0	0	0
1	0	0	0	1	0	0	1
1	0	0	1	0	0	0	0

# Synchronous BCD (continued)

---

- ✓ Use **K-Maps** to two-level optimize the next state equations:

$$D1 = \overline{Q1}$$

$$D2 = \overline{Q8}\overline{Q2}Q1 + Q2\overline{Q1}$$

$$D4 = \overline{Q4}Q2Q1 + Q4\overline{Q2} + Q4\overline{Q1}$$

$$D8 = Q8\overline{Q1} + Q4Q2Q1$$

- ✓ The logic diagram can be draw from these equations
  - An asynchronous or synchronous reset should be added
- ✓ What happens if the counter is perturbed by a power disturbance or other interference and it enters a state other than 0000 through 1001?

# Synchronous BCD (continued)

- ✓ Find the actual values of the six next states for the don't care combinations from the equations
- ✓ Find the overall state diagram to assess behavior for the don't care states (states in decimal)


$$D1 = \overline{Q1}$$

$$D2 = \overline{Q8} \overline{Q2} Q1 + Q2 \overline{Q1}$$

$$D4 = \overline{Q4} \overline{Q2} Q1 + Q4 \overline{Q2} + Q4 \overline{Q1}$$

$$D8 = Q8 \overline{Q1} + Q4 Q2 Q1$$

Present State	Next State
Q8 Q4 Q2 Q1	Q8 Q4 Q2 Q1
1 0 1 0	1 0 1 1
1 0 1 1	0 1 0 0
1 1 0 0	1 1 0 1
1 1 0 1	0 1 0 0
1 1 1 0	1 1 0 1
1 1 1 1	1 0 0 0

 

# Synchronous BCD (continued)

---

- ✓ For the BCD counter design, if an invalid state is entered, return to a valid state occurs within two clock cycles
- ✓ Is this adequate? If not:
  - Is a signal needed that indicates that an invalid state has been entered? What is the equation for such a signal?
  - Does the design need to be modified to return from an invalid state to a valid state in one clock cycle?
  - Does the design need to be modified to return from a invalid state to a specific state (such as 0)?
- ✓ The action to be taken depends on:
  - the application of the circuit
  - design group policy

# Counting Modulo N


---

- ✓ The following techniques use an  $n$ -bit binary counter with asynchronous or synchronous clear and/or parallel load:
  - Detect a terminal count of  $N$  in a Modulo- $N$  count sequence to asynchronously Clear the count to 0 or asynchronously Load in value 0
  - Detect a terminal count of  $N - 1$  in a Modulo- $N$  count sequence to Clear the count synchronously to 0
  - Detect a terminal count of  $N - 1$  in a Modulo- $N$  count sequence to synchronously Load in value 0
  - Detect a terminal count and use Load to preset a count of the terminal count value minus  $(N - 1)$
- ✓ Alternatively, custom design a modulo  $N$  counter as done for BCD
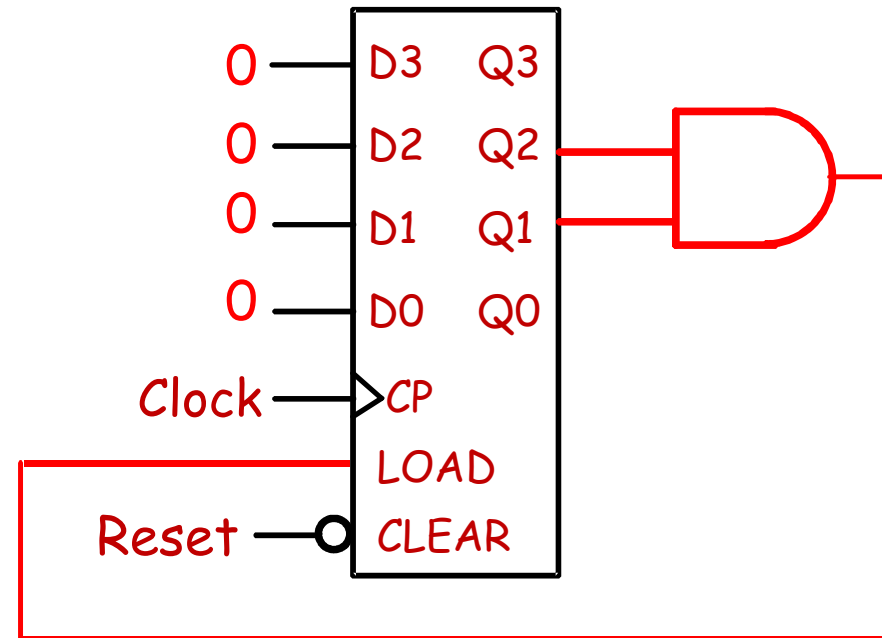
# Counting Modulo 7: Synchronously Load on Terminal Count of 6

---

- ✓ A synchronous 4-bit binary counter with a synchronous load and an asynchronous clear is used to make a Modulo 7 counter
- ✓ Use the Load feature to detect the count "6" and load in "zero". This gives a count of 0, 1, 2, 3, 4, 5, 6, 0, 1, 2, 3, 4, 5, 6, 0, ...
- ✓ Using don't cares for states above 0110





 
# Counting Modulo 6: Synchronously Preset 9 on Reset and Load 9 on Terminal Count 14

✓ A synchronous, 4-bit binary counter with a synchronous Load is to be used to make a Modulo 6 counter.

✓ Use the Load feature to preset the count to 9 on Reset and detection of count 14.



✓ This gives a count of 9, 10, 11, 12, 13, 14, 9, 10, 11, 12, 13, 14, 9, ...

✓ If the terminal count is 15 detection is usually built in as Carry Out (CO)

Example 4: Design a modulo-8 up-counter which counts in the way specified below, use J-K FF

---

Decimal	Gray
0	000
1	001
2	011
3	010
4	110
5	111
6	101
7	100

# Example 4: TRUTH TABLE



---

present state			next state		
$Y_3$	$Y_2$	$Y_1$	$Y_{3+}$	$Y_{2+}$	$Y_{1+}$
0	0	0	0	0	1
0	0	1	0	1	1
0	1	0	1	1	0
0	1	1	0	1	0
1	0	0	0	0	0
1	0	1	1	0	0
1	1	0	1	1	1
1	1	1	1	0	1


# Example 4: Gray code counter

---

$y_3$

  


$$J_{y_3} = y_2 \bar{y}_1$$

 


$$K_{y_3} = \bar{y}_2 y_1$$

# Example 4: Gray code counter


---

 

$y_2$

 


$$J_{y_2} = \bar{y}_3 y_1$$

 


$$K_{y_2} = y_3 y_1$$

# Example 4: Gray code counter

 

$y_1$

 

$$J_{y_1} = \bar{y}_3 \bar{y}_2 + y_3 y_2$$

$$K_{y_1} = \bar{y}_2 y_3 + y_2 \bar{y}_3$$

# Objective: Eliminate redundant states

---

- ✓ Reduce the number of states in the state table to the minimum.
  - Remove redundant states
  - Use don't cares effectively
- ✓ Reduction to the minimum number of states reduces
  - The number of F/Fs needed
  - Reduces the number of next states that has to be generated  $\Rightarrow$  Reduced logic.

# An example circuit

---


- ✓ A sequential circuit has one input  $X$  and one output  $Z$ .
- ✓ The circuit looks at the groups of four consecutive inputs and sets  $Z=1$  if the input sequence 0101 or 1001 occurs.
- ✓ The circuit returns to the reset state after four inputs.
- ✓ Design the Mealy machine.




 
# Elimination of Redundant States

- ✓ When first setting up the state table, we will not be overly concerned with inclusion of extra states, and when the table is complete, we will eliminate any redundant states.



# State table

---

- ✓ Set up a table for all the possible input combinations

Input Sequence	Present State	Next State		Present Output	
		X = 0	X = 1	X = 0	X = 1
reset	A	B	C	0	0
0	B	D	E	0	0
1	C	F	G	0	0
00	D	H	I	0	0
01	E	J	K	0	0
10	F	L	M	0	0
11	G	N	P	0	0
000	H	A	A	0	0
001	I	A	A	0	0
010	J	A	A	0	1
011	K	A	A	0	0
100	L	A	A	0	1
101	M	A	A	0	0
110	N	A	A	0	0
111	P	A	A	0	0

- ✓ For the two sequences when the last bit is a 1 return to reset with Z=1.

# Note on state table generation

- ✓ When generated by looking at all combinations of inputs the state table is far from minimal.
- ✓ First step is to remove redundant states.
  - There are states that you cannot tell apart
    - Such as H and I - both have A with Z=0 as output.
    - State H is equivalent to State I and state I can be removed from the table.
    - Examining table shows states K, M, N and P are also the same - they can be deleted.
    - States J and L are also equivalent.

Input Sequence	Present State	Next State		Present Output	
		X = 0	X = 1	X = 0	X = 1
reset	A	B	C	0	0
0	B	D	E	0	0
1	C	F	G	0	0
00	D	H	I	0	0
01	E	J	K	0	0
10	F	L	M	0	0
11	G	N	P	0	0
000	H	A	A	0	0
001	I	A	A	0	0
010	J	A	A	0	1
011	K	A	A	0	0
100	L	A	A	0	1
101	M	A	A	0	0
110	N	A	A	0	0
111	P	A	A	0	0

# Reduction continued

- ✓ Having made these reductions move up to the D E F G section where the next state entries have been changed.
- ✓ Note that State D and State G are equivalent.
- ✓ State E is equivalent to F.
- ✓ The result in a reduced state table.


Present State	Next State		Present Output	
	X = 0	X = 1	X = 0	X = 1
A	B	C	0	0
B	D	E	0	0
C	<del>F</del> E	<del>G</del> D	0	0
D	H	I	0	0
E	J	K	0	0
<del>F</del>	<del>L</del> J	<del>M</del> H	0	0
<del>G</del>	<del>N</del> H	<del>R</del> H	0	0
H	A	A	0	0
<del>I</del>	A	A	0	0
J	A	A	0	1
<del>K</del>	A	A	0	0
<del>L</del>	A	A	0	1
<del>M</del>	A	A	0	0
<del>N</del>	A	A	0	0
<del>P</del>	A	A	0	0

# The result

- ✓ Reduced state table and graph

Present State	Next State		Output	
	X = 0	X = 1	X = 0	X = 1
A	B	C	0	0
B	D	E	0	0
C	E	D	0	0
D	H	H	0	0
E	J	H	0	0
H	A	A	0	0
J	A	A	0	1


(a)

 

- ✓ Original - 15 states - reduced 7 states
 
# Elimination of Redundant States

- ✓ Design a binary checker that has in input a sequence of BCD numbers and for every four bits (LSB order) has output 0 if the number is  $0 \leq N \leq 9$  and 1 if  $10 \leq N \leq 15$




# Elimination of Redundant States

- ✓ Design a binary checker that has in input a sequence of BCD numbers and for every four bits (LSB order) has output 0 if the number is  $0 \leq N \leq 9$  and 1 if  $10 \leq N \leq 15$

Input Sequence	Present State	Next State		Present Output	
		$X = 0$	$X = 1$	$X = 0$	$X = 1$
reset	<i>A</i>	<i>B</i>	<i>C</i>	0	0
0	<i>B</i>	<i>D</i>	<i>E</i>	0	0
1	<i>C</i>	<i>F</i>	<i>G</i>	0	0
00	<i>D</i>	<i>H</i>	<i>I</i>	0	0
01	<i>E</i>	<i>J</i>	<i>K</i>	0	0
10	<i>F</i>	<i>L</i>	<i>M</i>	0	0
11	<i>G</i>	<i>N</i>	<i>P</i>	0	0
000	<i>H</i>	<i>A</i>	<i>A</i>	0	0
001	<i>I</i>	<i>A</i>	<i>A</i>	0	1
010	<i>J</i>	<i>A</i>	<i>A</i>	0	1
011	<i>K</i>	<i>A</i>	<i>A</i>	0	1
100	<i>L</i>	<i>A</i>	<i>A</i>	0	0
101	<i>M</i>	<i>A</i>	<i>A</i>	0	1
110	<i>N</i>	<i>A</i>	<i>A</i>	0	1
111	<i>P</i>	<i>A</i>	<i>A</i>	0	1

# Elimination of Redundant States

---

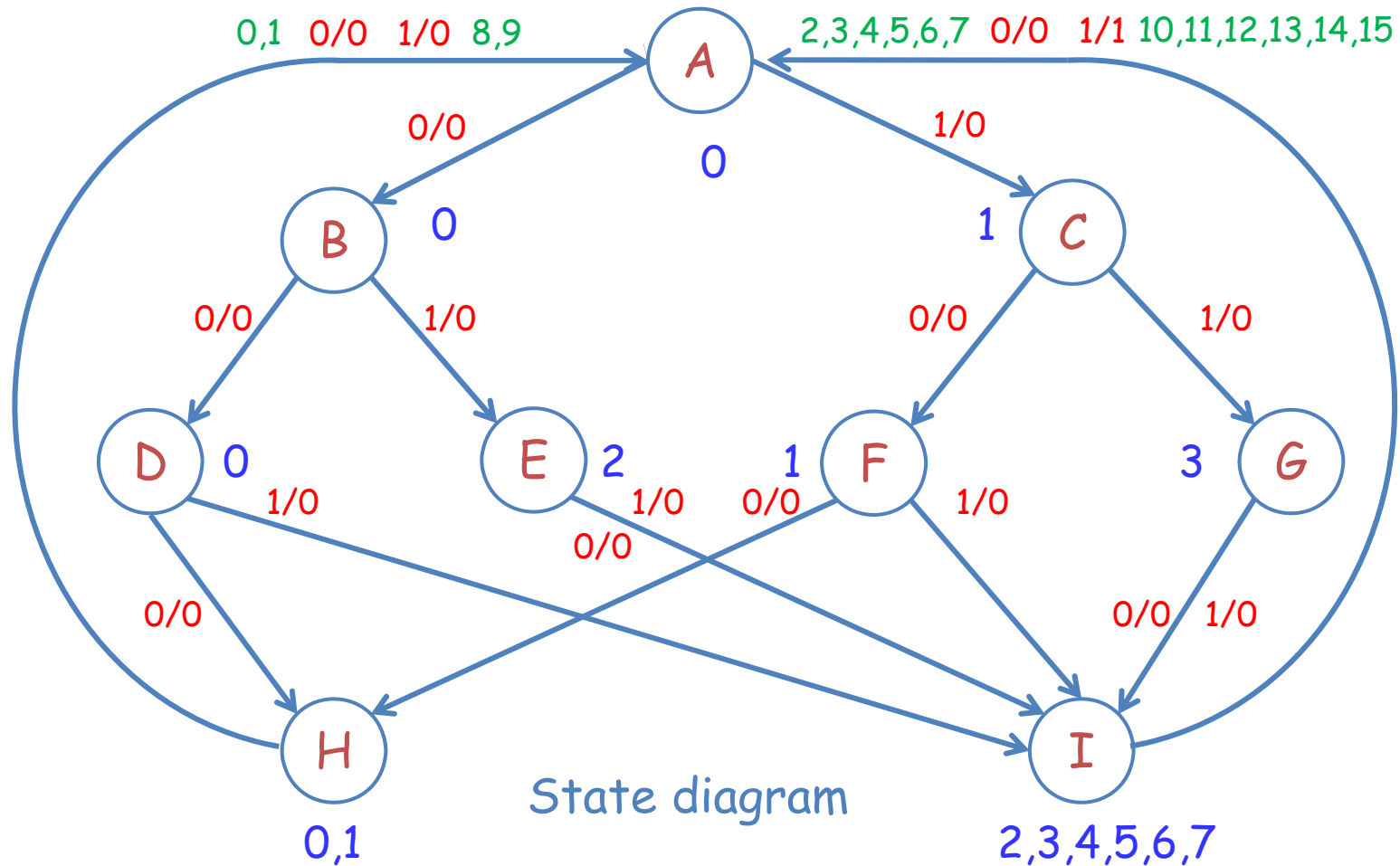



# Elimination of Redundant States


	Input Sequence	Present State	Next State		Present Output	
			X = 0	X = 1	X = 0	X = 1
0	reset	A	B	C	0	0
0	<del>0</del>	B	D	E	0	0
1	<del>1</del>	C	F	G	0	0
0	<del>00</del>	D	H	I	0	0
2	01	E	I	I	0	0
1	<del>10</del>	F	H	I	0	0
3	11	G	I	I	0	0
0,1	000 100	H	A	A	0	0
2,3,4,5,6,7	001 101	I	A	A	0	1
	010 110					
	011 111					

{D,F}, {E,G}, {B,C}

State table

# Elimination of Redundant States

---

 

State diagram

# Equivalence


---

- ✓ Two states are equivalent if there is no way of telling them apart through observation of the circuit inputs and outputs.
- ✓ Formal definition:
  - Let  $N_1$  and  $N_2$  be sequential circuits (not necessarily different). Let  $\underline{X}$  represent a sequence of inputs of arbitrary length. Then state  $p$  in  $N_1$  is equivalent to state  $q$  in  $N_2$  iff  $\lambda_1(p, \underline{X}) = \lambda_2(q, \underline{X})$  for every possible input sequence  $\underline{X}$ .
- ✓ The definition is not practical to apply in practice. Theorem:
  - Two states  $p$  and  $q$  of a sequential circuit are equivalent iff for every single input  $X$ , the outputs are the same and the next states are equivalent, that is,  $\lambda(p, X) = \lambda(q, X)$  and  $\delta(p, X) = \delta(q, X)$  where  $\lambda(p, X)$  is the output given present state  $p$  and input  $X$ , and  $\delta(p, X)$  is the next state given the present state  $p$  and input  $X$ .
- ✓ So the outputs have to be the same and the next states equivalent.
 
# Implication Tables

---

- ✓ A procedure for finding all the equivalent states in a state table.
- ✓ Use an implication table - a chart that has a square for each pair of states.




# Step 1

---

- ✓ Use a X in the square to eliminate output incompatible states.
- ✓ 1<sup>st</sup> output of **a** differs from **c, e, f, and h**

Present State	Next State		Present Output
	X = 0	1	
a	d	c	0
b	f	h	0
c	e	d	1
d	a	e	0
e	c	a	1
f	f	b	1
g	b	h	0
h	c	g	1

 


# Step 1 continued

---

- ✓ Continue to remove output incompatible states


Present State	Next State		Present Output
	$X = 0$	1	
<i>a</i>	<i>d</i>	<i>c</i>	0
<i>b</i>	<i>f</i>	<i>h</i>	0
<i>c</i>	<i>e</i>	<i>d</i>	1
<i>d</i>	<i>a</i>	<i>e</i>	0
<i>e</i>	<i>c</i>	<i>a</i>	1
<i>f</i>	<i>f</i>	<i>b</i>	1
<i>g</i>	<i>b</i>	<i>h</i>	0
<i>h</i>	<i>c</i>	<i>g</i>	1

 

# Now what?



- ✓ Implied pair are now entered into each non X square.
- ✓ Here  $a \equiv b$  iff  $d \equiv f$  and  $c \equiv h$

Present State	Next State		Present Output
	X = 0	1	
a	d	c	0
b	f	h	0
c	e	d	1
d	a	e	0
e	c	a	1
f	f	b	1
g	b	h	0
h	c	g	1

 
  
# Self redundant pairs



- ✓ **Self redundant pairs** are removed, i.e., in square a-d it contains a-d.





 
 
# Next pass

- ✓ X all squares with implied pairs that are not compatible.
- ✓ Such as in **a-b** have **d-f** which has an X in it.
- ✓ Run through the chart until no further X's are found.


  
# Final step

- ✓ Note that  $a-d$  is not  $X$  and is equivalent if  $c \equiv e$ , and the same for  $c-e$ : is not  $X$  and is equivalent if  $a \equiv d$ . We can conclude that  $a \equiv d$ , i.e. and  $c \equiv e$ .



# Reduced table

---

- ✓ Removing equivalent states.

Present State	Next State		Present Output
	X = 0	1	
<i>a</i>	<i>d</i>	<i>c</i>	0
<i>b</i>	<i>f</i>	<i>h</i>	0
<i>c</i>	<i>e</i>	<i>d</i>	1
<i>d</i>	<i>a</i>	<i>e</i>	0
<i>e</i>	<i>c</i>	<i>a</i>	1
<i>f</i>	<i>f</i>	<i>b</i>	1
<i>g</i>	<i>b</i>	<i>h</i>	0
<i>h</i>	<i>c</i>	<i>g</i>	1

Present State	Next State		Present Output
	X = 0	1	
<i>a</i>	<i>a</i>	<i>c</i>	0
<i>b</i>	<i>f</i>	<i>h</i>	0
<i>c</i>	<i>c</i>	<i>a</i>	1
<i>f</i>	<i>f</i>	<i>b</i>	1
<i>g</i>	<i>b</i>	<i>h</i>	0
<i>h</i>	<i>c</i>	<i>g</i>	1

## Summary of method


---

- ✓ Construct a chart with a square for each pair of states.
- ✓ Compare each pair of rows in the state table. X a square if the outputs are different. If the output is the same enter the implied pairs. Remove redundant pairs. If the implied pair is the same place a check mark as  $i \equiv j$ .
- ✓ Go through the implied pairs and X the square when an implied pair is incompatible.
- ✓ Repeat until no more Xs are added.
- ✓ For any remaining squares not Xed,  $i \equiv j$ .

# Another example

---

- ✓ Consider the state diagram:

 

Present State	NEXT STATE		OUTPUT	
	X=0	X=1	X=0	X=1
S0	S1	S4	0	0
S1	S1	S2	0	0
S2	S3	S4	1	0
S3	S5	S2	0	0
S4	S3	S4	0	0
S5	S1	S2	0	1


# Set up Implication Chart

- ✓ Remove output incompatible states
- ✓ and indicate implied pairs


Present State	NEXT STATE		OUTPUT	
	X=0	X=1	X=0	X=1
S0	S1	S4	0	0
S1	S1	S2	0	0
S2	S3	S4	1	0
S3	S5	S2	0	0
S4	S3	S4	0	0
S5	S1	S2	0	1

Check implied pairs and X

1<sup>st</sup> pass

 

2<sup>nd</sup> pass

 

- ✓ In this case the state table is minimal as no state reduction can be done.

# Implication Table (another example)

Present State	Next State		Output	
	X=0	X=1	X=0	X=1
<i>a</i>	<i>d</i>	<i>b</i>	0	0
<i>b</i>	<i>e</i>	<i>a</i>	0	0
<i>c</i>	<i>g</i>	<i>f</i>	0	1
<i>d</i>	<i>a</i>	<i>d</i>	1	0
<i>e</i>	<i>a</i>	<i>d</i>	1	0
<i>f</i>	<i>c</i>	<i>b</i>	0	0
<i>g</i>	<i>a</i>	<i>e</i>	1	0

- ✓ It's clear that (e,d) are equivalent. And this leads (a,b) and (e,g) to be equivalent too.
- ✓ Finally we have [(a,b) , c , (e,d,g) , f ] so four states.
- ✓ So the original flow table can be reduced to:

<i>b</i>	<i>d, e</i> ✓					
<i>c</i>	x	x				
<i>d</i>	x	x	x			
<i>e</i>	x	x	x	✓		
<i>f</i>	<i>c, d</i> x	<i>c, e</i> x <i>a, b</i>	x	x	x	
<i>g</i>	x	x	x	<i>d, e</i> ✓	<i>d, e</i> ✓	x
	<i>a</i>	<i>b</i>	<i>c</i>	<i>d</i>	<i>e</i>	<i>f</i>

# Implication Table

Present State	Next State		Output	
	X=0	X=1	X=0	X=1
<i>a</i>	<i>d</i>	<i>b</i>	0	0
<i>b</i>	<i>e</i>	<i>a</i>	0	0
<i>c</i>	<i>g</i>	<i>f</i>	0	1
<i>d</i>	<i>a</i>	<i>d</i>	1	0
<i>e</i>	<i>a</i>	<i>d</i>	1	0
<i>f</i>	<i>c</i>	<i>b</i>	0	0
<i>g</i>	<i>a</i>	<i>e</i>	1	0

<i>b</i>	<i>d, e</i> ✓					
<i>c</i>	x	x				
<i>d</i>	x	x	x			
<i>e</i>	x	x	x	✓		
<i>f</i>	<i>c, d</i> x	<i>c, e</i> x <i>a, b</i>	x	x	x	
<i>g</i>	x	x	x	<i>d, e</i> ✓	<i>d, e</i> ✓	x
	<i>a</i>	<i>b</i>	<i>c</i>	<i>d</i>	<i>e</i>	<i>f</i>

Present State	Next State		Output	
	X=0	X=1	X=0	X=1
<i>a</i>	<i>d</i>	<i>a</i>	0	0
<i>c</i>	<i>d</i>	<i>f</i>	0	1
<i>d</i>	<i>a</i>	<i>d</i>	1	0
<i>f</i>	<i>c</i>	<i>a</i>	0	0