

Example 1: Design a modulo-8 binary-up counter using T- Flip Flop

- ✓ Modulo 8 counter : Counts upto 7. So we need three Flip-flops for eight states

Truth Table

Y_3	Y_2	Y_1	Y_{3+}	Y_{2+}	Y_{1+}	Z
0	0	0	0	0	1	0
0	0	1	0	1	0	0
0	1	0	0	1	1	0
0	1	1	1	0	0	0
1	0	0	1	0	1	0
1	0	1	1	1	0	0
1	1	0	1	1	1	0
1	1	1	0	0	0	1

“ Z “ is the output

Modulo-8 counter

$$y_{3+} = \Sigma(3,4,5,6)$$

y_{3+}

		1	1
	1		1

y_{3+}

	1	1	
\bar{q} -half			q -half

$$T_{y3} = y_1 y_2$$

Modulo-8 counter

$$y_{2+} = \Sigma(1,2,5,6)$$



	y_{2+}		
	1	1	
1			1

	y_{2+}		
1	1	1	1
\bar{q} -half	q-half		\bar{q} -half

$$T_{y2} = y_1$$

Modulo-8 counter

$$y_{1+} = \Sigma(0,2,4,6)$$

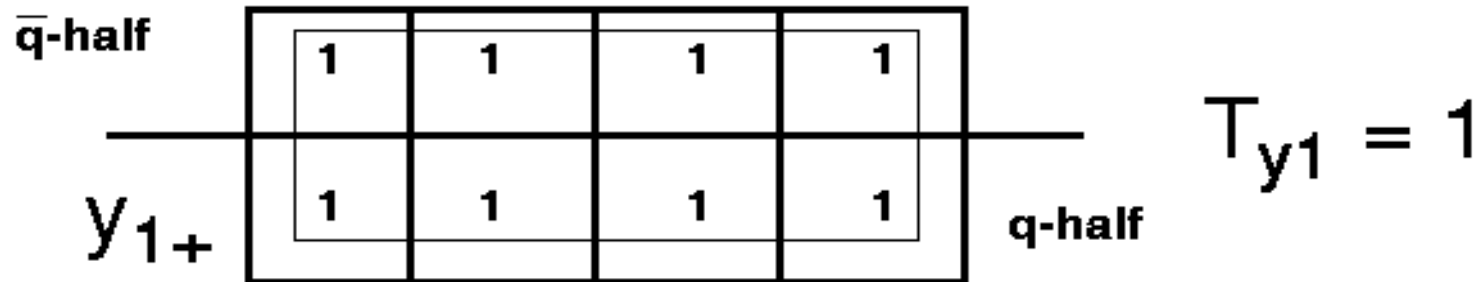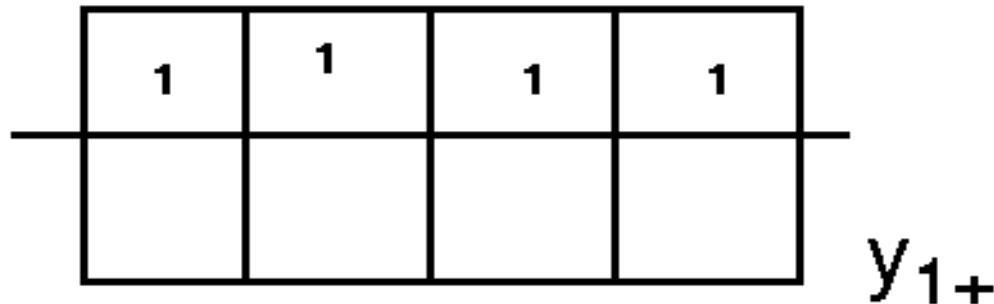



Example 2: Design a modulo-8 binary-up counter with input x using T-Flip Flop

- ✓ Modulo 8 counter : Counts upto 7 . So we need three Flip-flops for eight states

x	y ₃	y ₂	y ₁	y ₃₊	y ₂₊	y ₁₊
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	0	1	0
0	0	1	1	0	1	1
0	1	0	0	1	0	0
0	1	0	1	1	0	1
0	1	1	0	1	1	0
0	1	1	1	1	1	1
1	0	0	0	0	0	1
1	0	0	1	0	1	0
1	0	1	0	0	1	1
1	0	1	1	1	0	0
1	1	0	0	1	0	1
1	1	0	1	1	1	0
1	1	1	0	1	1	1
1	1	1	1	0	0	0


	$y_{3+} = \Sigma(4,5,6,7,11,12,13,14)$
	$y_{2+} = \Sigma(2,3,6,7,9,10,13,14)$
	$y_{1+} = \Sigma(1,3,5,7,8,10,12,14)$

Example 2: modulo 8 counter with I/p x

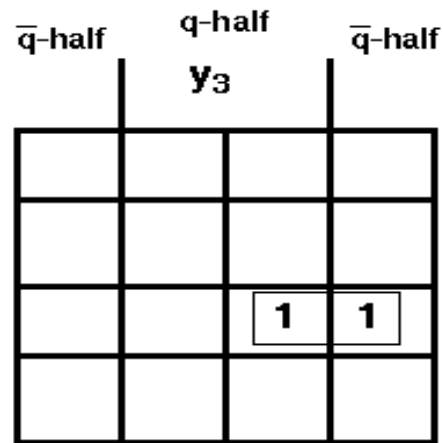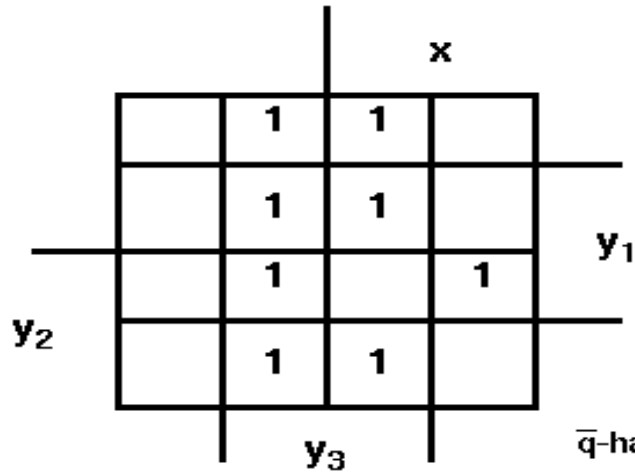


$$T_{y_3} = xy_1y_2$$


Example 2: modulo 8 counter with I/p x

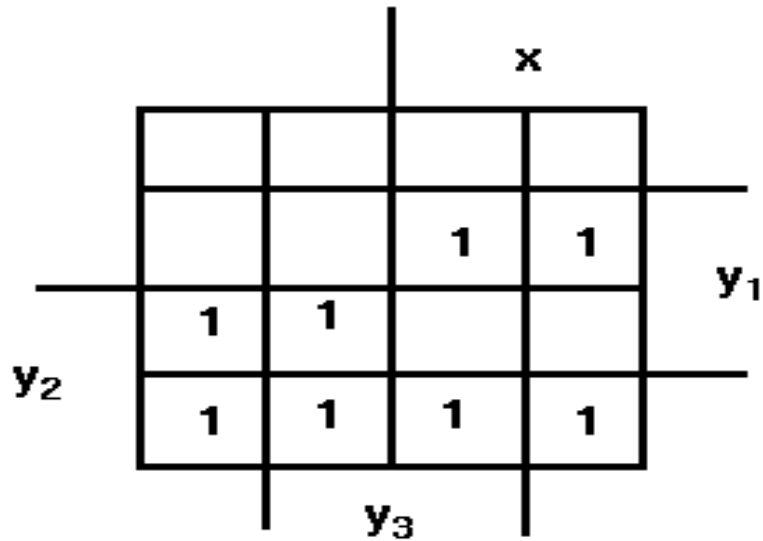


$$T_{y_2} = xy_1$$

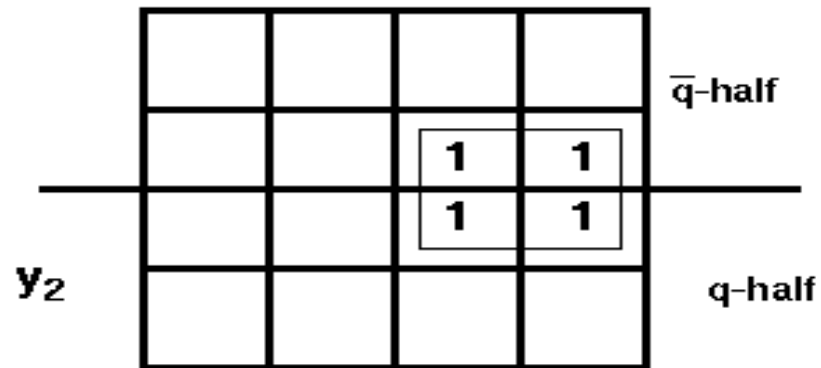

Example 2: modulo 8 counter with I/p x

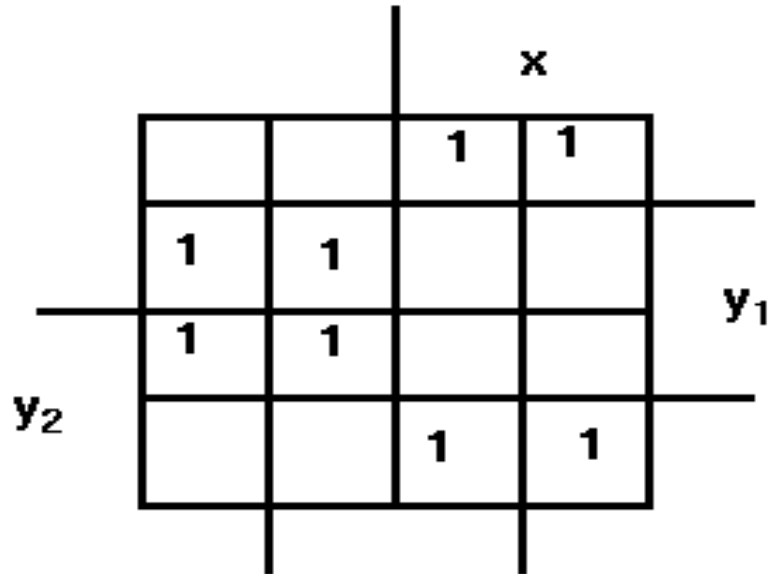

$$T_{y_1} = X$$

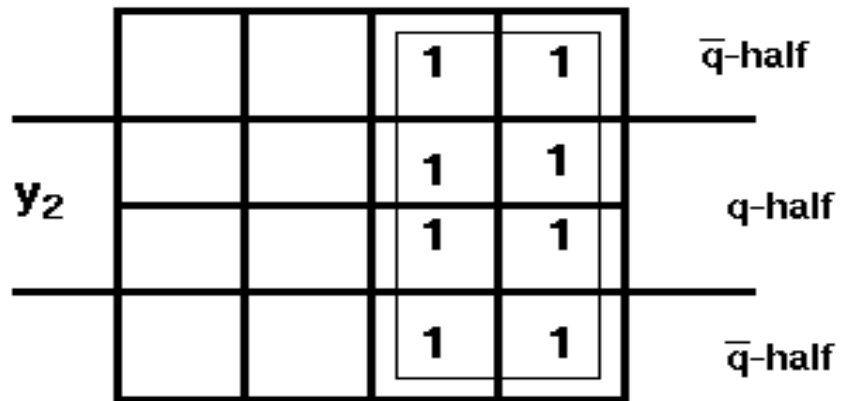



Example 3: Design a binary-down decade counter using SR- Flip Flop without input x

- ✓ Decade Counter: Counts up to 9 . So we need four Flip-Flops for ten states


y_4	y_3	y_2	y_1	y_{4+}	y_{3+}	y_{2+}	y_{1+}
0	0	0	0	1	0	0	1
0	0	0	1	0	0	0	0
0	0	1	0	0	0	0	1
0	0	1	1	0	0	1	0
0	1	0	0	0	0	1	1
0	1	0	1	0	1	0	0
0	1	1	0	0	1	0	1
0	1	1	1	0	1	1	0
1	0	0	0	0	1	1	1
1	0	0	1	1	0	0	0
1	0	1	0	x	x	x	x
1	0	1	1	x	x	x	x
1	1	0	0	x	x	x	x
1	1	0	1	x	x	x	x
1	1	1	0	x	x	x	x
1	1	1	1	x	x	x	x

$y_{4+} = \Sigma(0,9) + \Sigma_x(10,11,12,13,14,15)$
$y_{3+} = \Sigma(5,6,7,8) + \Sigma_x(10,11,12,13,14,15)$
$y_{2+} = \Sigma(3,4,7,8) + \Sigma_x(10,11,12,13,14,15)$
$y_{1+} = \Sigma(0,2,4,6,8) + \Sigma_x(10,11,12,13,14,15)$



Example 3: Binary decade counter

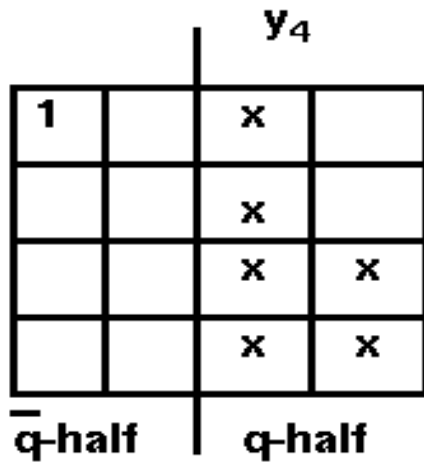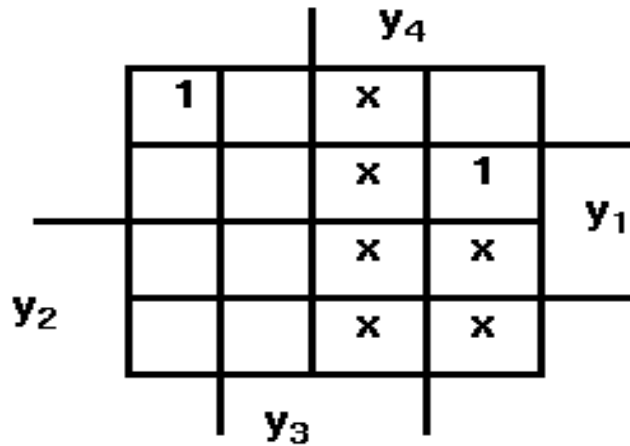


$$S_{y_4} = \bar{y}_1 \bar{y}_2 \bar{y}_3 \bar{y}_4$$

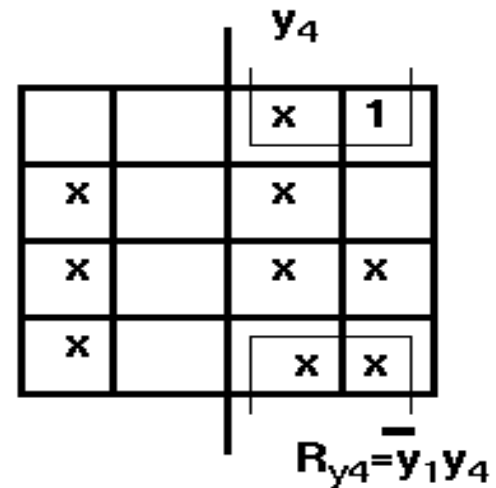

Example 3: Binary decade counter


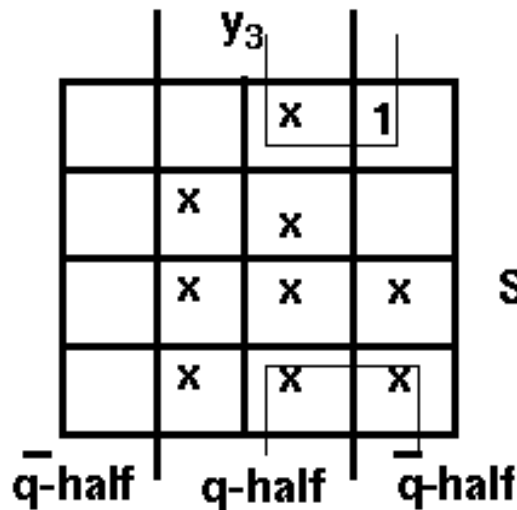
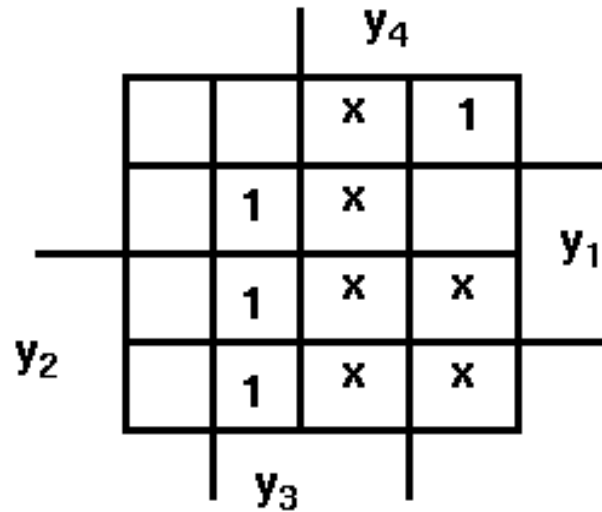


$$S_{y3} = \bar{y}_1 y_4$$



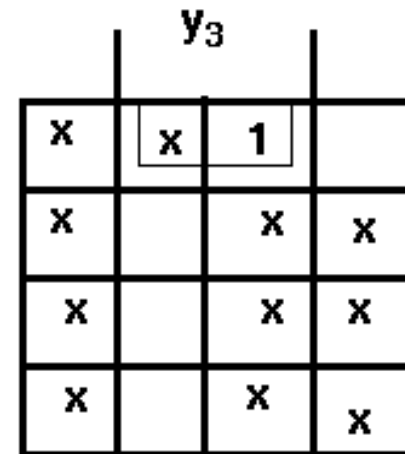


$$R_{y3} = \bar{y}_1 \bar{y}_2 y_3$$

Example 3: Binary decade counter

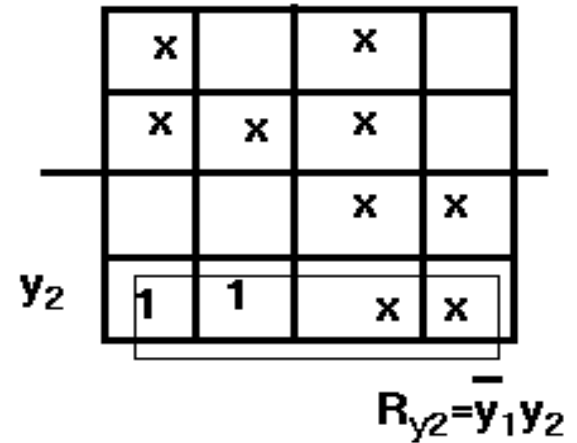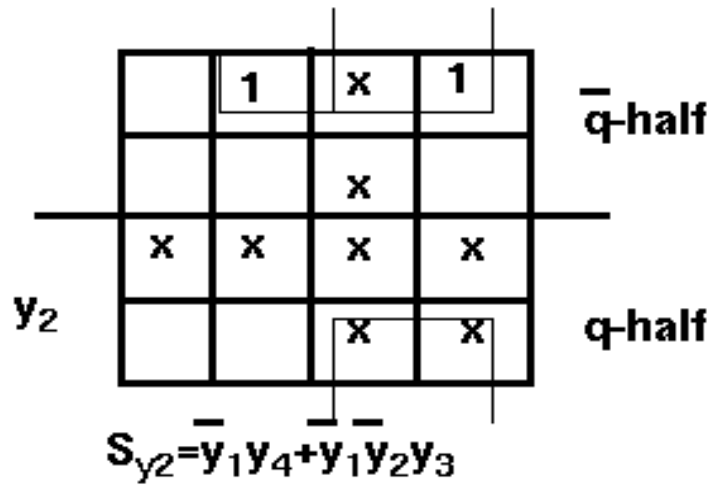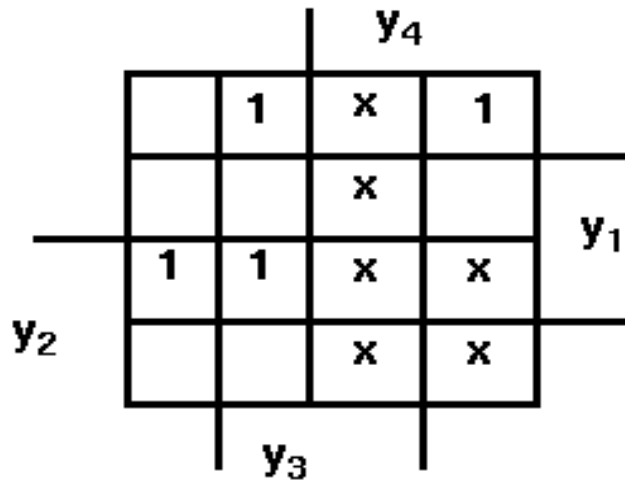

Example 3: Binary decade counter

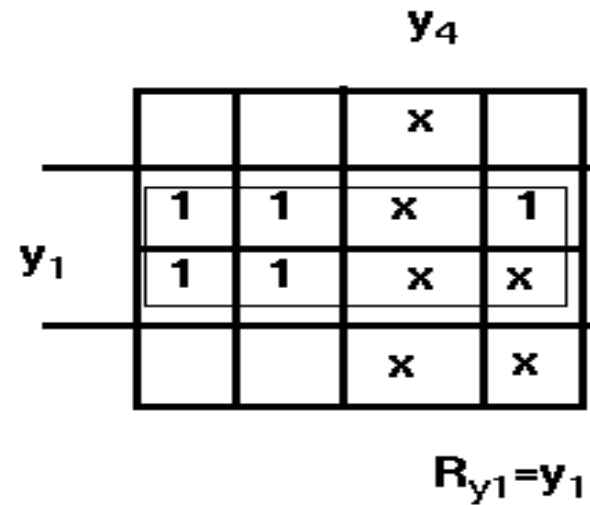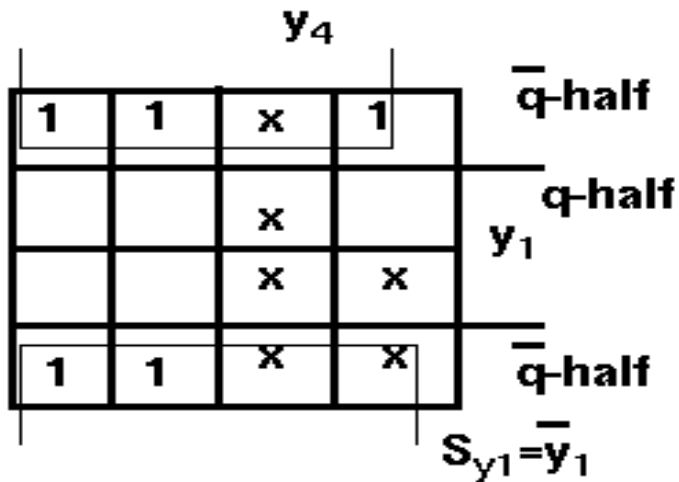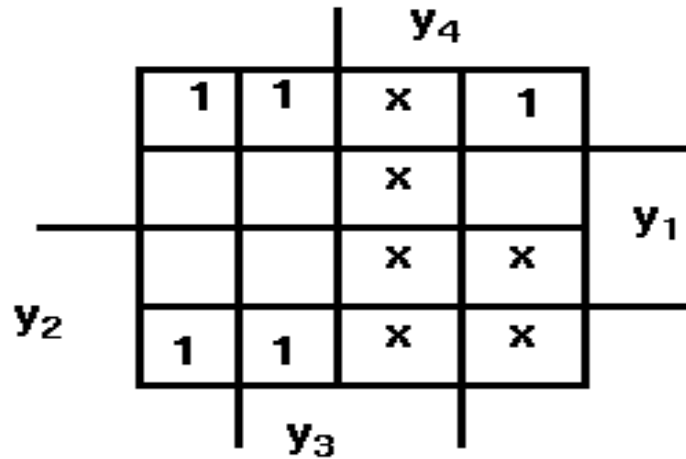

A slightly fancier counter

- ✓ Let's try to design a slightly different two-bit counter:
 - Again, the counter outputs will be 00, 01, 10 and 11.
 - Now, there is a single input, X . When $X=0$, the counter value should *increment* on each clock cycle. But when $X=1$, the value should *decrement* on successive cycles.
- ✓ We'll need two flip-flops again. Here are the four possible states:

00


01

11

10

The complete state diagram and table

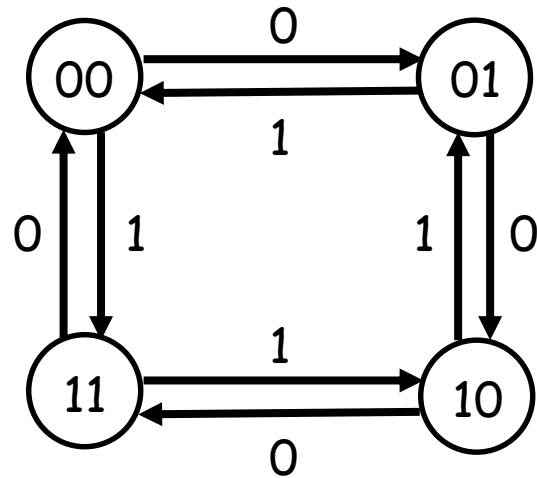- Here's the complete state diagram and state table for this circuit.



Present State		Inputs X	Next State	
Q ₁	Q ₀		Q ₁	Q ₀
0	0	0	0	1
0	0	1	1	1
0	1	0	1	0
0	1	1	0	0
1	0	0	1	1
1	0	1	0	1
1	1	0	0	0
1	1	1	1	0

D flip-flop inputs

- ✓ If we use D flip-flops, then the D inputs will just be the same as the desired next states.
- ✓ Equations for the D flip-flop inputs are shown at the right.
- ✓ Why does $D_0 = Q_0'$ make sense?

Present State		Inputs X	Next State	
Q_1	Q_0		Q_1	Q_0
0	0	0	0	1
0	0	1	1	1
0	1	0	1	0
0	1	1	0	0
1	0	0	1	1
1	0	1	0	1
1	1	0	0	0
1	1	1	1	0

		Q_0		
	0	1	0	1
Q_1	1	0	1	0
		X		

$$D_1 = Q_1 \oplus Q_0 \oplus X$$

		Q_0		
	1	1	0	0
Q_1	1	1	0	0
		X		


$$D_0 = Q_0'$$

Example 5: Synthesis Using T Flip-Flops

- ✓ The synthesis using T flip-flops will be demonstrated by designing a binary counter. An n-bit binary counter consists of n flip-flops that can count in binary from 0 to 2^n-1 . The state diagram of a 3-bit counter is:

$Q(t)$	$Q(t + 1)$	T
0	0	0
0	1	1
1	0	1
1	1	0

(b) T

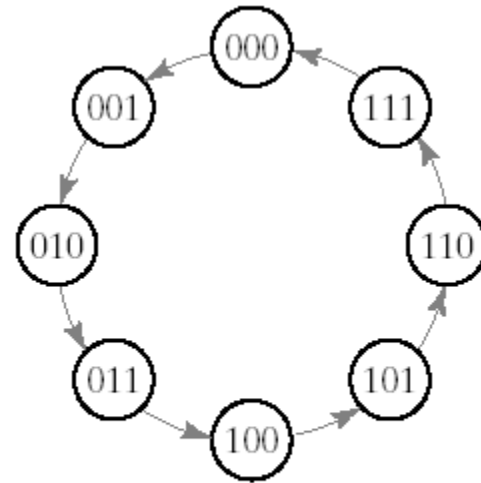

Synthesis Using T Flip-Flops

Table 5-14
State Table for 3-Bit Counter

Present State			Next State			Flip-Flop Inputs		
A_2	A_1	A_0	A_2	A_1	A_0	T_{A2}	T_{A1}	T_{A0}
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	1	1
1	1	1	0	0	0	1	1	1



1

1

Synthesis using T Flip-Flops

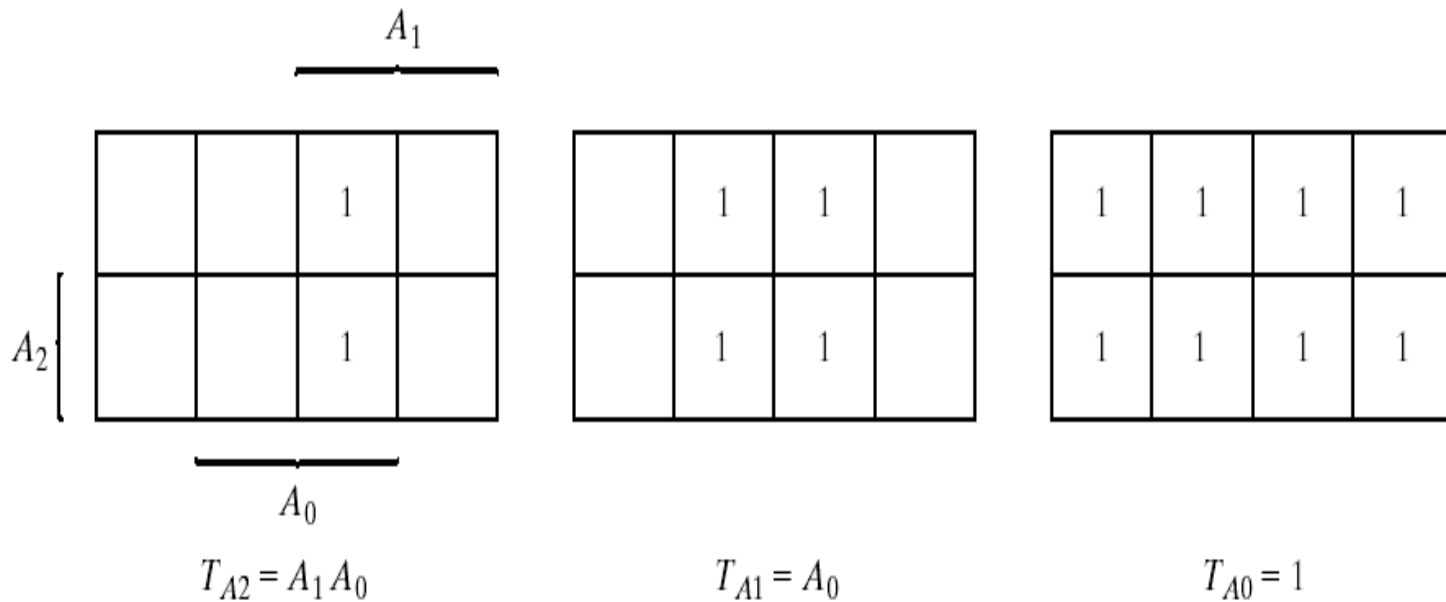


Table 5-14
State Table for 3-Bit Counter

Present State			Next State			Flip-Flop Inputs		
A_2	A_1	A_0	A_2	A_1	A_0	T_{A2}	T_{A1}	T_{A0}
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	1	1
1	1	1	0	0	0	1	1	1

Synthesis Using T Flip-Flops

